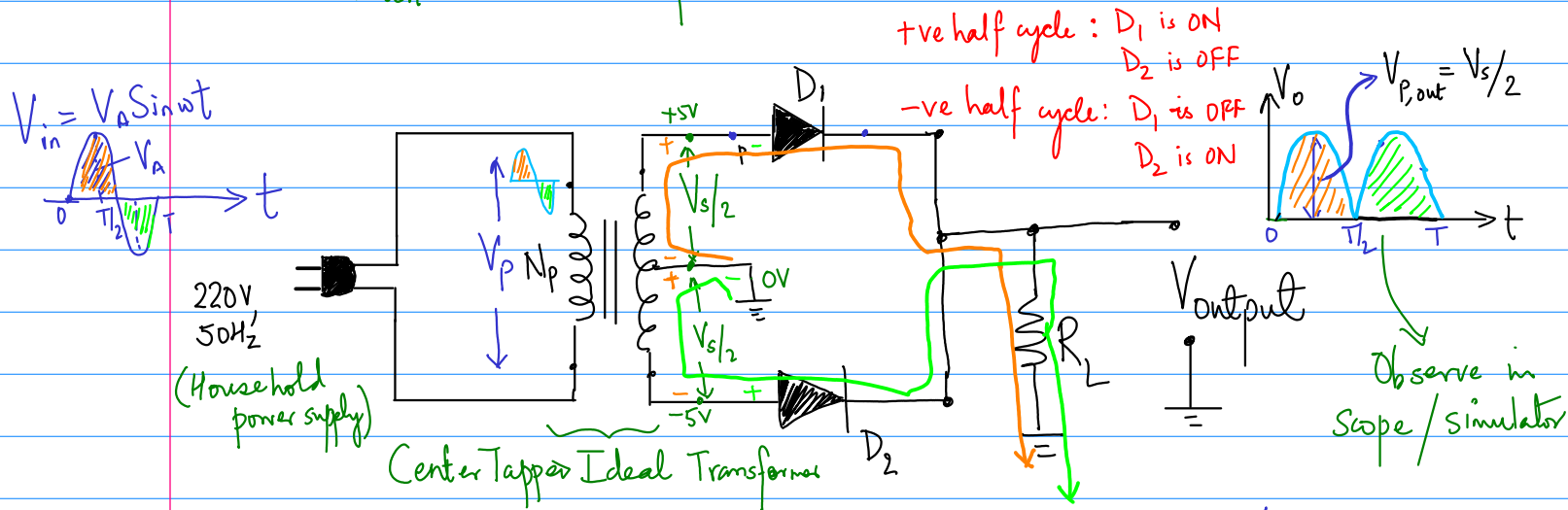


Rectifier and Filter Circuits

Recap:

Full wave rectifier circuit:




$$V_{p,out} = V_s/2 \quad ; \quad V_{ave} = \frac{2 V_{p,out}}{\pi} = \frac{2 \cdot V_s/2}{\pi}$$

For practical diode;

$$V_{p,out} = \left(\frac{V_s}{2} - 0.7V \right)$$

$$\Rightarrow V_{ave} = \frac{2 V_{p,out}}{\pi} = \frac{2}{\pi} \left(\frac{V_s}{2} - 0.7V \right)$$

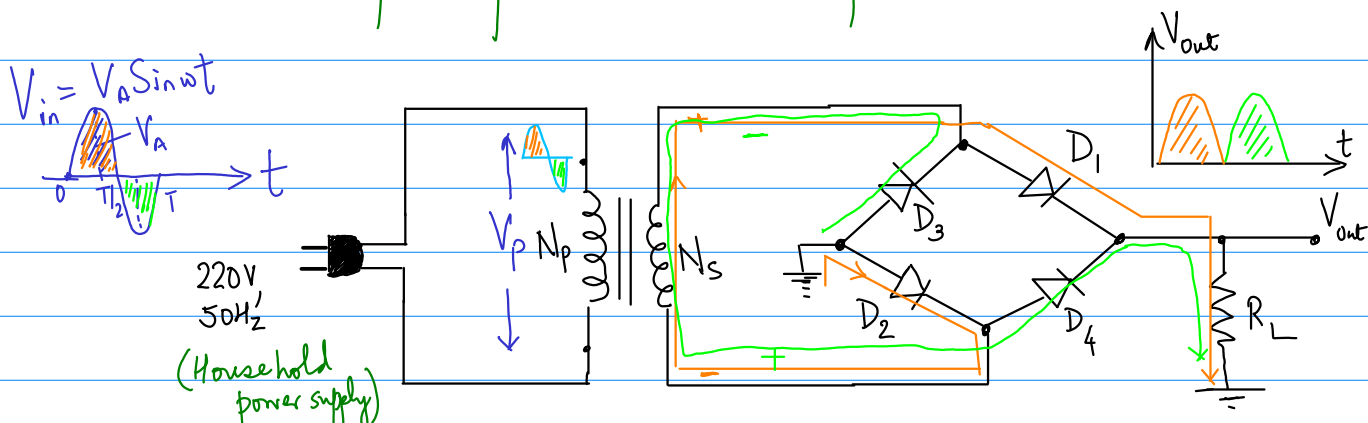Alternate circuit for full-wave rectifier:



for +ve half cycle: D_1 & D_2 - ON ; D_3 & D_4 - OFF

for -ve half cycle: D_3 & D_4 - ON ; D_1 & D_2 - OFF

$$V_s = n V_p = n V_A$$

$$V_{out} = V_s \quad (\text{Considering diodes to be Ideal})$$

$$V_{ave.} = \frac{2 V_{out}}{\pi}$$



For practical circuit:

$$V_{out} = V_s - 1.4 V$$

Since two diodes are replaced with two voltage sources of $0.7 V$ each.

$$V_{ave} = \frac{2}{\pi} (V_s - 1.4 V)$$

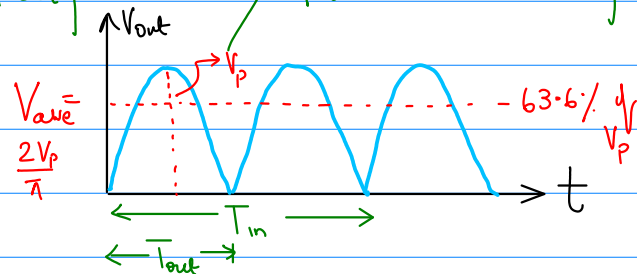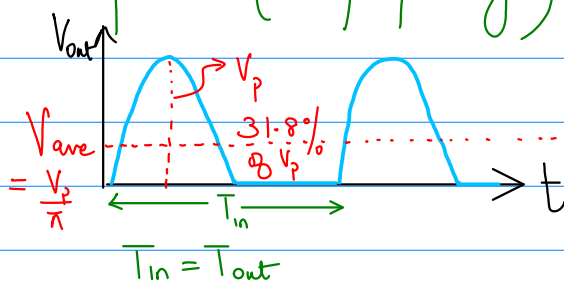Time-period (or frequency) of Half-wave / Full-wave rectifier




- For half-wave rectifier: Time-period of output voltage is same as

input voltage. That is, if input frequency is 50 Hz then output frequency is also 50 Hz.


- For full-wave rectifier, the time-period of output voltage is half of the input voltage. That is, the frequency of output voltage will be 100 Hz for 50 Hz input frequency.

Remember: Output of the rectifier ckt. is time-varying

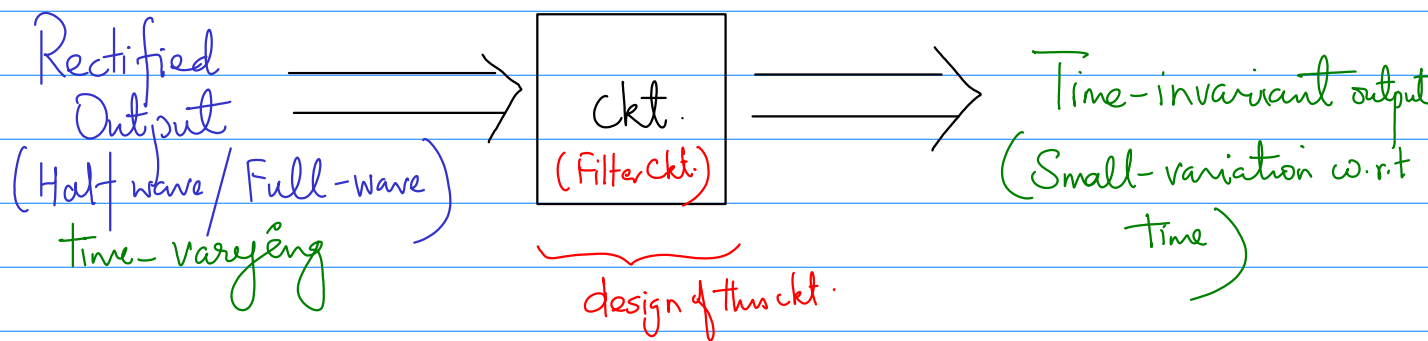⇒ To get time-invariant output, we need another circuit
→ Filter circuit:




RC circuit: (a) charging

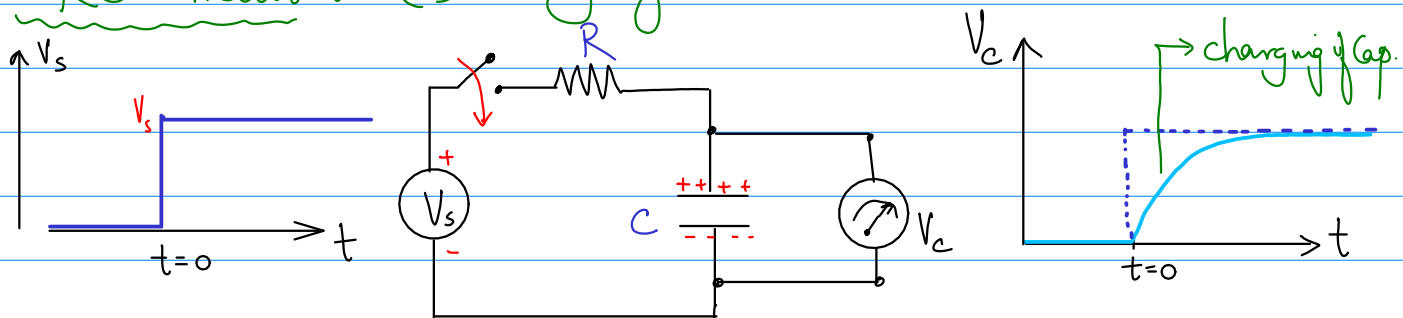

$$V_c(t) = V_s (1 - e^{-t/\tau})$$

Time constant: $\tau = RC$; $t = 5\tau$; $V_c(t) \approx V_s$

b) Discharging :

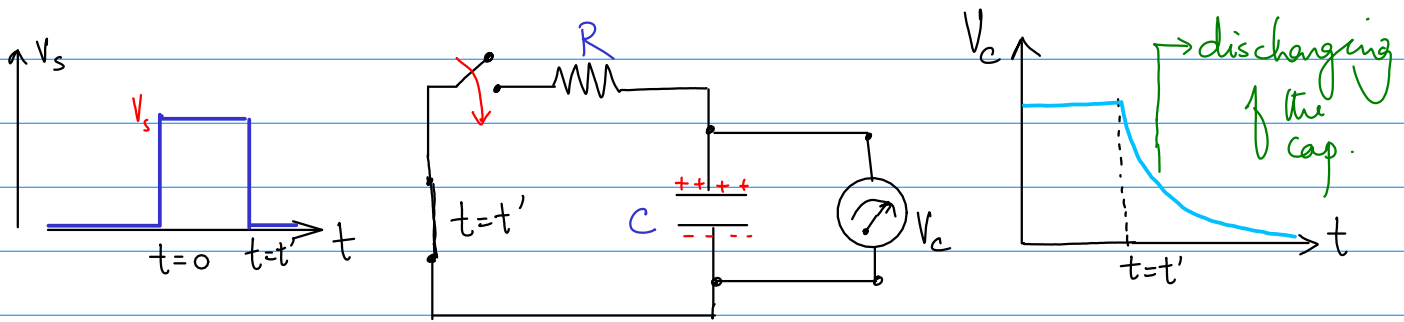

$$V_c(t) = V_s e^{-t/\tau}$$

$$\tau = RC$$

When $t = 5\tau$, then $V_c \approx 0$

