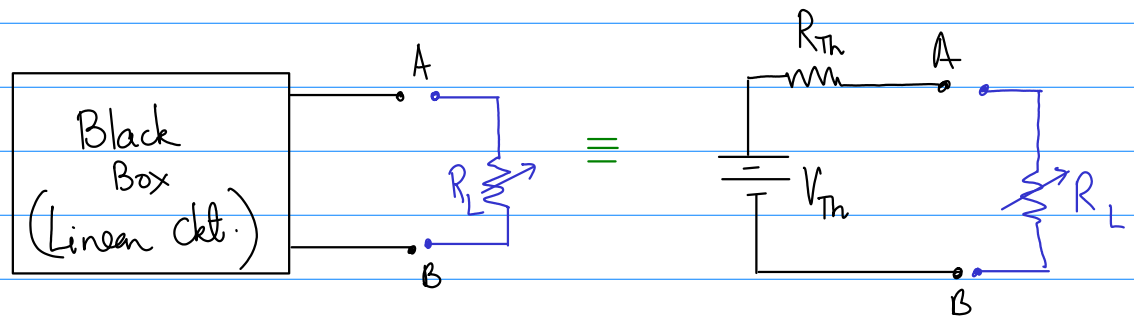


Circuit Theorems


Recap:

- 1) Superposition Theorem
- 2) Thevenin Theorem



Black Box \equiv replaced with a single voltage source V_{Th} & a series resistance R_{Th} .


3) Norton Theorem :

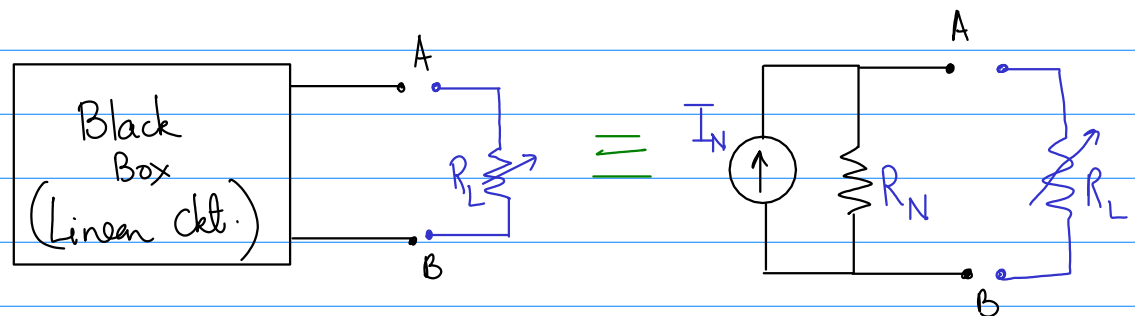

here, $I_N = I_{sc}$ in Thevenin's equivalent ckt.

$$I_N = \frac{V_{Th}}{R_{Th}}$$


$$R_N = R_{Th}$$

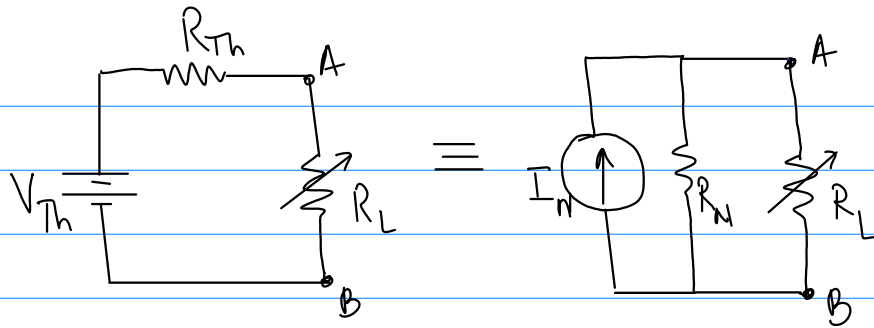

Thevenin's voltage $V_{Th} = V_{oc}$ (open ckt. voltage)

Norton's Current $I_N = I_{sc}$ (short ckt. current)


Example :

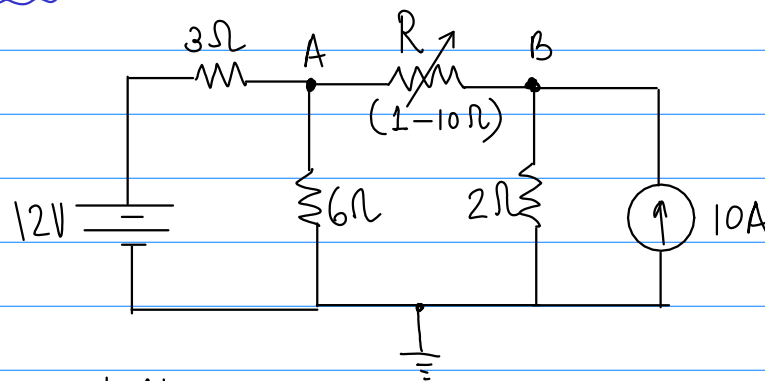

Fill this table :

$R \text{ (in } \Omega \text{)}$	$V_{AB} \text{ (in V)}$	$I_{AB} \text{ (in A)}$
1	2.4 V	2.4 A
2	4.0 V	2 A
3	5.1 V	1.7 A
4	\vdots	\vdots
\vdots	\vdots	\vdots
10	\vdots	\vdots

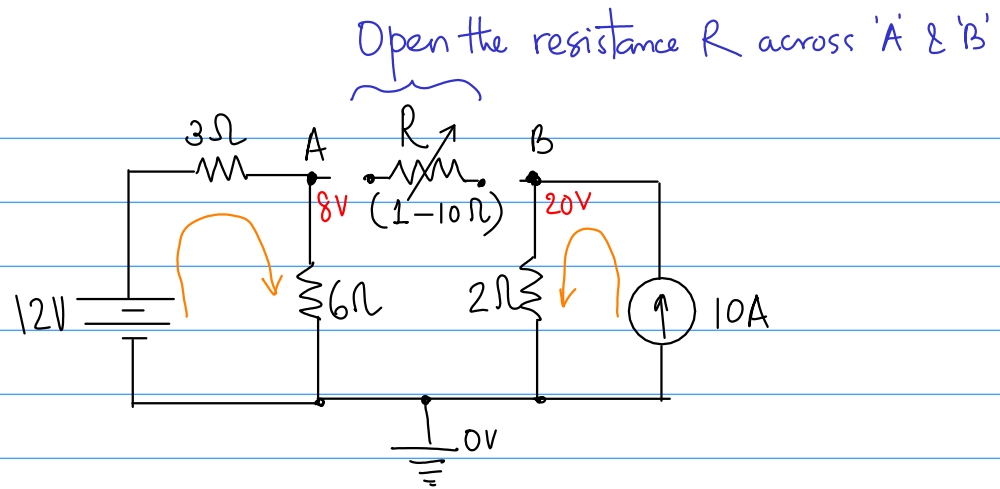Here we make use of Thevenin's theorem :
ie Thevenize the ckt. across the terminals A & B



$$V_{AB} (\text{open ckt.}) = V_A - V_B$$

$$V_B = 2\Omega \cdot 10A = 20V$$


$$V_A = \frac{6\Omega}{3\Omega + 6\Omega} \cdot 12V = 8V$$

$$V_{AB} = V_A - V_B = 8V - 20V = -12V$$

$$V_{Th} = V_{AB} = -12V$$

Determination of R_{Th} :


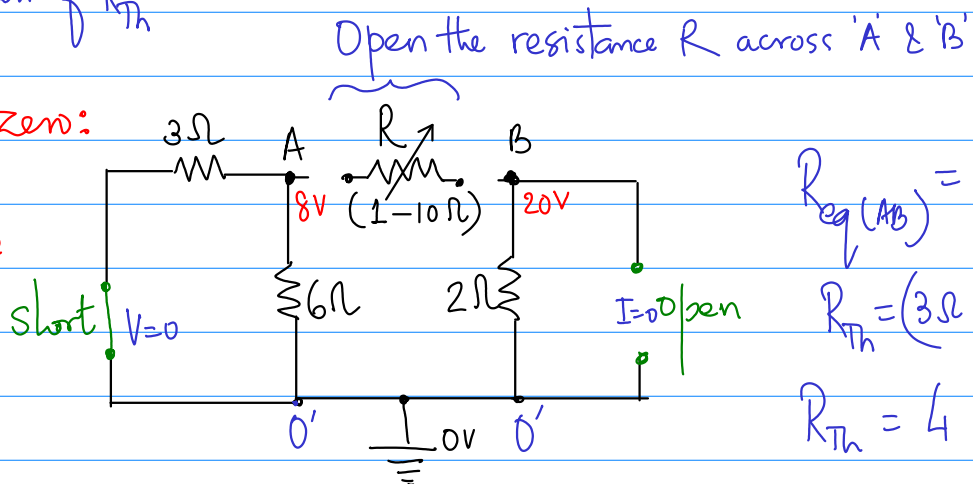
- To make the source zero:
- short voltage source
 - open current source



$$R_{eq(AB)} = R_{Th}$$


$$R_{Th} = (3\Omega \parallel 6\Omega) + 2\Omega$$

$$R_{Th} = 4\Omega$$

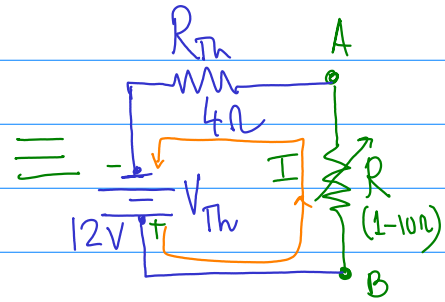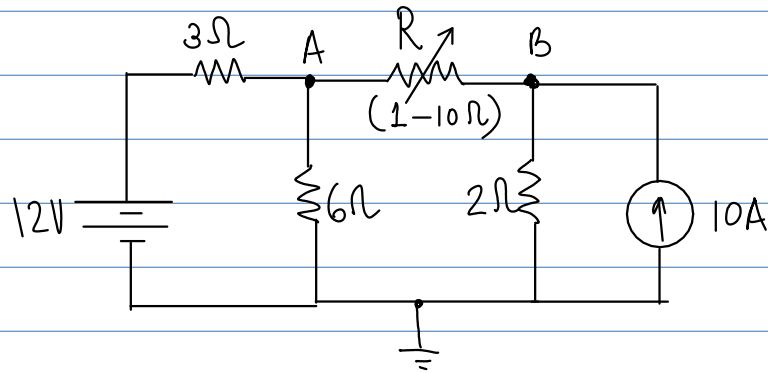


$$I_{AB} = \frac{V_{Th}}{R_{Th} + R} = \frac{12V}{4\Omega + R}$$
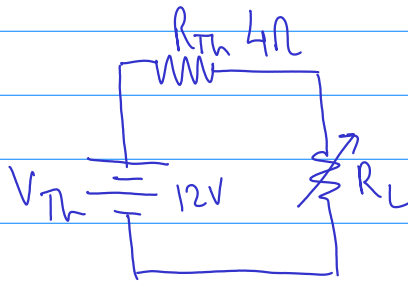
$$V_{AB} = I_{AB} \cdot R = \left[\frac{12V}{4\Omega + R} \right] \cdot R$$



\equiv

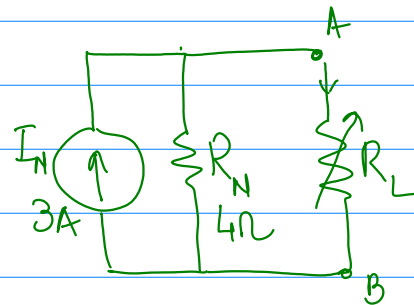

$$I_{AB} =$$

$$V_{AB} =$$

$$I_N = I_{sc} = \frac{V_{Th}}{R_{Th}} = \frac{12V}{4\Omega} = 3A$$