







Name: _____

ID: _____


Assignment - 01

(Submission due : 22 Sep 2023)

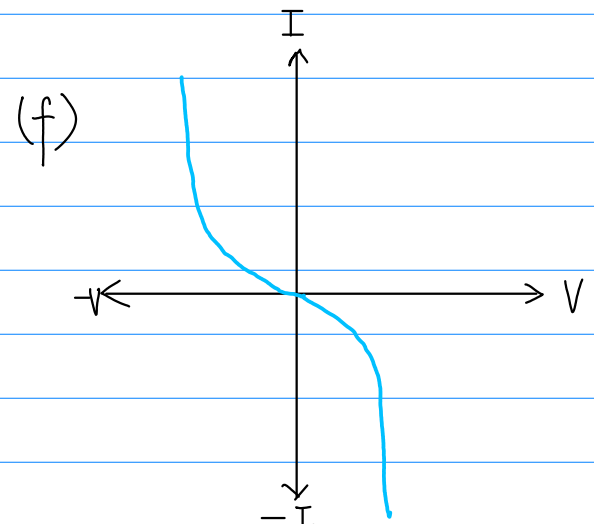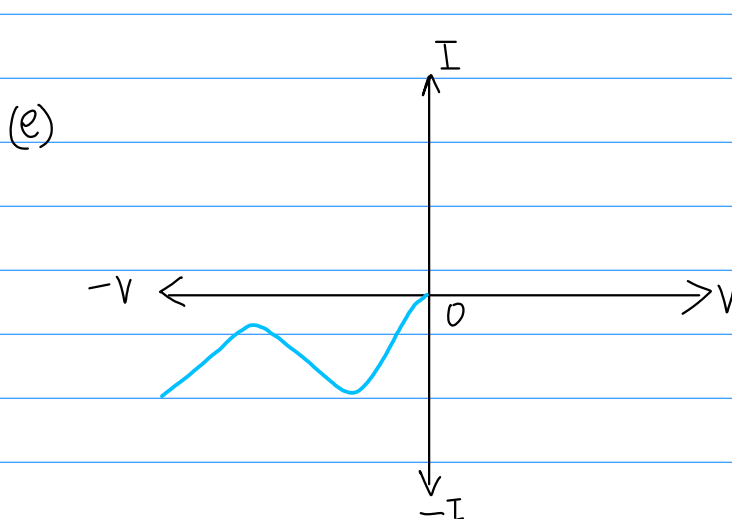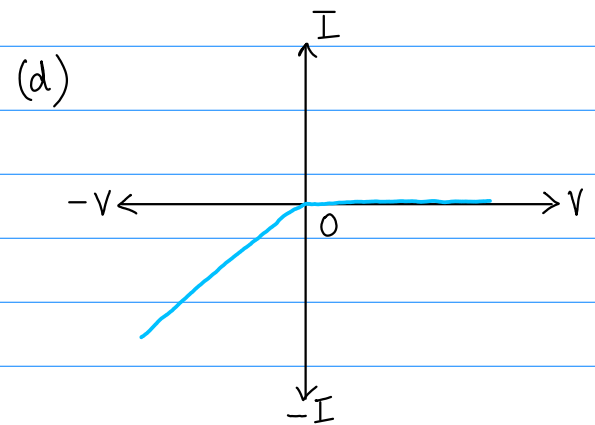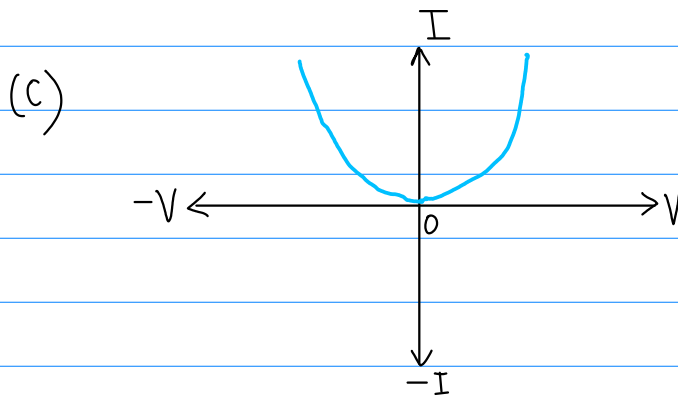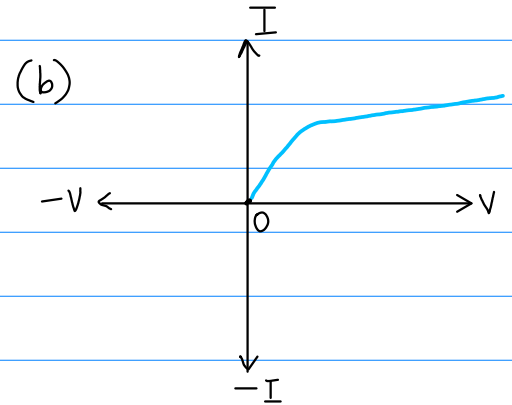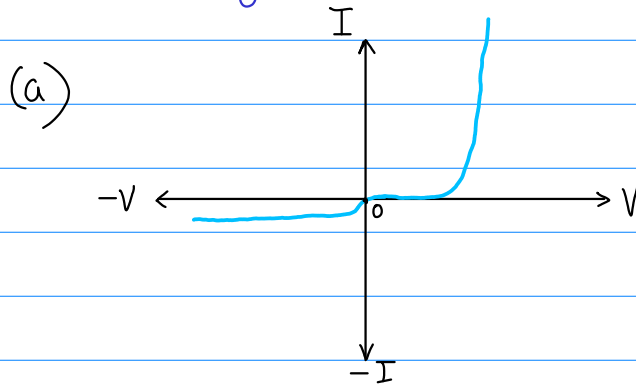
Q 1. The current-voltage characteristics of a circuit element is given below. Identify whether it is Active or Passive element.



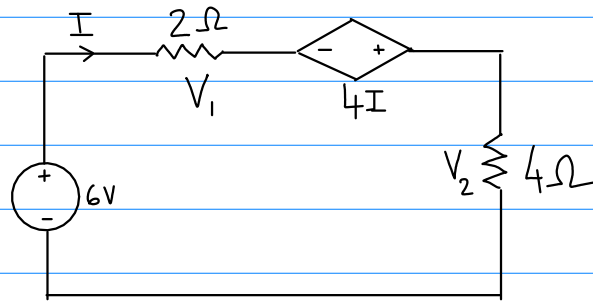
Q2. Apply Kirchhoff's voltage law (KVL) to find the values of current I and voltage drops V_1 and V_2 in the ckt. below.



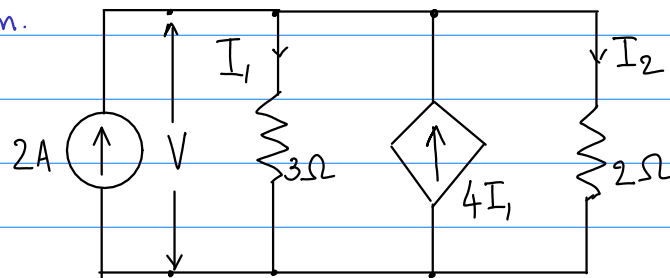
Q3. Apply Kirchhoff's current law (KCL) to find the values of current I_1 and I_2 in the ckt. below. Comment on the direction of current shown.



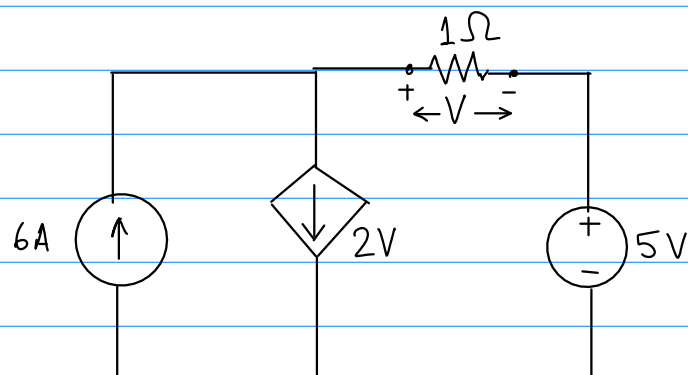
Q4. Apply KCL to find the value of V in the ckt. shown below



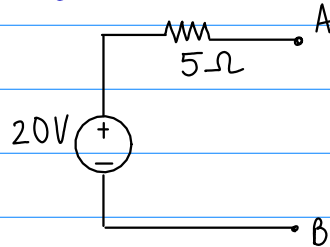
Q5. Convert a given voltage source into equivalent current source.



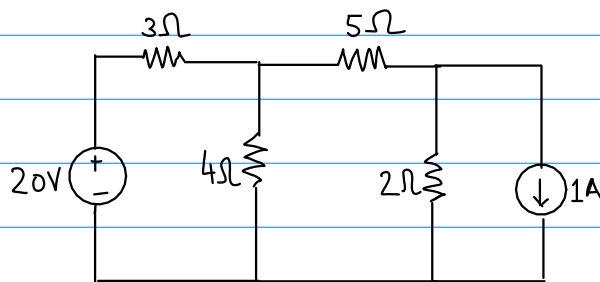Q6. Calculate the direction and magnitude of current flowing through 5Ω resistor. [Hint: You may convert one source to other.]



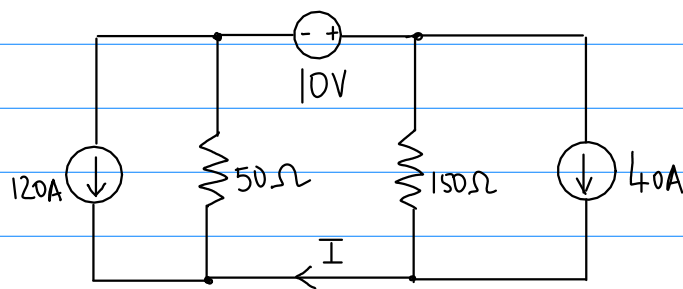Q7. Use superposition theorem to determine the current I shown in the ckt. below.



Q8. Calculate the total power delivered to the 10Ω resistor in the ckt. Use superposition theorem.

