
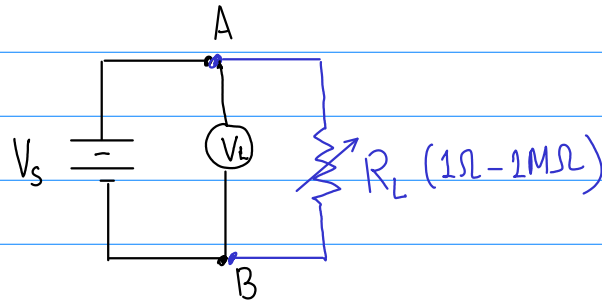


Sources & Circuit Theorems


① Voltage Sources :

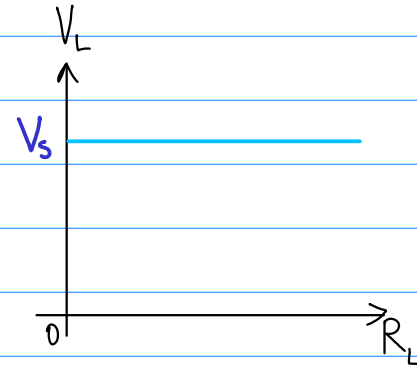


Ideal Voltage source



Real Voltage Source :

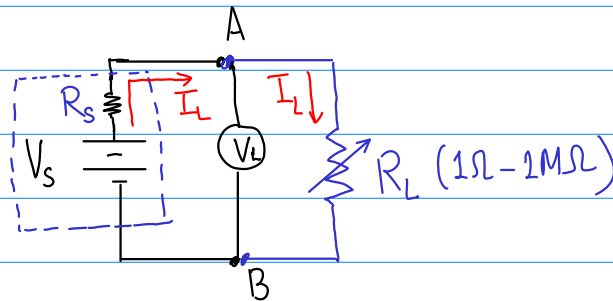

Real Voltage source

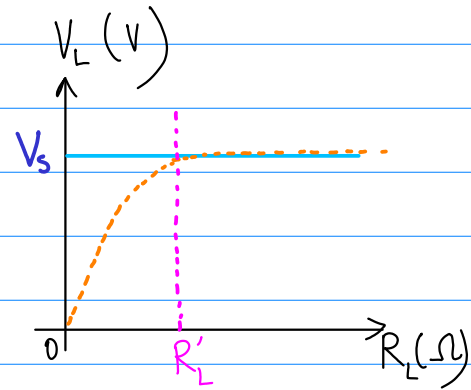

$$\text{Load Current, } I_L = \frac{V_s}{R_s + R_L}$$

$$V_L = I_L R_L = \left(\frac{R_L}{R_s + R_L} \right) V_s$$

$$V_L = \left(\frac{R_L}{R_s + R_L} \right) V_s$$

Load voltage we will measure across the load resistance R_L .

Special Case:

(i)


$$R_s = 0 \Omega \Rightarrow V_L = V_s \Rightarrow \text{Ideal Voltage Source}$$

(ii) $R_s \neq 0$ (finite value) for example $R_s = 100\Omega$

$$V_L = \left(\frac{R_L}{100\Omega + R_L} \right) V_s$$

$$R_L = 10\Omega \Rightarrow V_L = \frac{10}{110} \times V_s$$
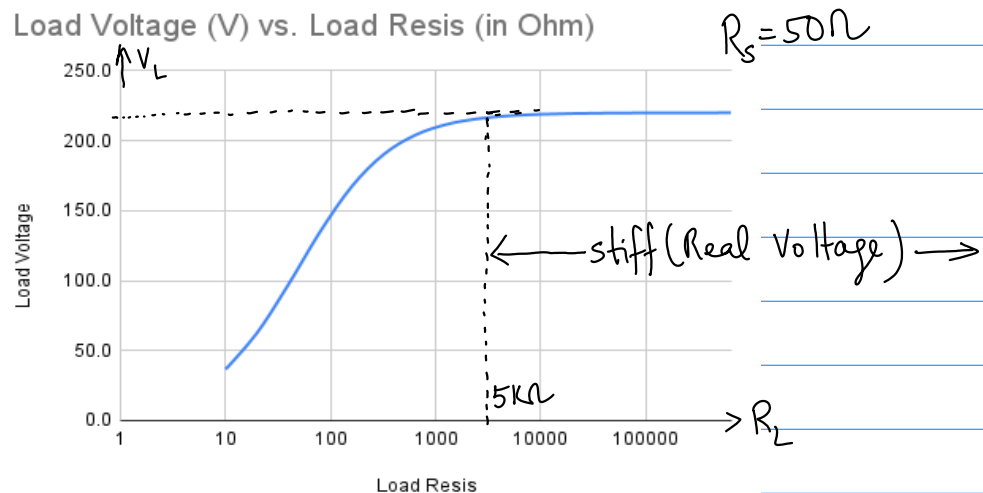
$$R_L = 500\Omega \Rightarrow V_L = \frac{500\Omega}{100\Omega + 500\Omega} \cdot V_s$$






For real (stiff) voltage source,

$$R_L \geq 100 R_s$$

Current Sources :

Ideal Current Source

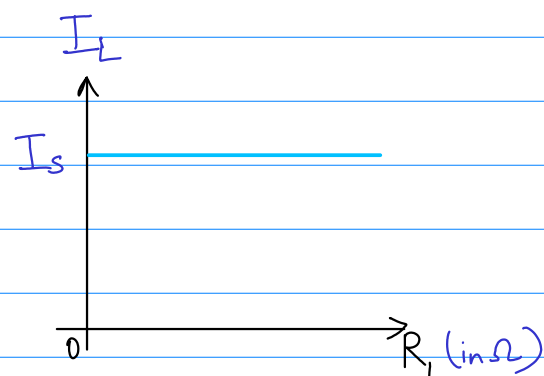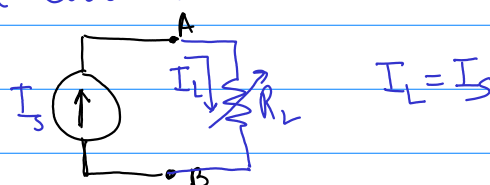


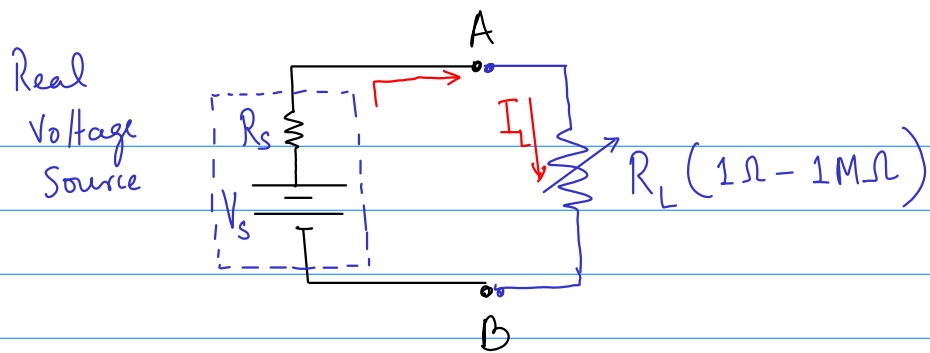

$$I_L = \frac{V_s}{R_s + R_L}$$


$$\Rightarrow I_L = \frac{V_s/R_s}{(R_s + R_L)/R_s}$$
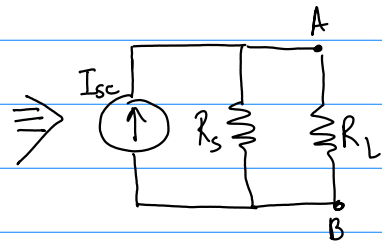
$$I_L = \left(\frac{R_s}{R_s + R_L} \right) I_{sc}$$



Recall;
(School level
concept)



KCL

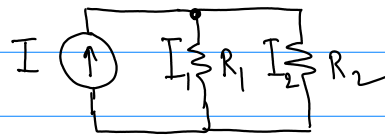

$$I = I_1 + I_2$$


$$I_2 = \left(\frac{R_1}{R_1 + R_2} \right) I$$
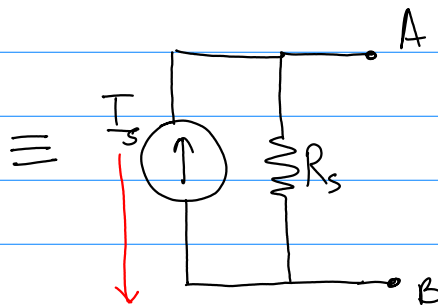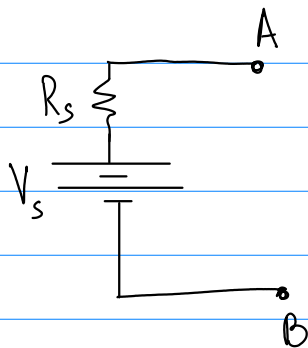
$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I$$



$$I_s = \left(\frac{V_s}{R_s} \right)$$




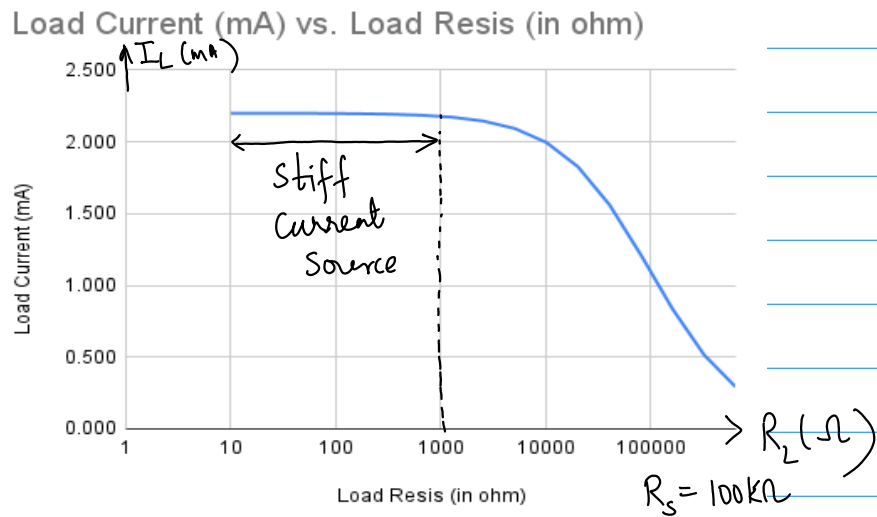

For a real (stiff) current source:

$$R_L \leq \frac{1}{100} R_S$$

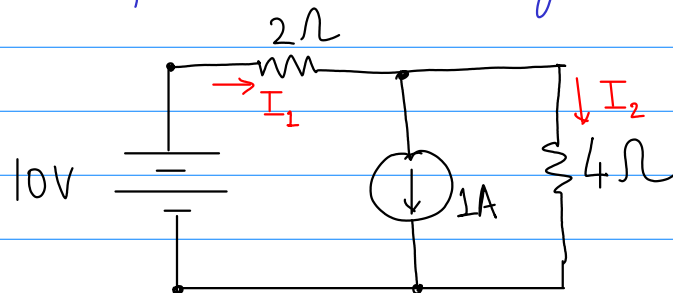Simple example with voltage & current sources:



Use : KCL, KVL to determine I_1 & I_2

Reference : Chapter 1, Malvino & Bates.