
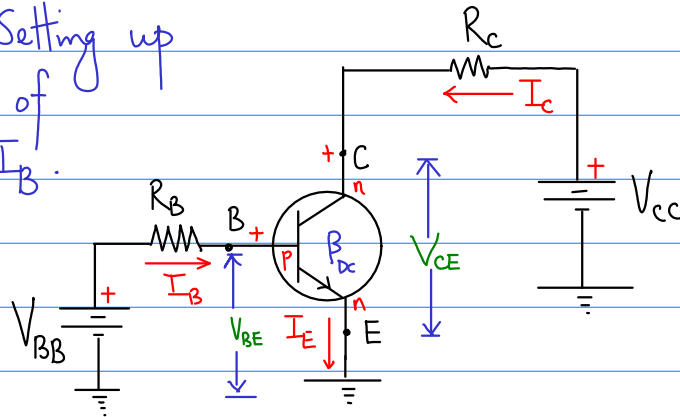


# BJT Biasing Circuits

- Base-Emitter: Forward
- Collector-Base: Reverse

①

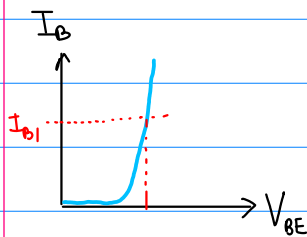Base Bias: Setting up a fixed value of base current  $I_B$ .



$$I_E = I_B + I_C$$

$$I_C = \beta \cdot I_B$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} \quad \dots \text{sets-up the base current.}$$

Typically, for Silicon BJTs,  $V_{BE} = 0.7V$

$$I_B = \frac{V_{BB} - 0.7V}{R_B}$$


Once,  $I_B$  is fixed, then we see the variation of  $I_C$  with  $V_{CE}$ .

For different set of value of  $I_B$ , we have different output characteristic curves

$Q_1: V_{CE1}, I_{C1}$

$Q_2: V_{CE2}, I_{C2}$

$Q_3: V_{CE3}, I_{C3}$

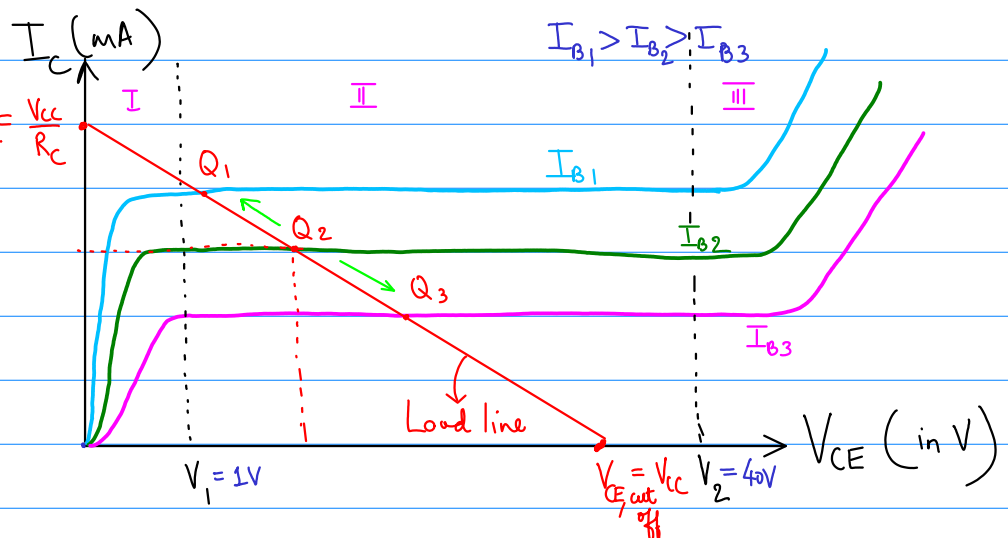


$$I_C = \left(-\frac{1}{R_C}\right) V_{CE} + \frac{V_{CC}}{R_C}$$

... st. line eq<sup>n</sup>. ( $Y = mx + c$ )

Here, the operating point  $Q (V_{CEQ}, I_{CQ})$  depends upon the value of  $I_B$  and the ckt. elements ( $V_{CC}, V_{BB}, R_C, R_B$ ) and the value of  $\beta_{DC}$ .

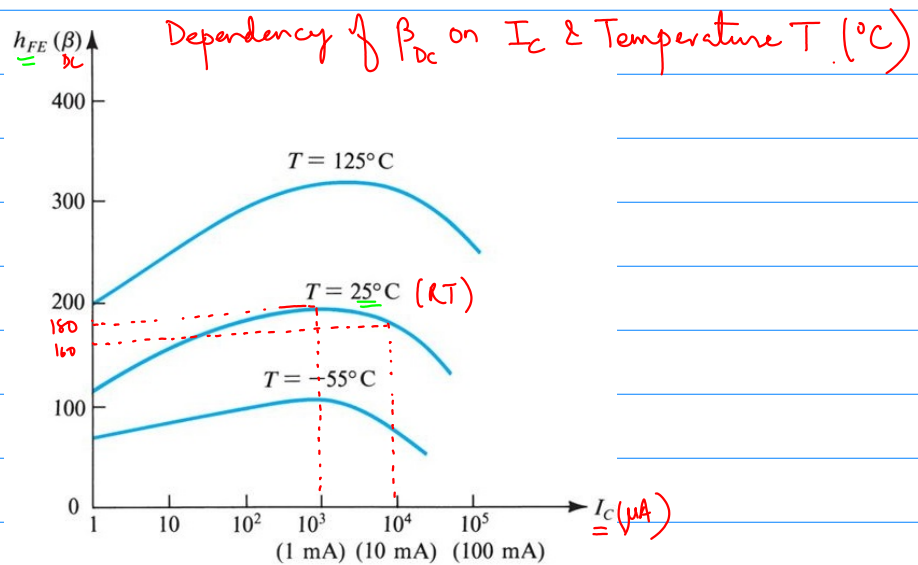Since,  $I_C = \beta_{DC} I_B$   
dependency of  $\beta_{DC}$



- Typically, the base bias ckt. is simple biasing ckt to understand the operation of a BJT, however it is heavily dependent on the value of  $\beta_{DC}$ .
- For amplifier ckt, the active region of the characteristic curve is used. Therefore, we need to immune the ckt. such that it withstand the changes due to  $\beta_{DC}$ . — i.e., design a biasing ckt which is independent of the value of  $\beta_{DC}$ .


Therefore, we need to re-design a bias ckt. to make it  $\beta_{DC}$  independent.

## (2) Emitter - Biasing ckt.

- Removing the base resistor, i.e., connect the  $V_{BB}$  directly to the base terminal.

- Connect a resistor  $R_E$  to the emitter terminal.

- No change in the collector ckt.

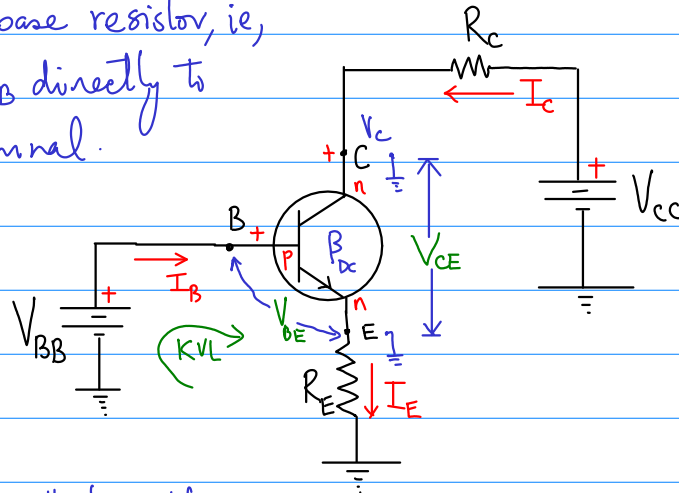

$$V_{BB} = V_{BE} + I_E R_E$$

$$\Rightarrow I_E = \frac{V_{BB} - V_{BE}}{R_E} \quad \left( \text{here, assume } V_{BE} = 0.7V \text{ for Silicon BJTs} \right)$$

$$\text{Since, } I_C \approx I_E$$

$$\left( \text{Since } I_E = I_B + I_C \right. \\ \left. I_B = \mu A; I_C \approx mA \right)$$

$$\Rightarrow V_C = V_{CC} - I_C R_C$$

From this, we can determine,

$$V_{CE} = V_C - V_E \quad \text{where, } V_E = I_E R_E \checkmark$$

$\Rightarrow$  Operating point  $Q (V_{CE}, I_C)$  becomes independent of  $\beta_{DC}$


Note: In previous biasing ckt's (Base-Bias / Emitter-Bias),

We are using two sources, ie,  $V_{BB}$  &  $V_{CC}$ .

Can we design a biasing ckt. with only one source?

Yes.

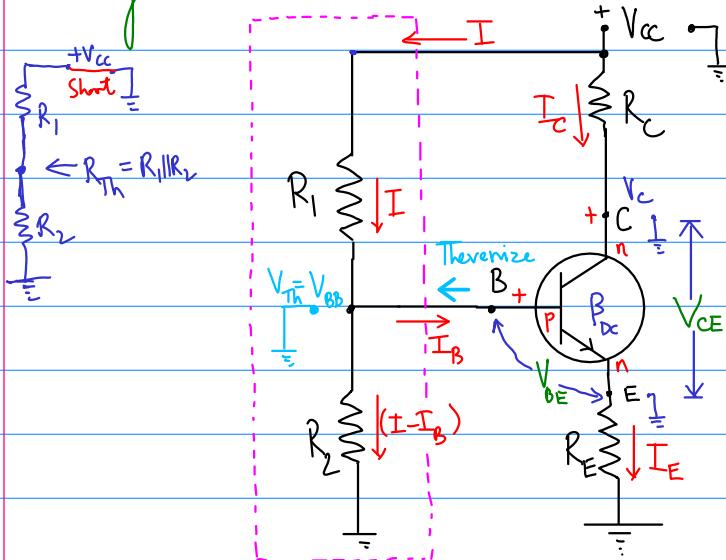
③ Voltage-Divider Bias circuit: Use single dc source  $V_{CC}$  to bias the BJT.



$$V_{Th} = V_{BB} = \frac{R_2}{R_1 + R_2} V_{CC}$$

$$R_{Th} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

Equivalent ckt. will be

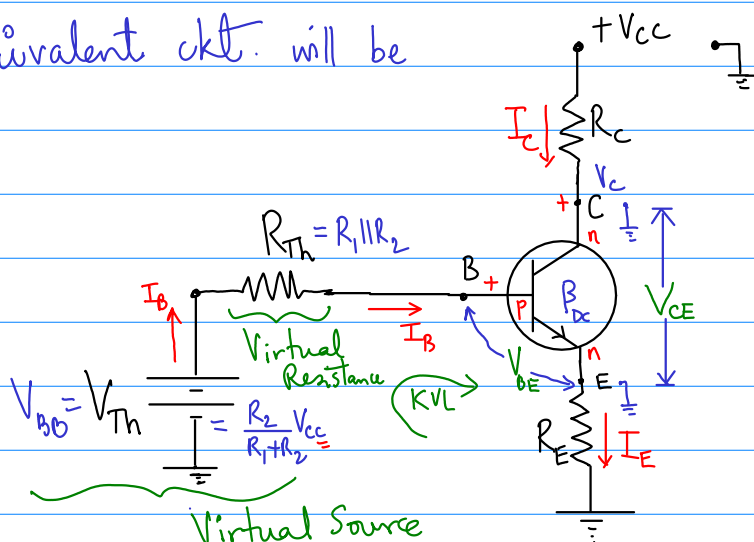

$$I_E = I_B + I_C$$

Reference: Chapter 6 & 7 from Malvinol Bates.