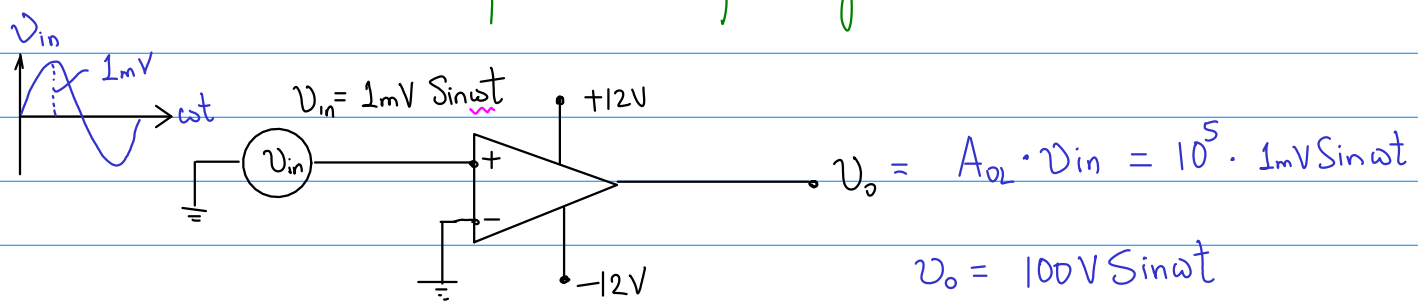


Op-Amp.


Recap: (i) Ideal & Practical Op-Amp. Parameters

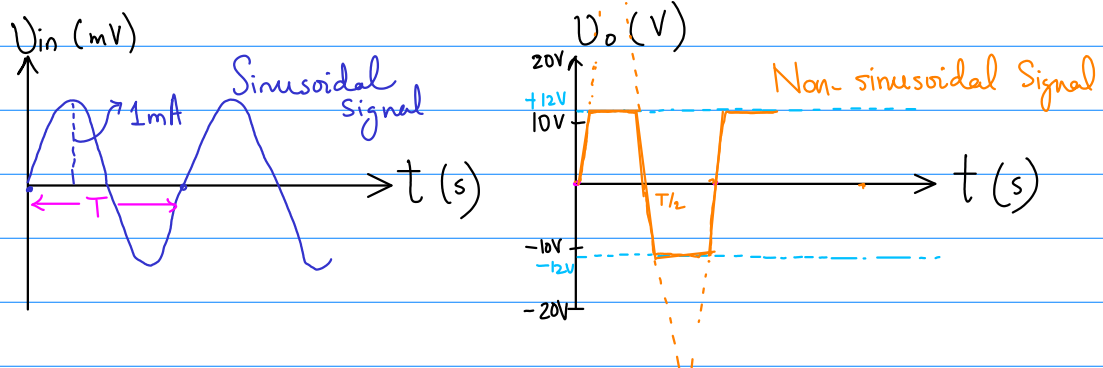(ii) Differential & Common mode Operation

Q: Let's us understand what will happen when we connect the ckt as per the following:



Assuming practical value of $A_{OL} = 10^5$





Open loop configuration leads to distortion in the signal.

Negative Feedback:

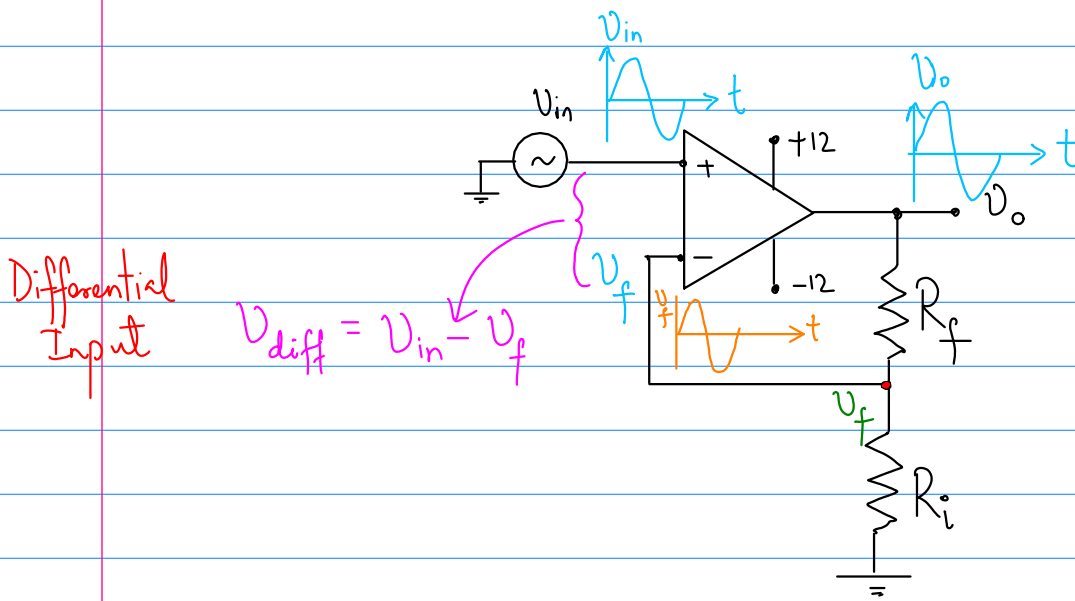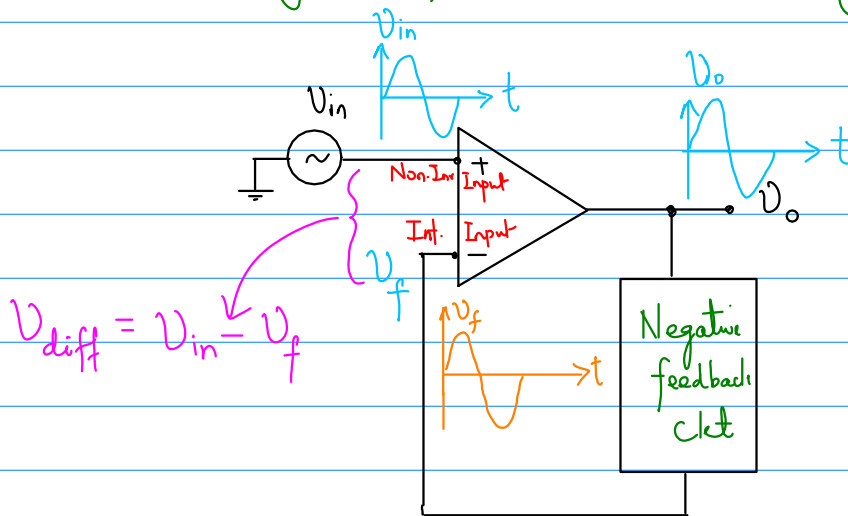1. Tune the gain of the op-amp with help of external ckt. element (Resistor).
— Controlled gain. (Tune the gain as per the need of the circuit.)
2. By tuning the gain, we can restrict the op-amp to operate in linear regime. (Not to go into saturation regime).

Non-inverting Amp. ckt. with negative feedback:



$$V_f = \frac{R_i}{R_i + R_f} V_o$$

↓

$$V_f = B V_o$$

$$\text{where } B = \frac{R_i}{R_i + R_f}$$

Now, with the negative feedback ckt, the op-amp have effective differential input voltage;

$$V_{\text{diff (input)}} = \underbrace{V_{\text{in}}}_{\text{applied to NI input}} - \underbrace{V_f}_{\text{applied to inverting input}}$$

$$V_{\text{diff (input)}} = V_{\text{in}} - B V_o \quad \text{where } B = \frac{R_i}{R_i + R_f}$$

If we have open-loop gain A_{OL}

$$V_o = A_{OL} \cdot V_{\text{diff (input)}} \quad \text{where } A_{OL} = \text{Open-loop gain.}$$

$$\Rightarrow V_o = A_{OL} \cdot (V_{\text{in}} - B V_o)$$

$$\Rightarrow V_o + A_{OL} \cdot B \cdot V_o = A_{OL} \cdot V_{\text{in}}$$

$$\Rightarrow V_o (1 + A_{OL} \cdot B) = A_{OL} \cdot V_{\text{in}}$$

$$\Rightarrow \frac{V_o}{V_{\text{in}}} = \frac{A_{OL}}{1 + A_{OL} \cdot B}$$

$$\Rightarrow A_{\text{CL (NI)}} = \frac{V_o}{V_{\text{in}}} = \frac{A_{OL}}{1 + A_{OL} \cdot B}$$

$$\Rightarrow \boxed{A_{\text{CL (NI)}} = \frac{A_{OL}}{1 + \underbrace{A_{OL} \cdot B}}}$$

As we know; $A_{OL} \sim 10^4 - 10^6$ & $B = \frac{R_i}{R_i + R_f}$

the product $A_{OL} \cdot B$ $\gg 1$

Under this condⁿ:

$$A_{CL(NI)} = \frac{\cancel{A_{OL}}}{\cancel{A_{OL}} \cdot B}$$

$$\Rightarrow A_{CL(NI)} = \frac{1}{B} = \frac{R_i + R_f}{R_i}$$

Eg: $A_{CL(NI)} = 50$
 $\frac{R_f}{R_i} \sim 50$
 $R_f \approx 50 R_i$

\Rightarrow

$$A_{CL(NI)} = 1 + \frac{R_f}{R_i}$$

under the condⁿ
 $A_{OL} \cdot B \gg 1$

Conclusion: • Closed loop gain is independent of the value of the open loop gain.

OR


Closed loop gain is dependant on the external ckt element. (R_i & R_f)

	VOLTAGE GAIN	INPUT Z	OUTPUT Z	BANDWIDTH
1.) Without negative feedback (open loop)	A_{OL} is too high for linear amplifier applications $10^4 - 10^6$	Relatively high (see Table 12-1) $\sim M\Omega$	Relatively low $\sim \text{few } \Omega$	Relatively narrow (because the gain is so high) 1Hz
2.) With negative feedback	A_{CL} is set to desired value by the feedback circuit (R_i & R_f) $A_{CL} = 1 + \frac{R_f}{R_i}$ dependent	Can be increased or reduced to a desired value depending on type of circuit (R_i & R_f) dependent	Can be reduced to a desired value (R_i & R_f) dependent	Significantly wider dependent

Voltage-Follower ckt :


High-impedance Source \longrightarrow Low-impedance load.

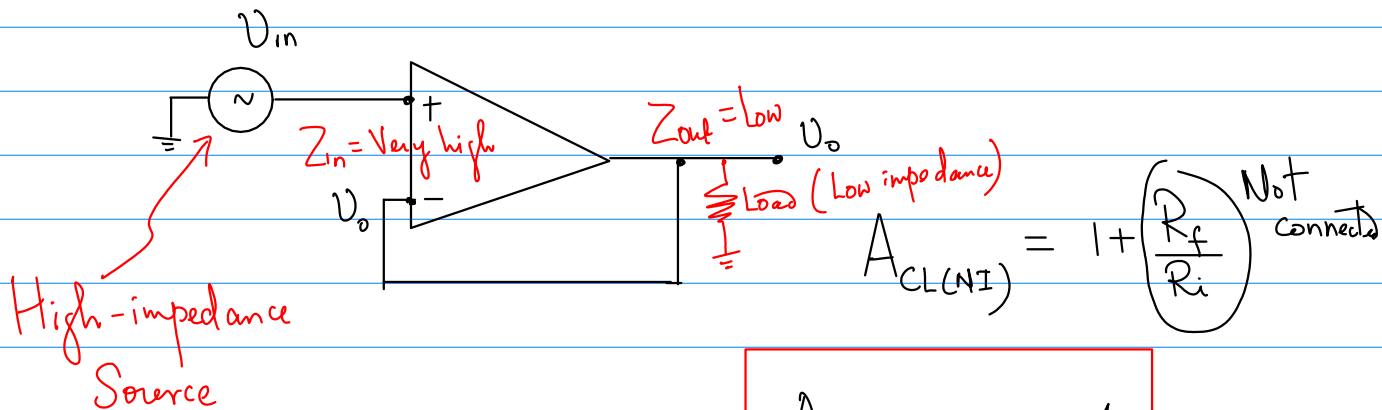\Rightarrow in voltage-follower ckt : $A_V = 1$ (unity)



$$A_{CL(NI)} \approx 1$$

Inverting Closed-Loop Configuration :

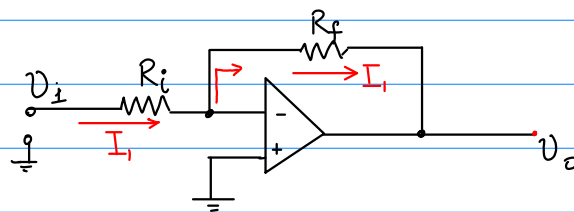

$$V_o = -R_f I_i = -R_f \left(\frac{V_i}{R_i} \right) = \left(-\frac{R_f}{R_i} \right) V_i$$


$$\Rightarrow A_{CL(IN)} = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

$$A_{CL(IN)} = -\frac{R_f}{R_i}$$

Op-Amp : Applications

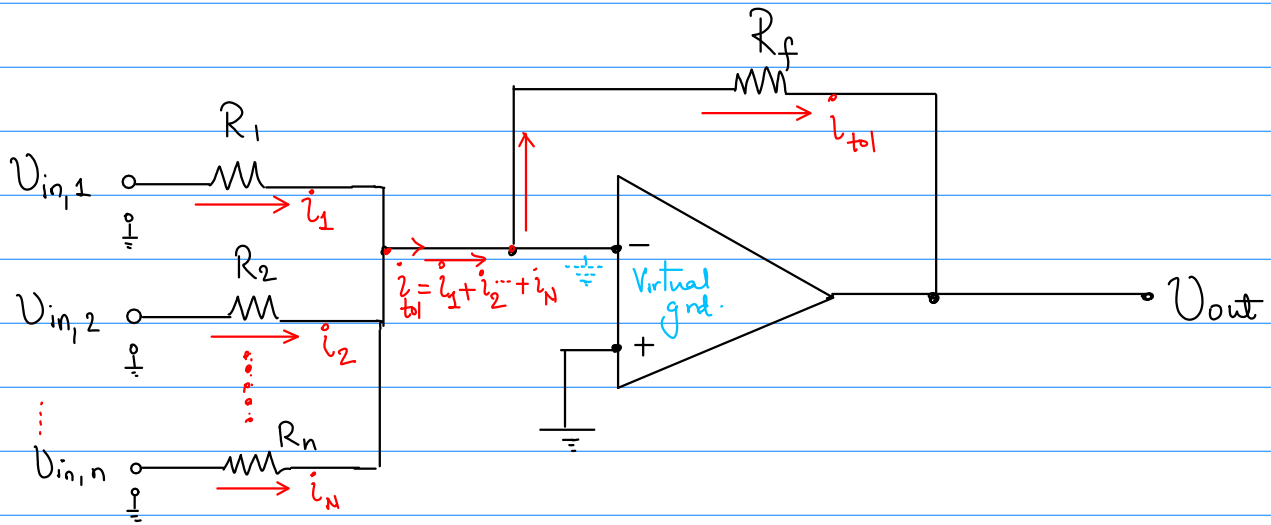1. Summing Amplifiers :

- Make use of inverting op-amp configuration
- It has two or more input ^{voltages} connected to the inverting input terminal.
- Output voltage is proportional to negative of the algebraic sum of its input voltages



Total current through R_f is given as

$$i_{tot} = i_1 + i_2 + \dots + i_N \text{ where, } i_1 = \frac{V_{in,1}}{R_1}$$

$$i_2 = \frac{V_{in,2}}{R_2}$$

here,
$$V_{out} = -R_f i_{tot} = -R_f (i_1 + i_2 + \dots + i_N)$$

$$V_{out} = -R_f \left[\frac{V_{in,1}}{R_1} + \frac{V_{in,2}}{R_2} + \dots + \frac{V_{in,N}}{R_N} \right]$$

$$V_{out} = - \left[\frac{V_{in1}}{R_1} + \frac{V_{in2}}{R_2} + \dots + \frac{V_{inN}}{R_N} \right] R_f$$

finally,

$$V_{out} = - \left[V_{in1} \left(\frac{R_f}{R_1} \right) + V_{in2} \left(\frac{R_f}{R_2} \right) + \dots + V_{inN} \left(\frac{R_f}{R_N} \right) \right]$$

Special Case: $R_1 = R_2 = \dots R_N = R_f = R$

$$V_{out} = - (V_{in1} + V_{in2} + \dots + V_{inN})$$

(i) Generalization: Let we have 'n' number of input voltages
and $R_1 = R_2 = R_3 = \dots = R_f = R$

$$V_{out} = - (V_{in1} + V_{in2} + \dots + V_{in,n})$$

(ii) Summing amplifier with gain greater than unity

$$R_1 = R_2 = R_3 = \dots R_N = R$$

$$R \neq R_f$$

$$V_{out} = - \left(\frac{R_f}{R} \right) [V_{in1} + V_{in2} + \dots + V_{in,n}]$$

factor with which the sum of inputs is multiplied with.

(iii) Lets choose $\frac{R_f}{R} = \frac{1}{n}$ where 'n' is the number of input voltages.

$$V_{out} = -\frac{1}{n} [V_{in,1} + V_{in,2} + \dots + V_{in,n}]$$

V_{out} (ave.) \rightarrow Averaging Operation.

(iv) Scaling Adder :

- Assigning different weights to each of the inputs of the summing amplifier.


$$V_{out} = - \left[V_{in,1} \underbrace{\left(\frac{R_f}{R_1} \right)}_{\text{Weight to } V_{in,1}} + V_{in,2} \underbrace{\left(\frac{R_f}{R_2} \right)}_{\text{Weight to } V_{in,2}} + \dots + V_{in,n} \underbrace{\left(\frac{R_f}{R_n} \right)}_{\text{Weight to } V_{in,n}} \right]$$

② Integrator Circuit :

Input is step voltage: $V_{in}(t) = \begin{cases} 0 & t < 0 \\ V_0 & t > 0 \end{cases}$

$$y(x) = \begin{cases} 0 & x < 0 \\ c & x > 0 \end{cases}$$
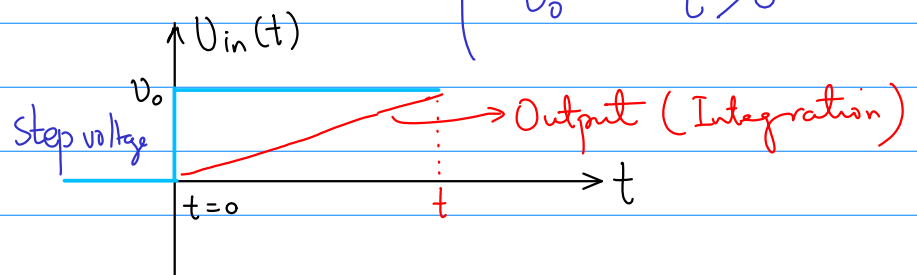
$$\int y(x) dx = \begin{cases} cx & x > 0 \end{cases}$$




Integration of input voltage

$$\int_{-\infty}^{\infty} V_{in}(t) dt = \underbrace{\int_{-\infty}^0 V_{in}(t) dt}_0 + \underbrace{\int_0^{\infty} V_{in}(t) dt}_{\int_0^t V_o dt} = V_o t$$

Integration of ^{constant} input voltage ^(w.r.t 't') is a linear function of 't'.

Ideal Integrator ckt :

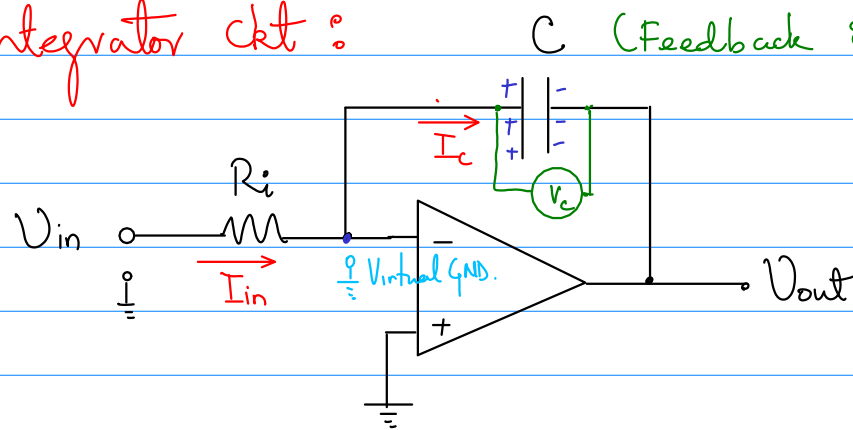

$$I_{in} = \frac{V_{in}}{R_i} = \text{Constant}$$

$$I_c = I_{in} = \text{Constant}$$

We know that the charge on the capacitor at any time 't' is given as

$$Q = I_c t$$

$$V_c = \frac{Q}{C} = \left(\frac{I_c}{C} \right) t$$

$$V_c = \left(\frac{I_c}{C} \right) t$$

$$\left\{ Y = Mx + C \right\}$$

Now,
$$V_{out} = -V_c = -\left(\frac{I_c}{C}\right) t$$

$$V_{out} = -\left(\frac{V_{in}}{R_i C}\right) t$$

$$\left\{ I_c = I_{in} = \frac{V_{in}}{R_i} \right.$$

$$V_{out} = -\frac{1}{R_i C} V_{in} t$$

$$Y = Mx$$

$$M = -\frac{V_{in}}{R_i C}$$

$$x = t$$

$$Y = V_{out}$$

