


## p-n Diode : Applications

Since p-n diodes are unidirectional element, meaning it has ability to conduct currents in one direction and block in other direction.

- Diodes are used in circuits called rectifiers that convert ac voltage into dc voltage.
- Rectifier ckt. are found in all dc power supply that operates from an ac source.

### A) Rectifier Operation:

#### (i) Half-Wave Rectifier:

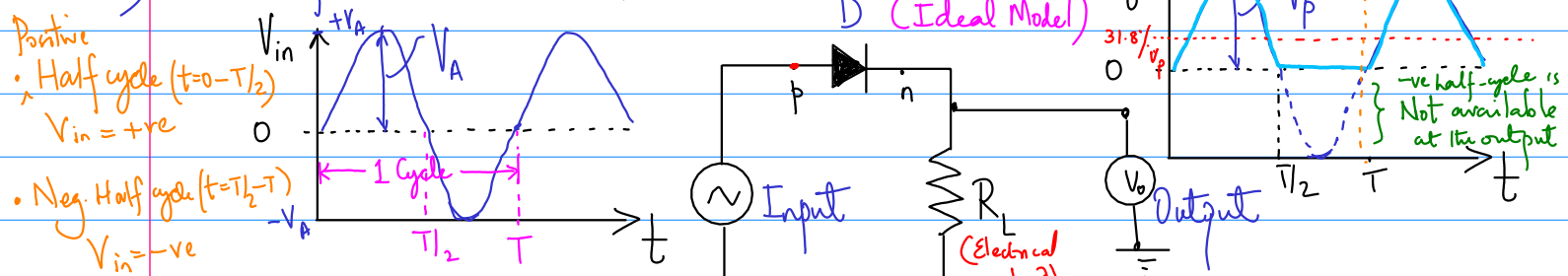

The output is observed on the scope/simulator

What would be voltage across  $R_L$  when a DC voltmeter is connected across it?

- It measures the average value of the output signal.

Mathematically, it is the area under the output signal over a full (one) cycle and then divided by  $2\pi$ , the number of radians in a full cycle.

$$V_{ave.} = \frac{1}{2\pi} \int_{t=0}^{t=T/2} V_p \sin \omega t \, d(\omega t) + \frac{1}{2\pi} \int_{t=T/2}^{t=T} V_p \sin \omega t \, d(\omega t)$$


+ve half-cycle                      -ve half-cycle = 0

$$\Rightarrow \boxed{V_{ave.} = \frac{V_p}{\pi}} \approx 31.8\% \text{ of } V_p$$

In order to incorporate the effect of barrier potential in p-n diode on half-wave rectifier,

We use "Modified Ideal Diode Model":



For practical p-n diode:

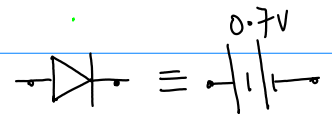

$$V_p = V_{in} - 0.7V$$

$$\boxed{V_{ave} = \frac{V_p}{\pi} = \frac{(V_{in} - 0.7V)}{\pi}}$$

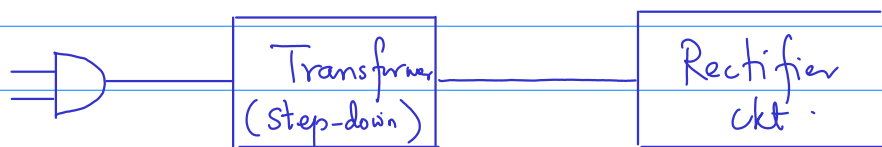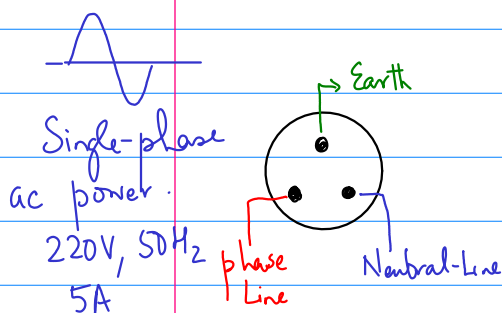
$V_{in}$  = Amplitude of the input signal.



In practice, the rectifier ckt. is connected with the step-down transformer at the input terminal.

Advantages:

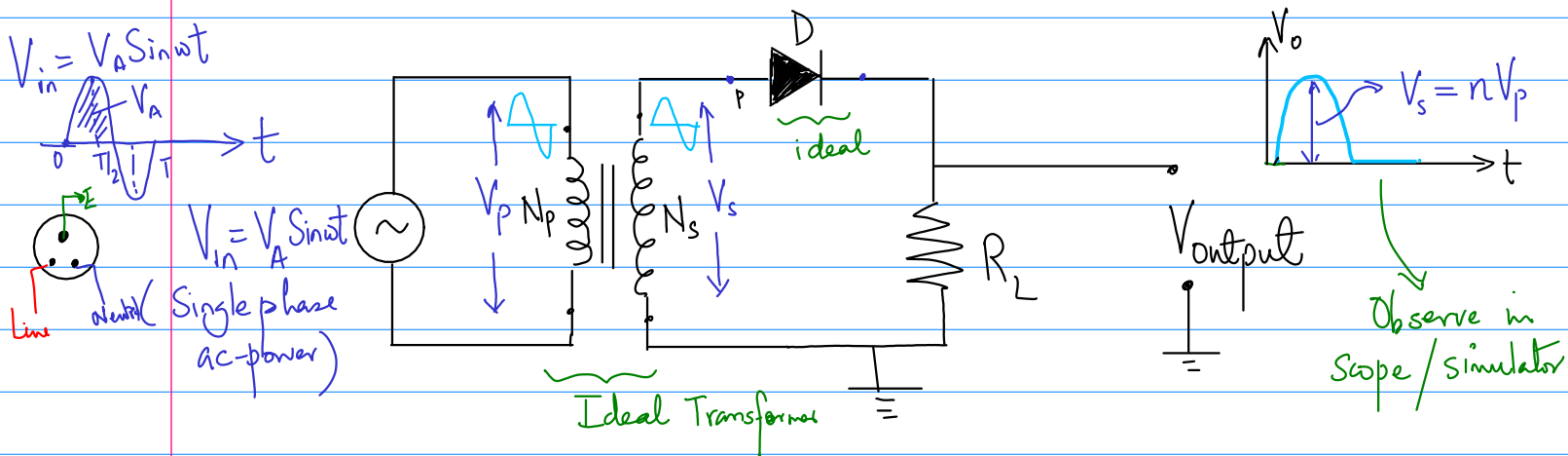- i) Allows the source voltage to step-down
- ii) Prevents rectifier ckt. with any electrical hazard.



In transformer, we define

Turn ratio;  $n = \frac{N_s}{N_p}$  (Number of turns in the secondary coil)  
(# turns in the primary coil)

$n > 1$  : step-up transformer

$n < 1$  : step-down transformer

$$V_s = n V_p$$

If you connect dc voltmeter across the  $R_L$

$$V_{ave} = \frac{V_s}{\pi} = \frac{n V_p}{\pi} = \frac{n V_{in}}{\pi}$$

## Transformer Coupled Rectifier

$N =$  turn-ratio of the transformer.

$V_{in}$  = Amplitude of the input voltage.

For practical divides:

## Tran. Couples

$V_{in}$  = amplitude of the input voltage.

## Full-Wave Rectifier:

