
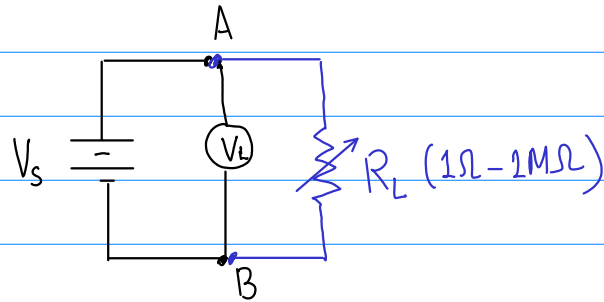


Sources & Circuit Theorems


① Voltage Sources :

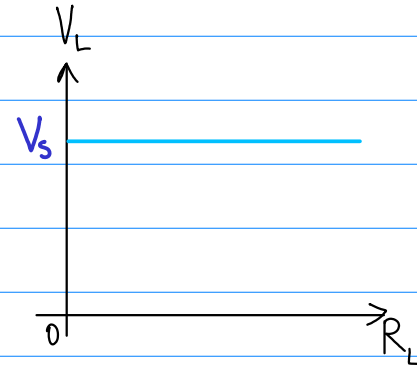


Ideal Voltage source



Real Voltage Source :

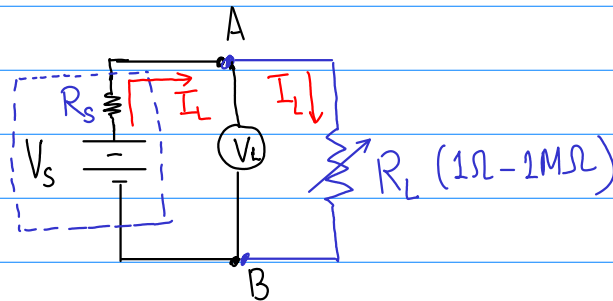

Real Voltage source

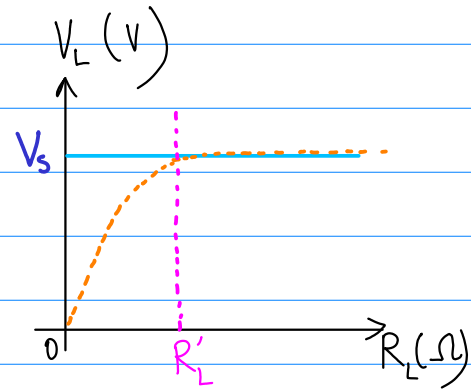

$$\text{Load Current, } I_L = \frac{V_s}{R_s + R_L}$$

$$V_L = I_L R_L = \left(\frac{R_L}{R_s + R_L} \right) V_s$$

$$V_L = \left(\frac{R_L}{R_s + R_L} \right) V_s$$

Load voltage we will measure across the load resistance R_L .

Special Case:

(i)

$$R_s = 0 \Omega \Rightarrow V_L = V_s \Rightarrow \text{Ideal Voltage Source}$$


(ii) $R_s \neq 0$ (finite value) for example $R_s = 100\Omega$

$$V_L = \left(\frac{R_L}{100\Omega + R_L} \right) V_s$$

$$R_L = 10\Omega \Rightarrow V_L = \frac{10}{110} \times V_s$$

$$R_L = 500\Omega \Rightarrow V_L = \frac{500\Omega}{100\Omega + 500\Omega} \cdot V_s$$

Load Voltage (V) vs. Load Resis (in Ohm)


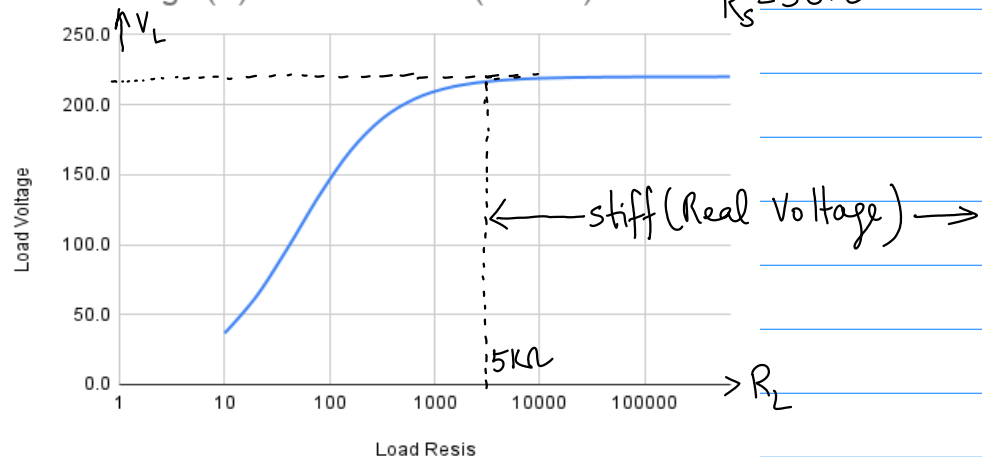



For real (stiff) voltage source,

$$R_L \geq 100 R_s$$

Current Sources :

Ideal Current Source

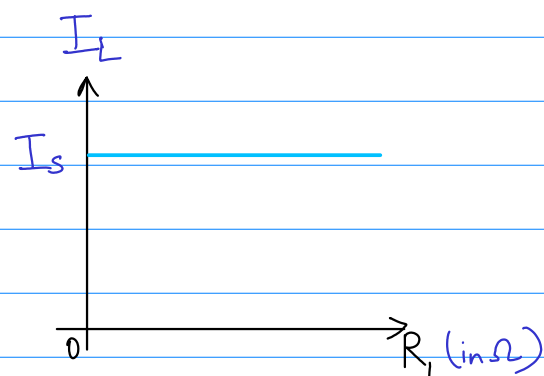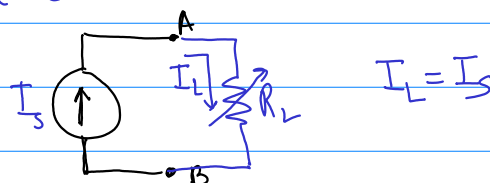


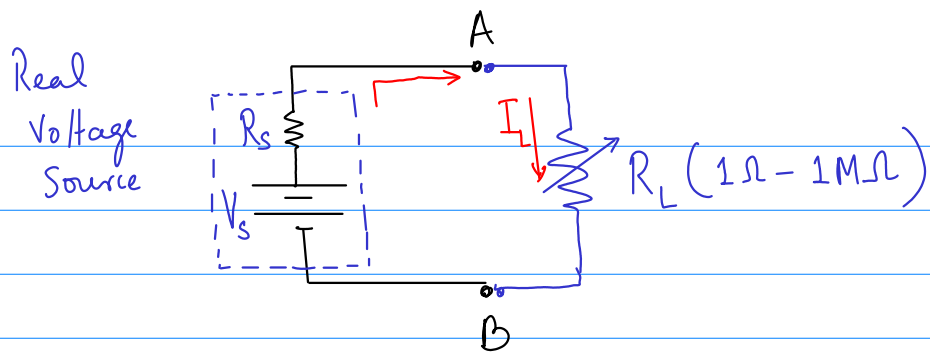

$$I_L = \frac{V_s}{R_s + R_L}$$

$$\Rightarrow I_L = \frac{V_s/R_s}{(R_s + R_L)/R_s}$$
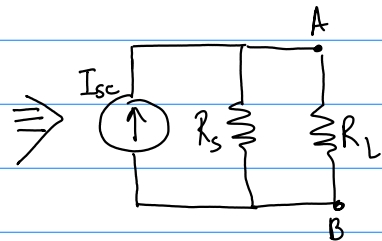
$$I_L = \left(\frac{R_s}{R_s + R_L} \right) I_{sc}$$



Recall;
(School level
concept)



KCL




$$I = I_1 + I_2$$

$$I_2 = \left(\frac{R_1}{R_1 + R_2} \right) I$$
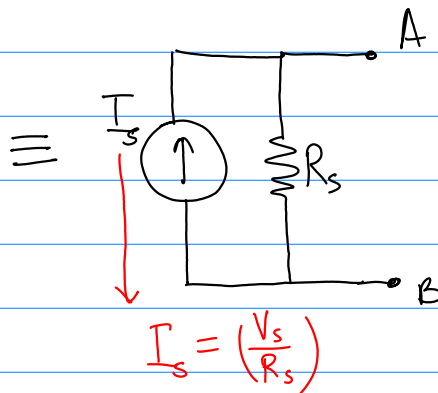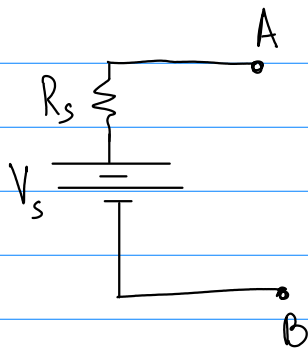
$$I_1 = \left(\frac{R_2}{R_1 + R_2} \right) I$$




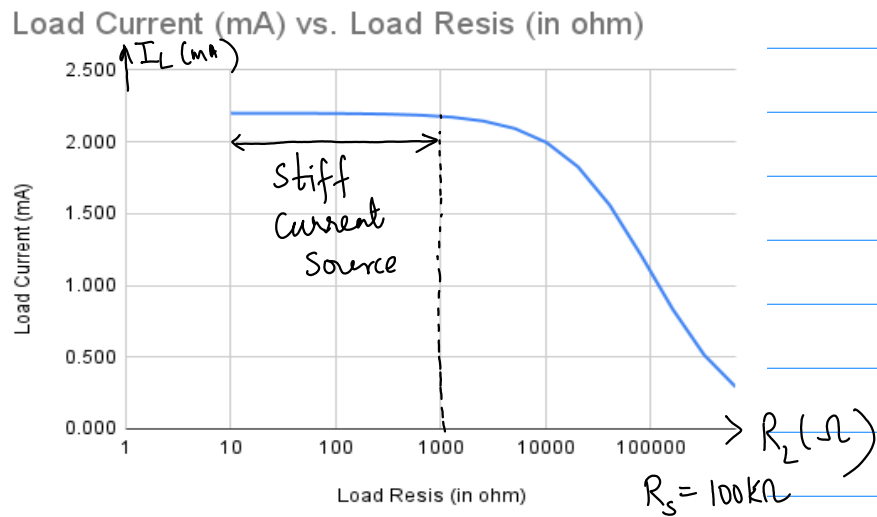

For a real (stiff) current source:

$$R_L \leq \frac{1}{100} R_S$$

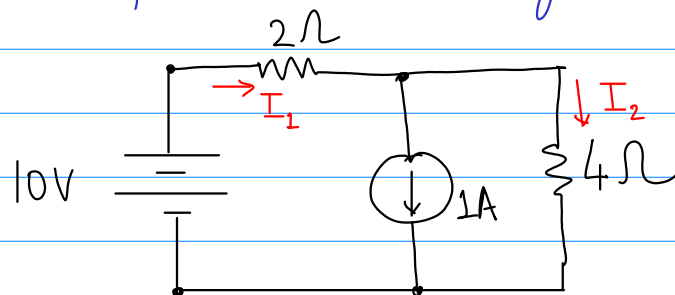
Simple example with voltage & current sources:



Use : KCL, KVL to determine I_1 & I_2

Circuit Theorems

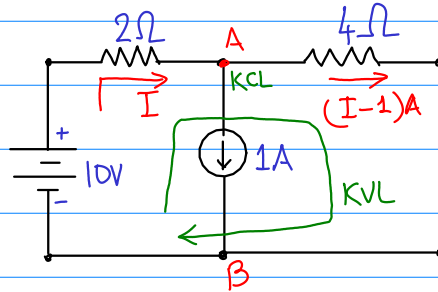Recap: A simple ckt. with both voltage and current sources.



KCL, KVL

$$10V = 2I + 4(I-1)$$

Solve to get I .

$$I = \frac{7}{3}A ; \frac{4}{3}A$$

Suppose we have more number of sources in the ckt., and we would like to determine the effect of all the sources to a given ckt. element (eg. resistor).


Superposition Theorem: The voltage across (or the current through) an element in a given linear ckt. is the algebraic sum of the voltages across (or current through) that element due to each sources acting alone.

⇒ This means that while determining voltage (or current) due to ^{one source,} we need to zero the other sources.

To make the sources zero, we need

Open : all ^{other} current sources


Short : all ^{other} voltage sources

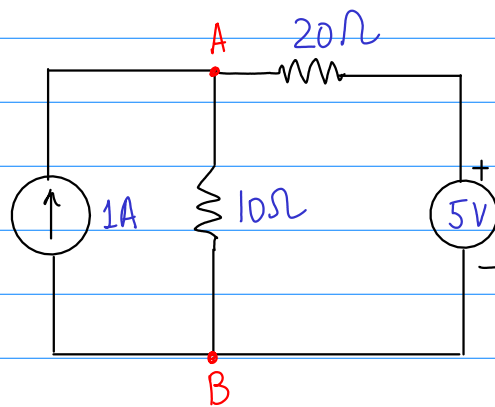

Use superposition theorem
to determine voltage
across AB (ie, V_{AB})

(i) Effect of the voltage source acting alone.

⇒ we need to zero the current source

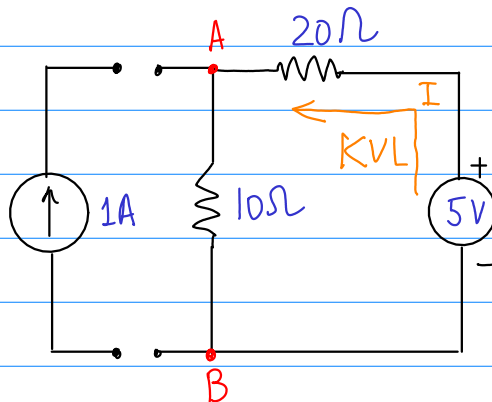



$$I = \frac{5V}{20\Omega + 10\Omega} = \frac{1}{6} A$$

$$V_{AB1} = \frac{10}{6} = \frac{5}{3} V$$

$$V_{AB1} = \frac{5}{3} V$$

(ii) effect of current source acting alone.

⇒ we need to zero the voltage source.

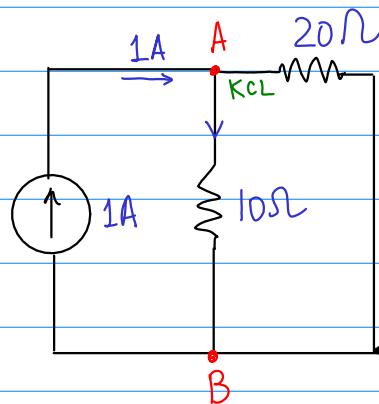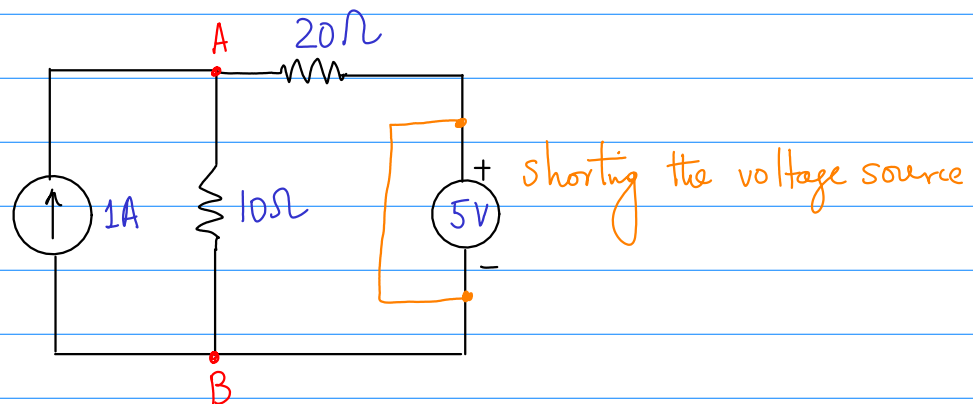

⇒ Current divider ckt.

Current through 10Ω resistor

$$= \left(\frac{20\Omega}{10\Omega + 20\Omega} \right) 1A$$

$$= \frac{2}{3} A$$

$$V_{AB(2)} = \frac{2}{3} A \cdot 10\Omega$$


$$= \frac{20}{3} V$$

Therefore, according to superposition theorem:

$$V_{AB} = V_{AB(1)} + V_{AB(2)} = \frac{5}{3} V + \frac{20}{3} V$$

$$= \frac{25}{3} V$$

$$V_{AB} = \frac{25}{3} V$$

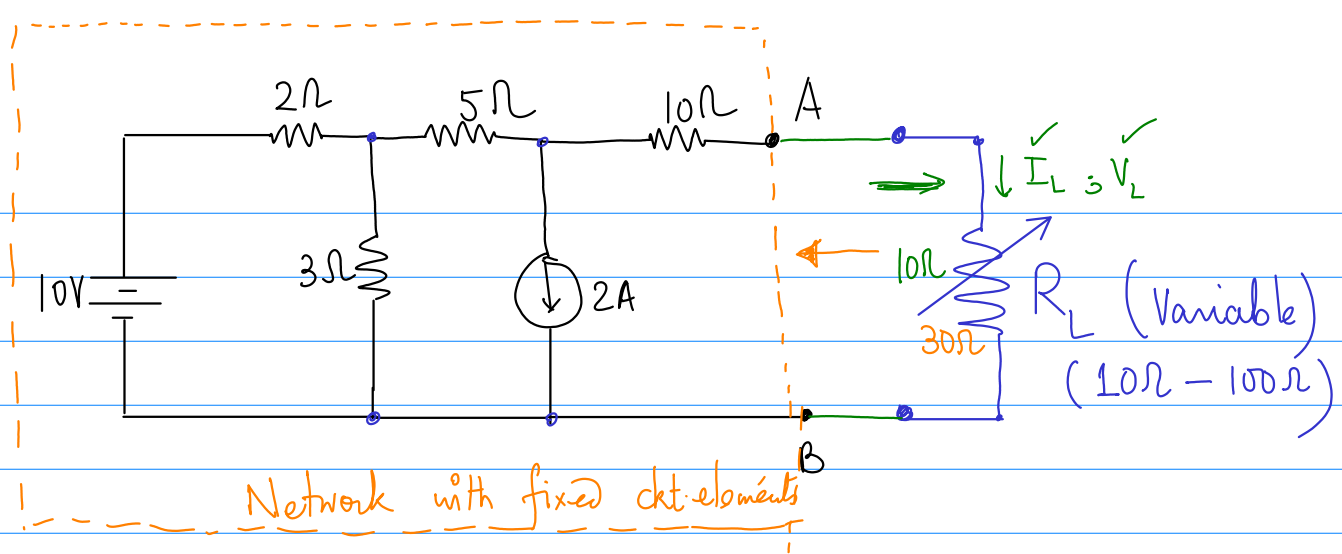

The value of load current (or load voltage) for a given network with fixed elements depends on the value of load resistance.

That is, each time value of R_L changes, you need re-calculate all the current/voltage to determine the value I_L & V_L .



To overcome this difficulty of ckt. analysis, we have a ckt. theorem.

Ckt. theorem given by a French Engineer
Leon Charles Thevenin.

Thevenin's Theorem :

A linear network with fixed values of ckt. elements

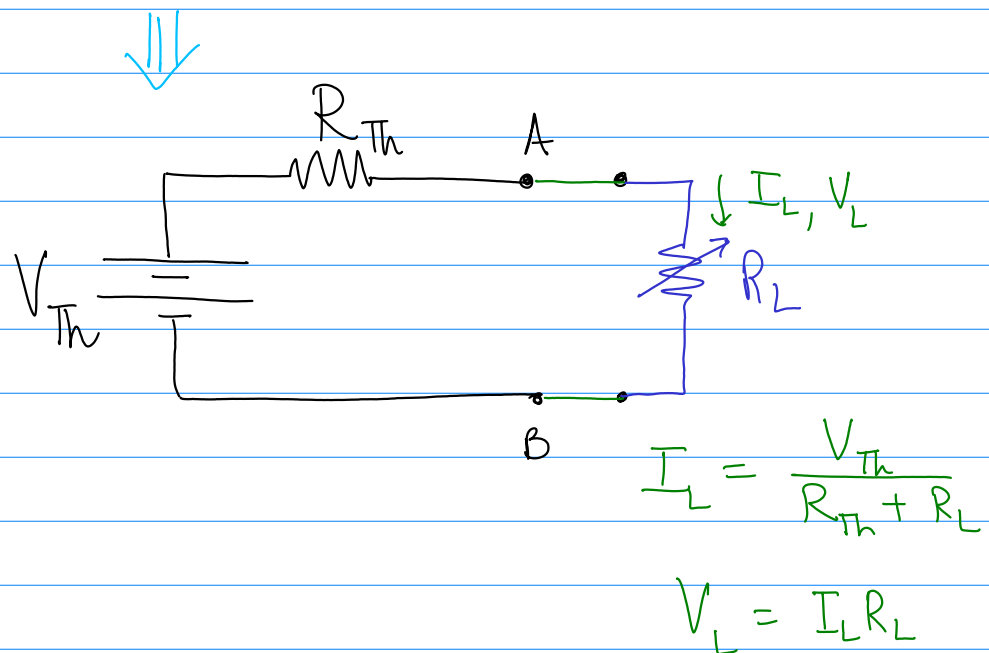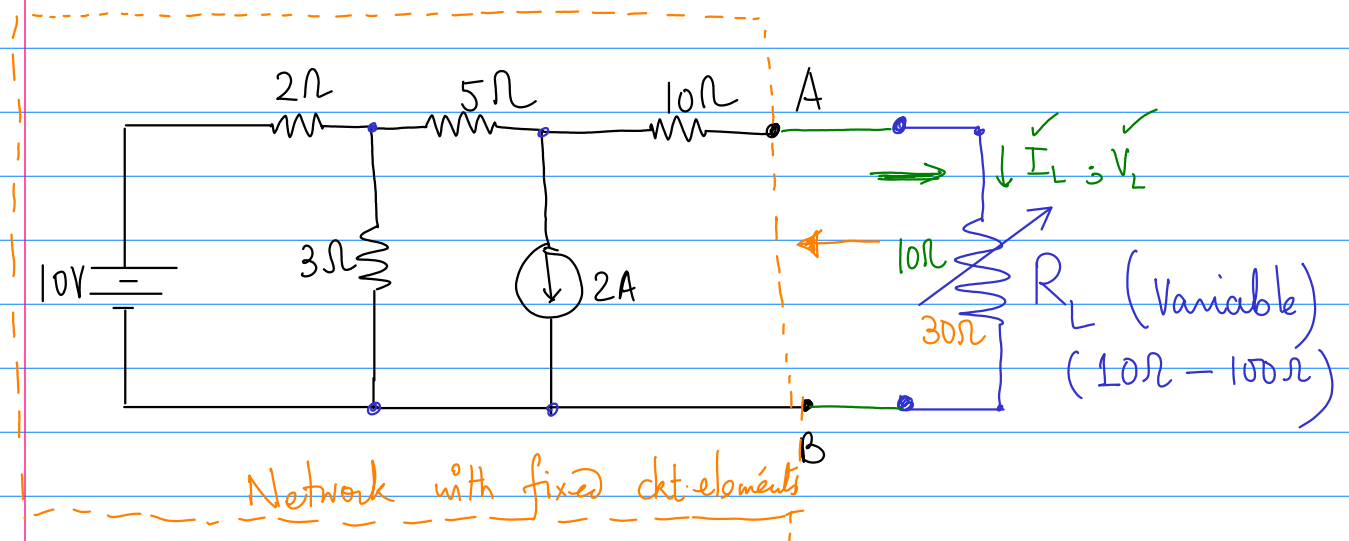can be replaced by an equivalent network consisting of a single voltage source and a series resistance.



Ques: How do we determine V_{Th} & R_{Th} for a given network.

V_{Th} = Open ckt. voltage across the load terminals (here AB)

⇒ Remove the load across AB & measure the open ckt. V_{AB} (open ckt.)

R_{Th} = Equivalent resistance of the given network across the load terminal (here AB) making all the sources zero.