
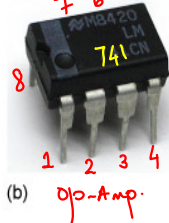




Operational Amplifiers (Op-Amps)

- To perform mathematical operations
(Additions, Subtraction, Integration, Differentiation)

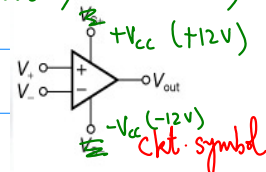1964, First integrated circuit Op-Amp was developed by Fairchild Semiconductor.




ckt. symbol w/o bias :

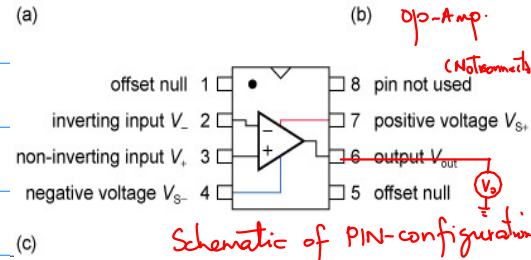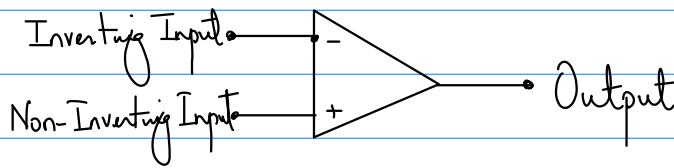


Characteristics of Op-Amps.

	<u>Characteristics</u>	<u>Ideal</u>	<u>Practical</u>
1.	Open-loop Voltage Gain, A_{OL}	∞	$\sim 10^4 - 10^6$
2.	Input Impedance, Z_{in}	∞	$\sim M\Omega (10^6\Omega)$
3.	Output Impedance, Z_{out}	0	$\sim 100\Omega$
4.	Bandwidth	∞	$\sim 1\text{ Hz}$
5.	Common-mode Rejection Ratio (CMRR)	∞	$\sim 80-120\text{ dB}$
6.	Slew Rate	∞	$\sim 1\text{ V}/\mu\text{sec}$

Ideal Representation of Op-Amp.

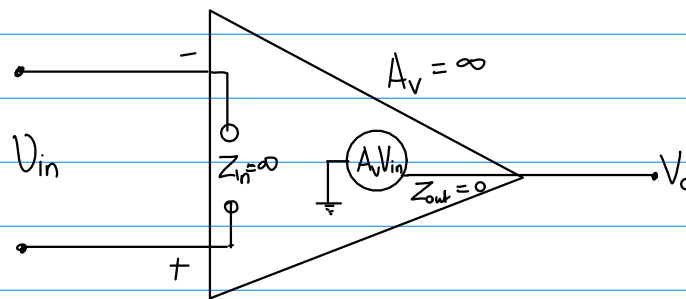


Practical Representation of Op-Amp.

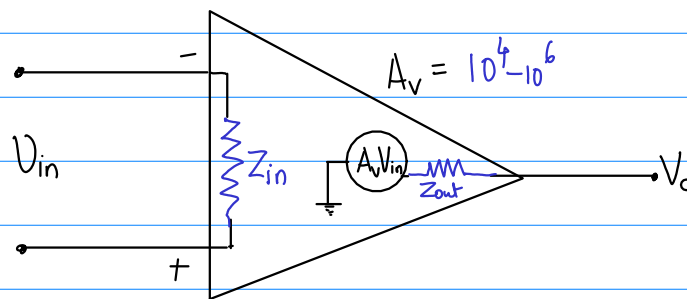

Op-Amp Input Modes :

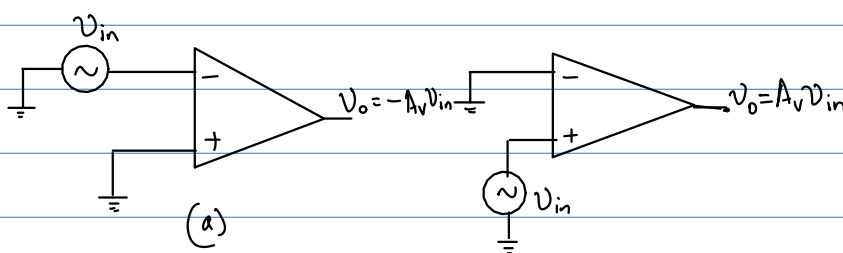
1) Differential Mode :

- One signal is applied to an input and the other input is grounded.



Single-ended differential mode.

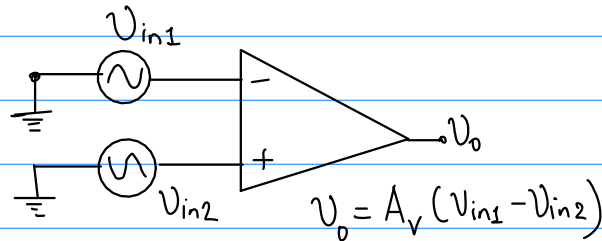- Two opposite-polarity signals are applied to the inputs.




Double-ended differential mode.

V_{in1} and V_{in2} has to be 180° out of phase.

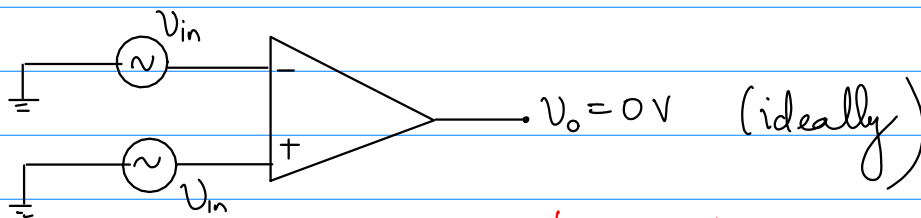2) Common Mode :

In this mode, two signal voltages of same phase, frequency and amplitude are applied to the two inputs.



This action is known as Common-Mode rejection.

Rejection of unwanted signal (noise) appearing commonly to both the inputs of the op-amp.

Example :

Differential Mode : $V_{in} = V_{in1} - V_{in2}$

Common Mode : $V_{in} = \frac{V_{in1} + V_{in2}}{2}$

Differential Mode : Gain (A_v) is very high (ideally ∞ , $10^4 - 10^6$)

Common Mode : Gain (A_v) is very low (ideally 0, 10^{-3} to 10^{-5})

$$A_{v,DM} \sim 10^4 - 10^6$$

$$A_{v,CM} \sim 10^{-3} - 10^{-5}$$

$$V_{in1} = 5V$$

$$V_{in2} = 5V + 0.001 \sin \omega t$$

$$V_{in,DM} = V_{in1} - V_{in2} = -0.001 \sin \omega t$$

$$V_{in,CM} = \frac{V_{in1} + V_{in2}}{2} = 5V + 0.0005 \sin \omega t$$

$$V_{o,DM} = A_{v,DM} \cdot V_{in,DM} = 10^5 \cdot (-0.001 \sin \omega t)$$

$$V_{o,DM} = -10^2 \sin \omega t = -100V \sin \omega t$$

$$\begin{aligned} V_{o,CM} &= A_{v,CM} \cdot V_{in,CM} = 10^{-5} (5V + 0.0005 \sin \omega t) \\ &= 5 \times 10^{-5} V + 10^{-9} \sin \omega t \end{aligned}$$

\Rightarrow Output voltage corresponding to DM input is very high whereas it is negligible for CM input.

The performance of Op-Amps is measured on the basis of its rejection of signal in common mode.

We define a parameter called 'Common-mode Rejection Ratio'.

$$\text{ie } CMRR = \frac{A_{OL}}{A_{CM}} \sim \frac{10^5}{10^{-3}} \sim 10^8$$

Higher the CMRR, better is the Op-Amp.

$$CMRR (\text{in dB}) = 20 \log_{10} \left(\frac{A_{OL}}{A_{CM}} \right)$$

$$\text{if } \frac{A_{OL}}{A_{CM}} = 10^8, \text{ then } CMRR (\text{in dB}) = 160 \text{ dB}$$

Maximum Output Voltage Swing ($V_{O(p-p)}$):

In the above example, we have seen that for differential input voltage,

$$V_{O,DM} = -100V \sin \omega t.$$

However, we never get $\pm 100V$ in one cycle of oscillation.

That is, the output voltage is clipped above $\pm V_{CC}$.

