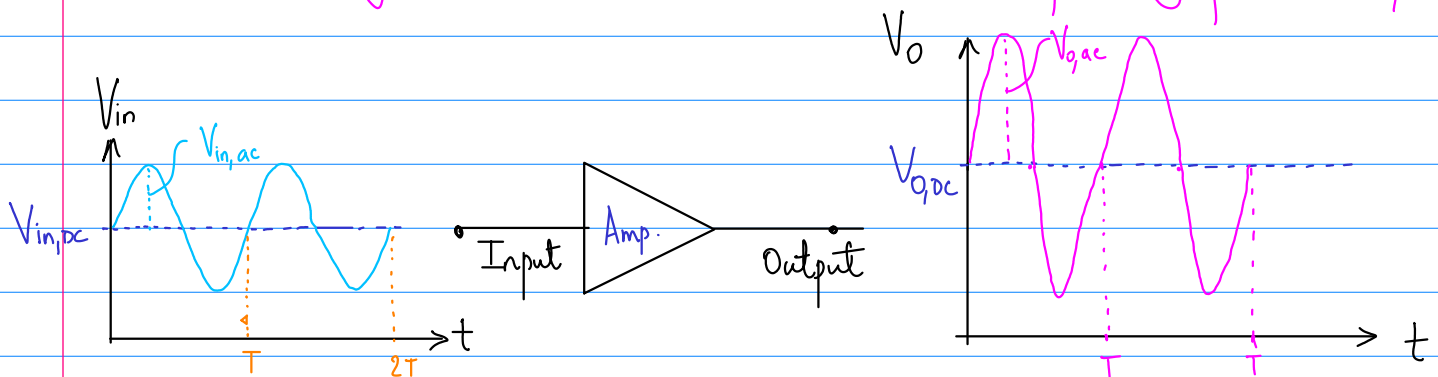


BJT Amplifiers

(Small Signal Amplifiers)

DC Biasing: It establishes stable dc operating point (Q-point)



$$V_{Q,ac} \gg V_{in,ac} \text{ whereas } T_{out} = T_{in}$$

Small-Signal Amplifiers:

- Variation about the set Q-point is relatively small.

(Case i) Q-point is set nearly in the middle of the load-line.

For the given biased BJT ckt.


$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{3.7V - 0.7V}{10k\Omega}$$

$$I_B = 0.3mA = 300\mu A$$

$$I_C = \beta_{DC} I_B = 100 \times 300\mu A = 30mA$$


$$V_{CE} = V_{CC} - I_C R_C = 10V - 30mA \times 220\Omega = 3.4V$$
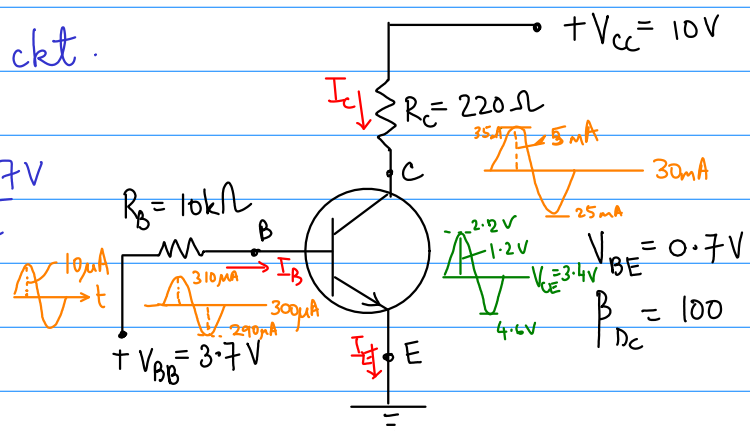
$$Q\text{-point} : V_{CE}, I_C \Rightarrow 3.4V, 30mA$$



$$I_{C,sat} = \frac{V_{CC}}{R_C} = \frac{10V}{220\Omega} = 45.5mA$$

$$V_{CE, cut-off} = V_{CC} = 10V$$

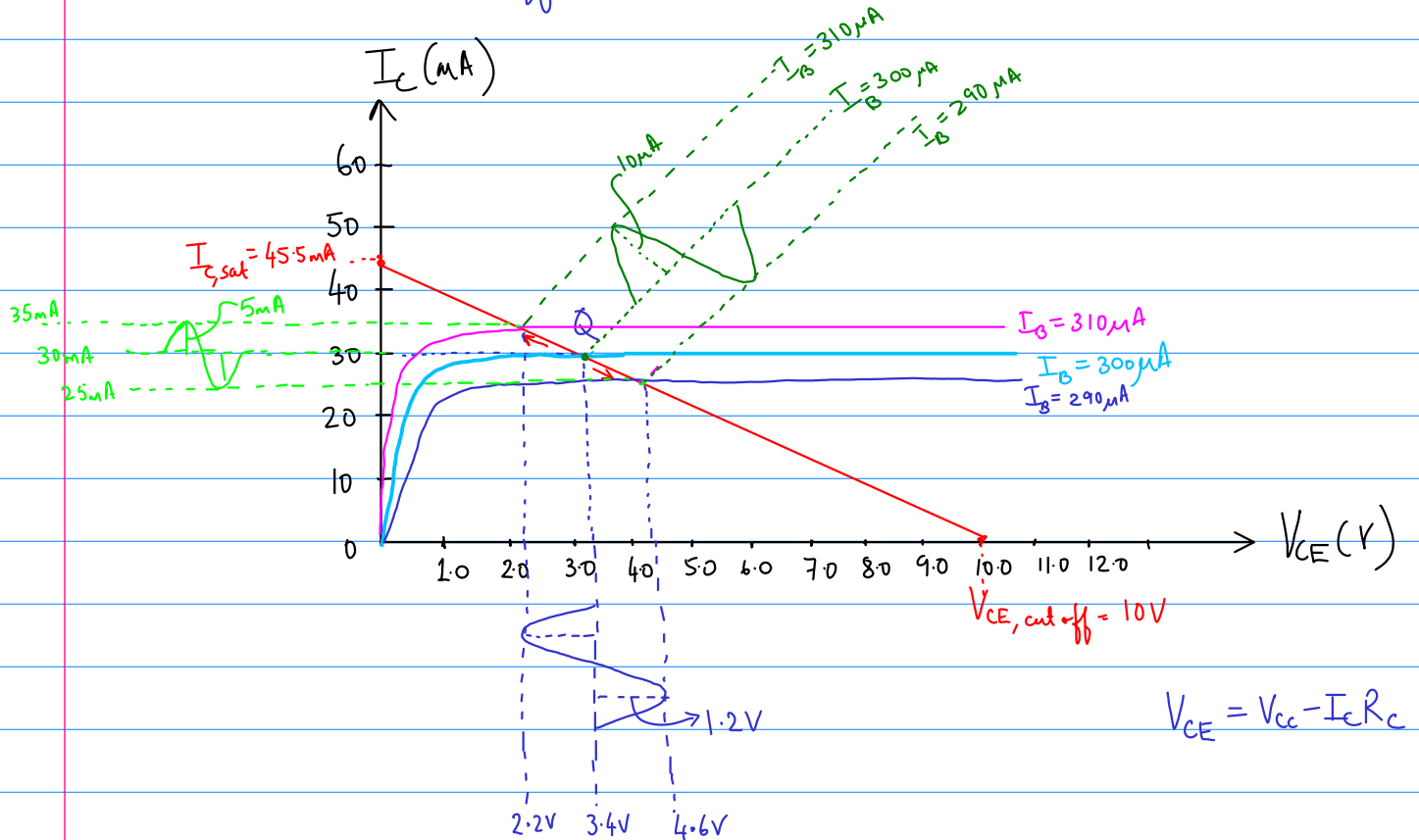

Look at the amplitude of the ac base-current = $10\mu A$

Amplitude of the ac collector-current = $5mA$


$$\text{Current Gain} = \frac{\text{Amp. of Collector-Current}}{\text{Amp. of Base-Current}}$$

$$= \frac{5mA}{10\mu A} = 500$$

⇒ The input signal strength is enhanced by 500 times.

How do we couple ac-signal with the DC current/voltage?

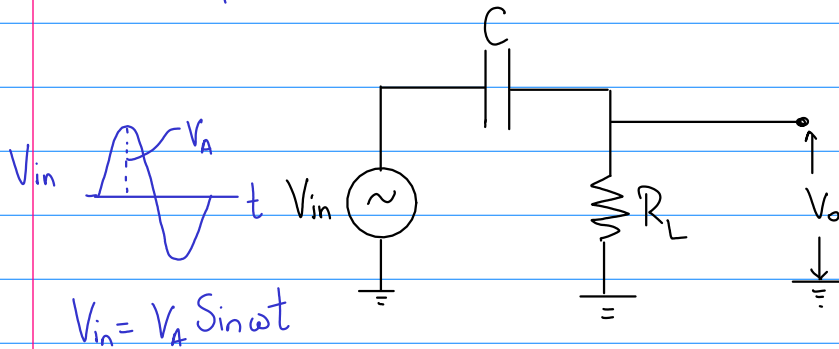To perform this task, we make use of the "Coupling Capacitor".



We know that, the capacitor reacts to the ac-signals.

$$X_c = \frac{1}{\omega C}$$

Case (i)

$$\Rightarrow X_c \propto \frac{1}{\omega}$$

Let $\omega \rightarrow 0$ (dc signal)

$$X_c \rightarrow \infty$$

\Rightarrow the capacitor is "OPEN-CIRCUITED"

Case (ii)

$\omega \rightarrow \infty$ (High-frequency)

$$X_c \rightarrow 0$$

\Rightarrow the capacitor behaves as "SHORT-CIRCUITED"

From the above discussion, we concluded that the capacitor is "OPEN" for DC signals and "SHORT" for ac signals

when $R_L \geq 10 X_c$ then the entire ac-signal will be available at R_L .

- Condition for a good Coupling .

Ckt. design of a simple amplifier ckt using BJT.

