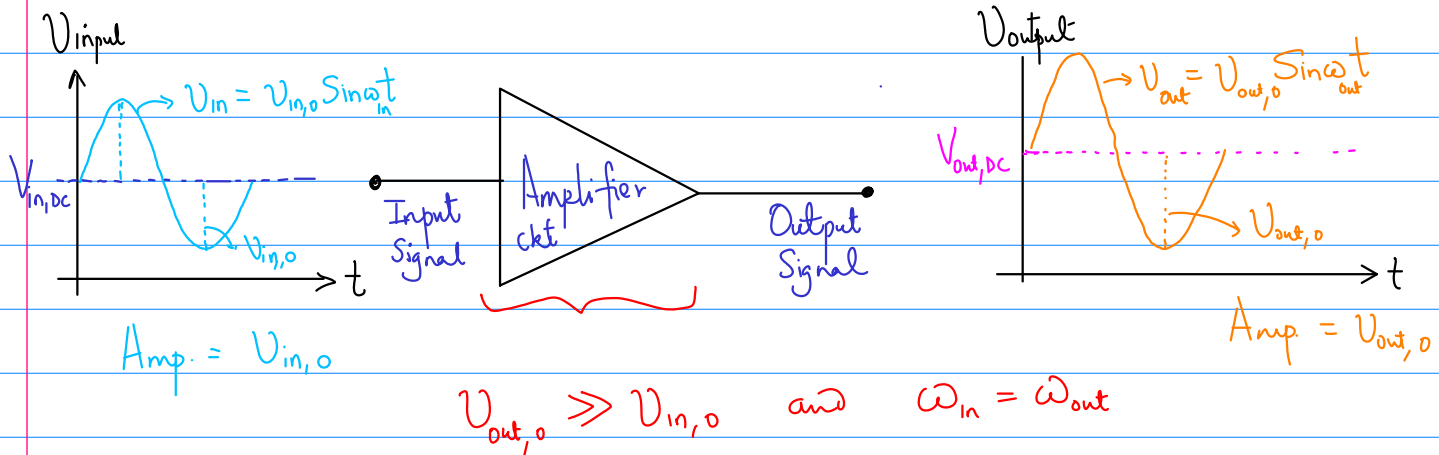



BJT Amplifiers

(Small Signal Amplifiers) { 10% Rule }

DC Biasing: It establishes stable dc operating point (Q-point)


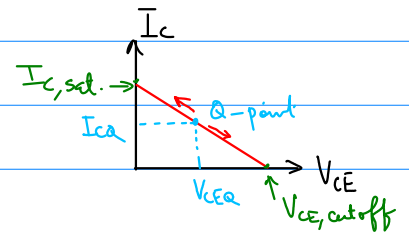
$$\Rightarrow \frac{V_{out,o}}{V_{in,o}} \gg 1$$




Small-Signal Amplifier: Variation about the 'Q-point' is relatively small.

Example: Lets look at a base-bias ckt. such that the Q-point lies nearly in middle of the load-line.

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{3.7V - 0.7V}{10k\Omega}$$

$$I_B = 0.3mA = 300\mu A$$
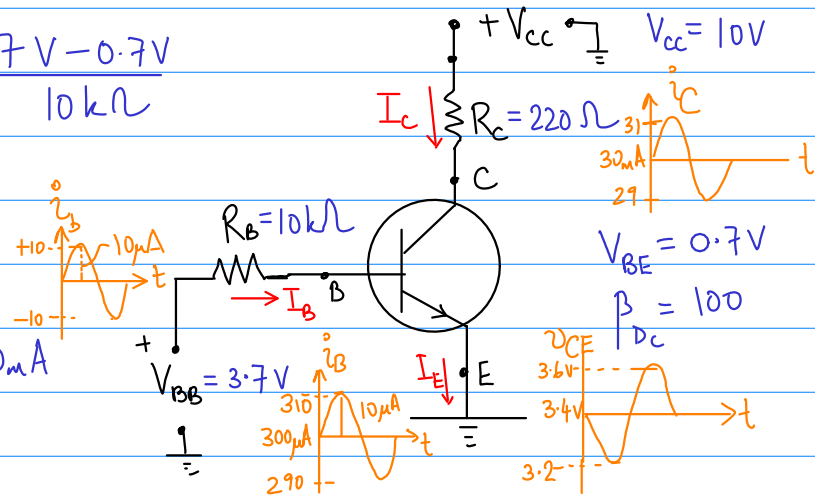
$$I_{C,DC} = \beta I_B = 100 \times 300\mu A = 30mA$$



$$V_c \downarrow = V_{cc} - I_c \uparrow R_c = 10V - (30mA)(220\Omega)$$


$$V_c = 3.4V$$

$$\Rightarrow V_{CE} = V_c - V_E = 3.4V - 0V = 3.4V$$

Q-point : 3.4V ; 30mA

$$I_{c,sat.} = \frac{V_{cc}}{R_c} = \frac{10V}{220\Omega} = 45.5mA$$

$$V_{CE, cut-off} = V_{cc} = 10V$$

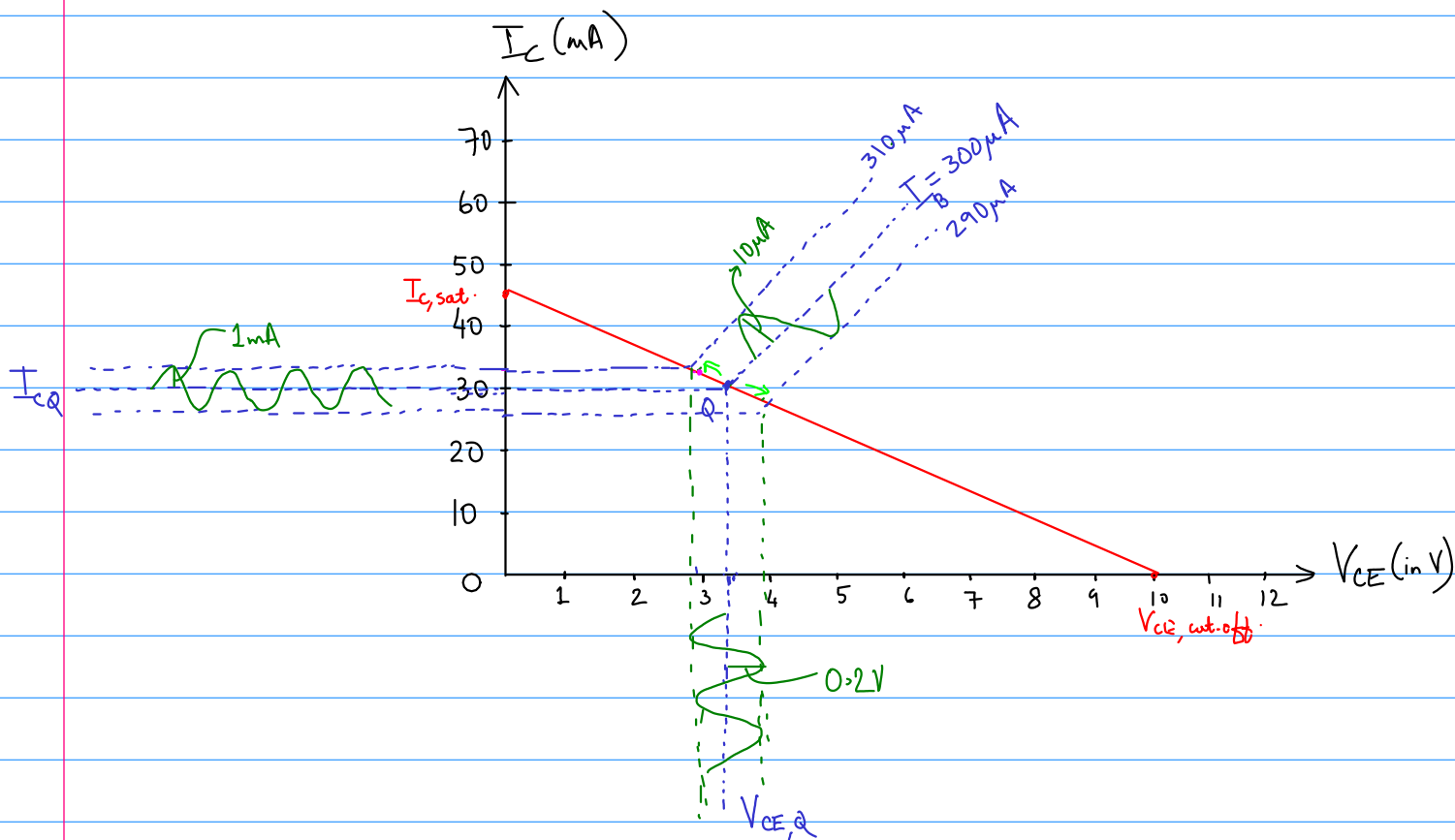

Amplitude of the input base-current = $10\mu A$


Amplitude of the output collector-current = $2mA$

$$\frac{i_{co}}{i_{bo}} = \frac{2mA}{10\mu A} = 200$$

⇒ Input signal is amplified by 200 times.

Ques: How do we couple / decouple ac-signal to the dc current/voltage level.

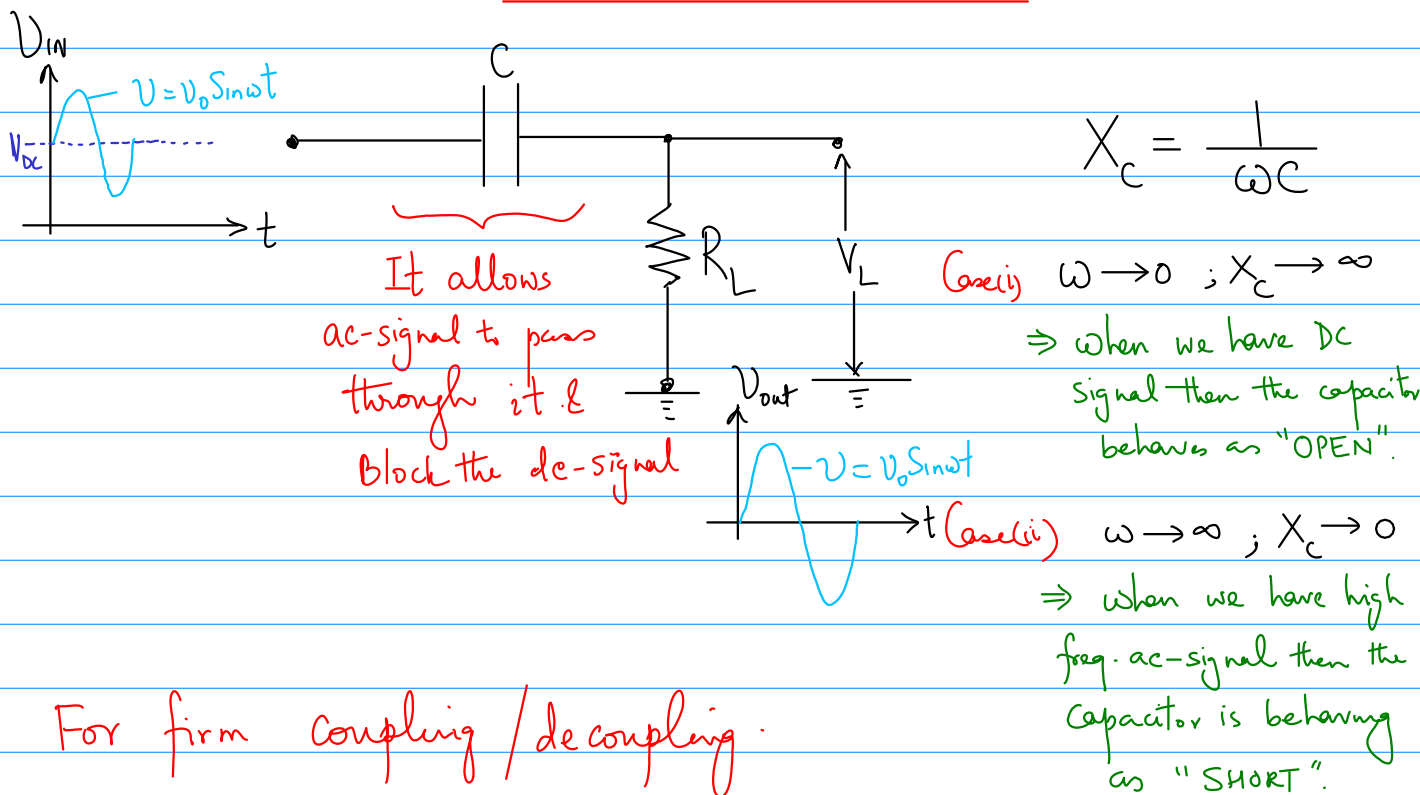
To perform this task, we make use of a capacitor called "COUPLING CAPACITOR".




For firm coupling / decoupling.

$$R_L \geq 10 X_C$$

Design of a base-bias amplifier ckt.

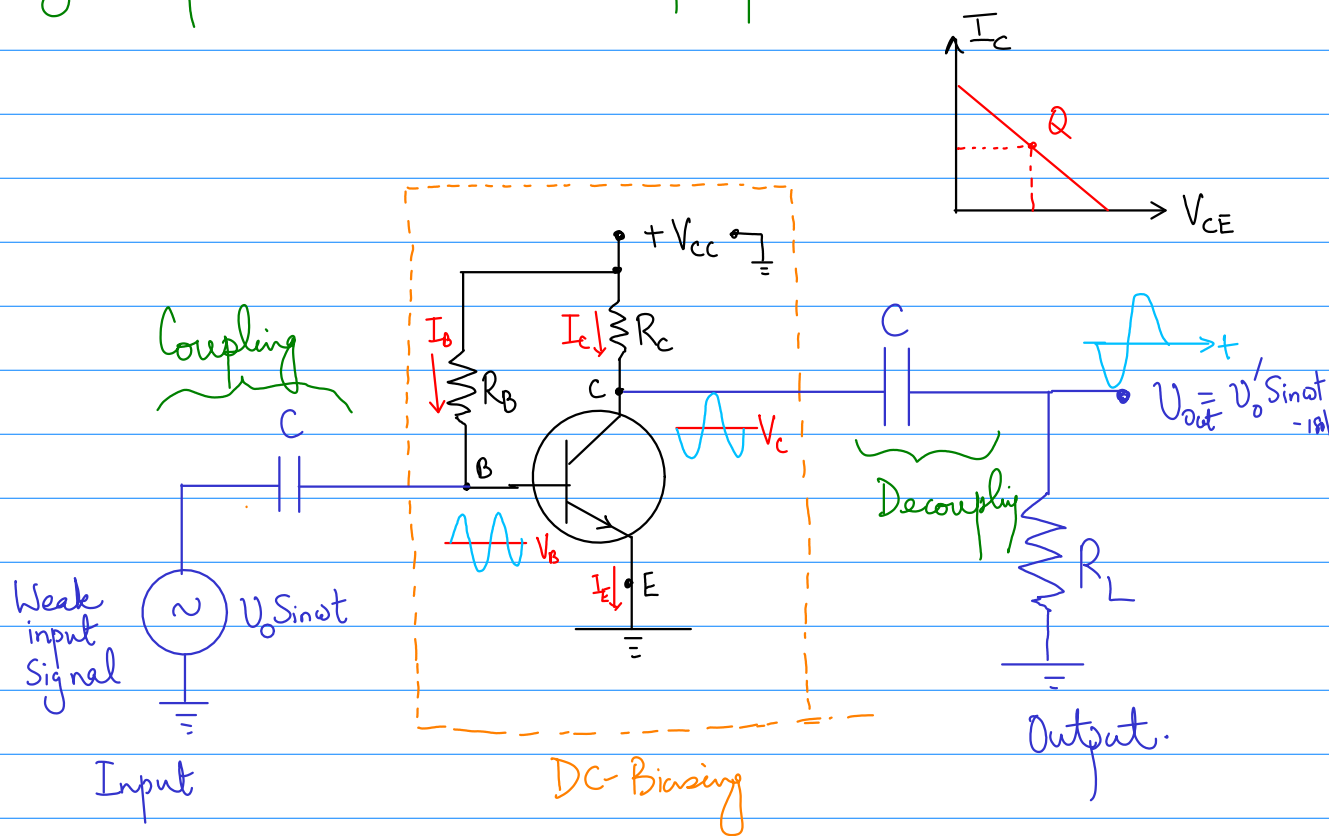

Common-Emitter Amplifier Circuit :

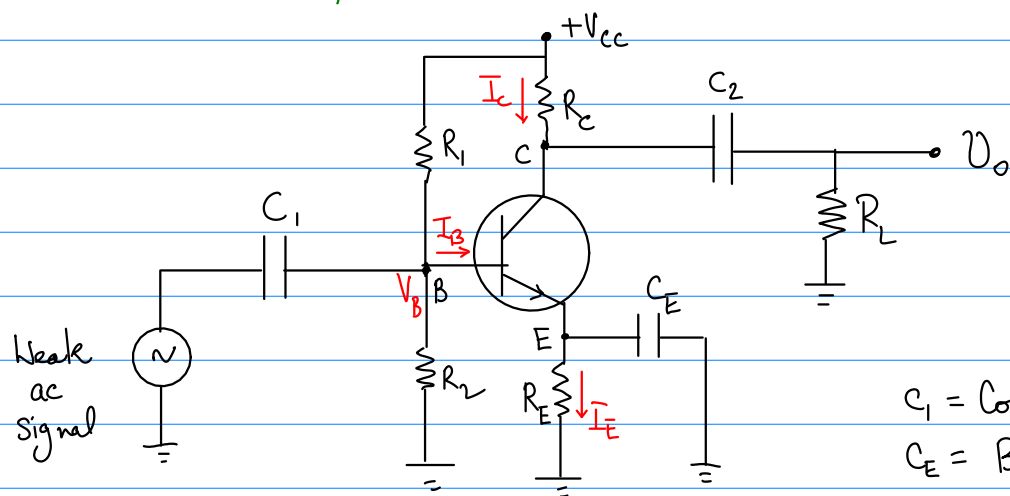

C_1 = Coupling Cap.
 C_E = By-pass Cap.
 C_2 = Decoupling Cap.