

Tutorial #05**AC analysis of the transistor:**

1. For a given circuit in Fig.1
 - a) Determine the lowest frequency (in Hz) of ac signal at which good coupling exist.
 - b) What would be the lowest frequency (in Hz) when the load resistance is reduced to $1\text{k}\Omega$?
 - c) What would be the lowest frequency (in Hz) when the capacitor is changed to $100\mu\text{F}$?
 - d) What would be the choice of resistor and capacitor if you would like to couple ac signal at 100Hz ?
2. For a given circuit in Fig.2
 - a) Discuss the condition at which terminal A appears to be ac ground.
 - b) If $R_1=600\Omega$ and $R_2=1\text{k}\Omega$, determine C for which terminal A appears to be ac ground.
 - c) For $R_1=2.2\text{k}\Omega$, $R_2=10\text{k}\Omega$ and $C=220\mu\text{F}$, determine the lowest frequency at which terminal A appears ac ground.
3. For the given VDB amplifier in Fig.3
 - a) Draw dc equivalent circuit and determine I_B , I_E , I_C , V_B , V_C , V_E and V_{CE} . (Assume dc current gain is β_{dc} and $V_{BE}=0.7\text{V}$)
 - b) Draw ac equivalent circuit considering (i) T-model of the transistor and (ii) π -model of the transistor.
 - c) Determine the emitter ac resistance r_e' for $R_1=10\text{k}\Omega$, $R_2=2.2\text{k}\Omega$, $R_C=3.6\text{k}\Omega$, $R_E=1\text{k}\Omega$ and $V_{CC}=10\text{V}$.
 - d) Using the result of (c) determine input impedance at base, i.e., $Z_{in(\text{base})}$. (use $\beta=100$)
 - e) Determine the voltage gain A_v , if $R_L=10\text{k}\Omega$. [use the value of other elements from (c) and (d)]
4. For the given circuit in Fig.4
 - a) Draw ac equivalent circuit. (use π -model of the transistor)
 - b) Determine $Z_{in(\text{stage})}$.
 - c) Determine v_{in} .
 - d) Draw dc equivalent circuit and determine r_e' and hence calculate voltage gain A_v .
 - e) Using the result of part (c) and (d) determine v_{out} .
5. For the given two stage amplifier in Fig. 5
 - a) Draw dc and ac equivalent circuits.
 - b) Determine r_e' , $Z_{in(\text{stage})}$ and v_{in} .
 - c) Calculate A_{v1} , A_{v2} , and A_v .
6. For the given swamped amplifier in Fig.6, use T-model of the transistor to determine voltage gain A_v and $Z_{in(\text{base})}$.
7. Using ac equivalent circuit of Fig.7, determine the output voltage. (use $\beta=200$ and ignore r_e')

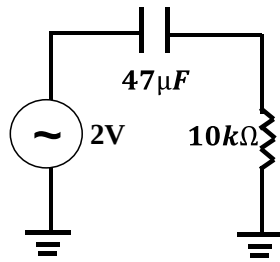


Fig.1

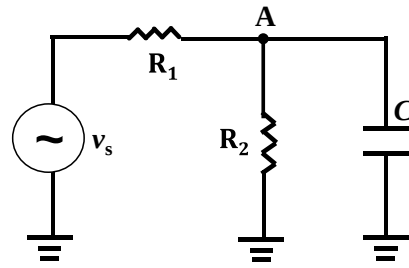


Fig.2

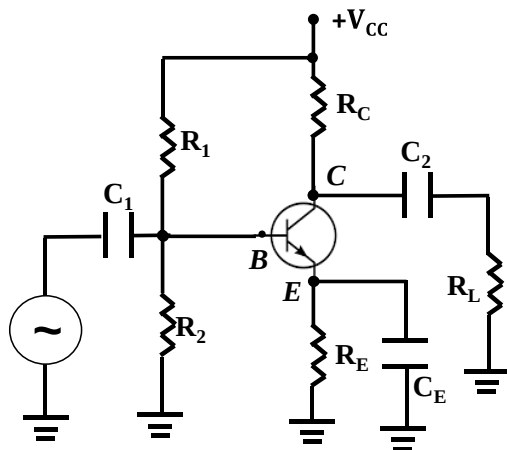


Fig.3

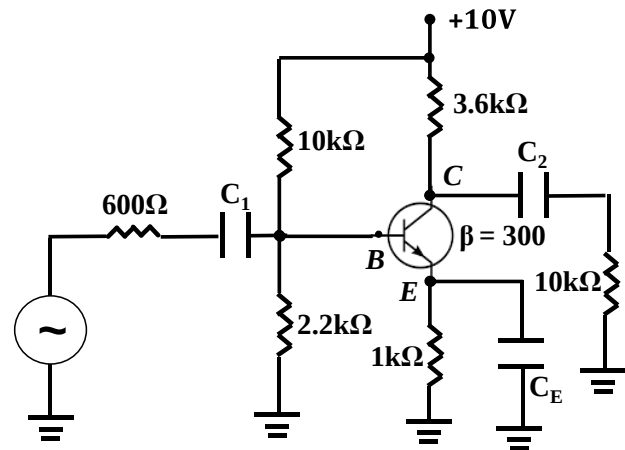


Fig.4

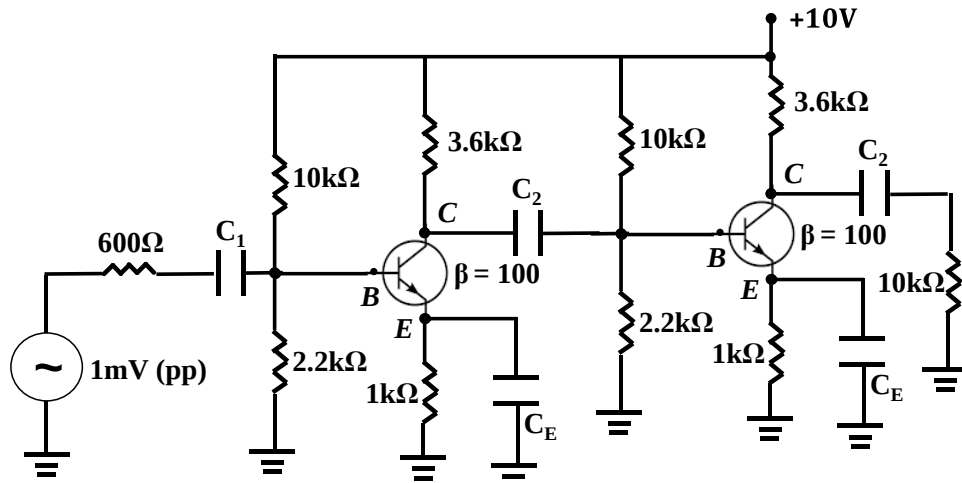


Fig.5

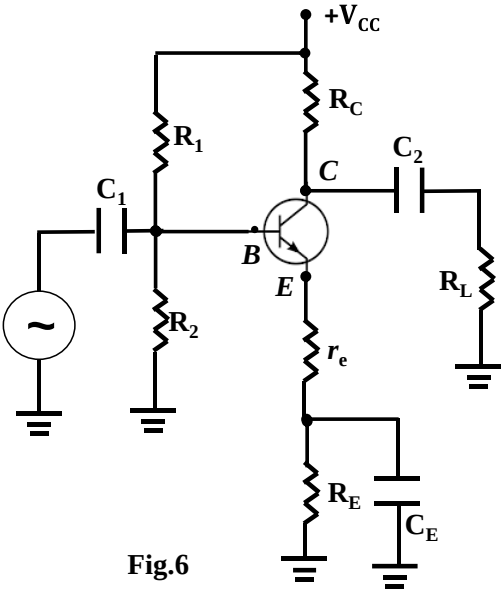


Fig.6

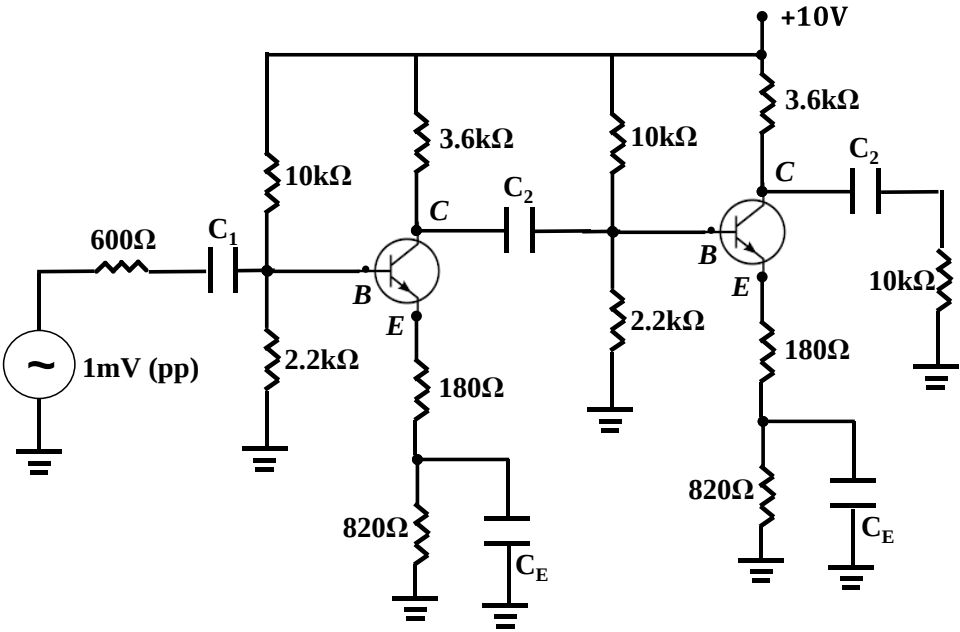


Fig.7