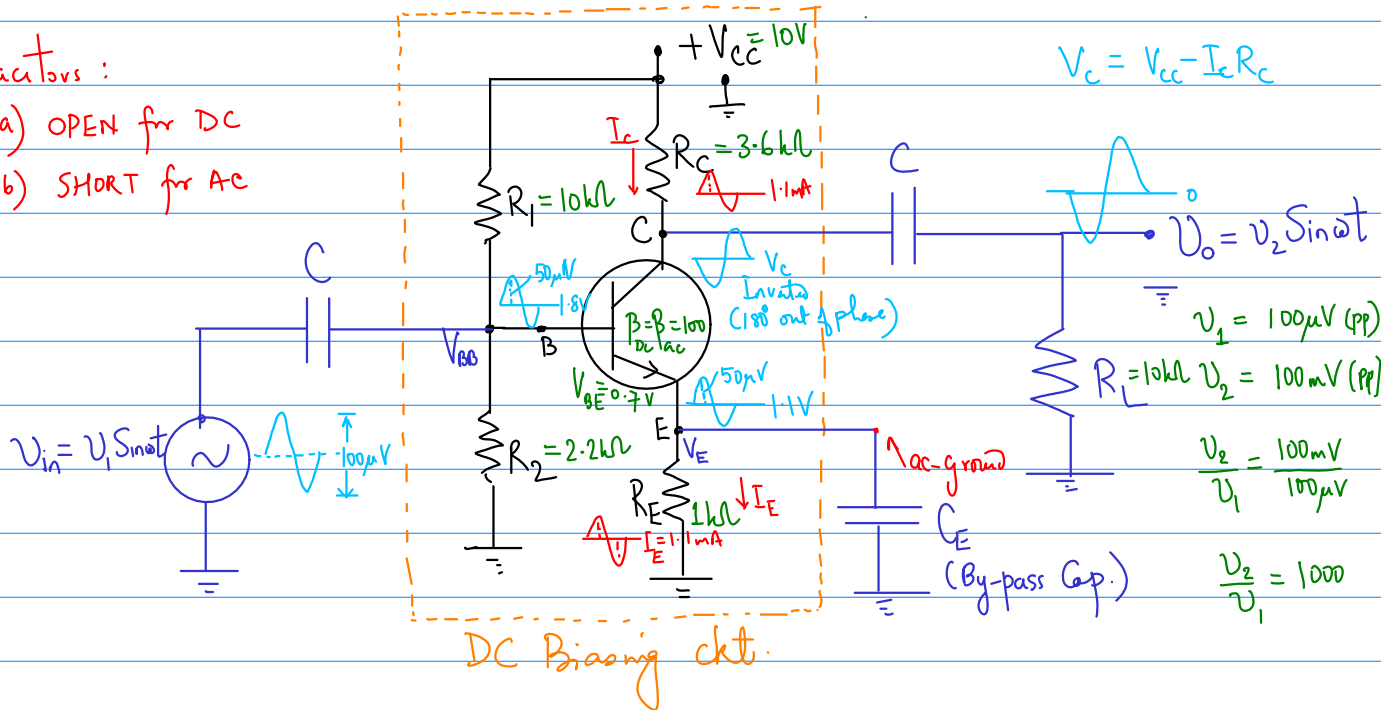


BJT Amplifier : DC and AC Analysis

Common Emitter (CE) Amplifier Circuit :

Capacitors :

- OPEN for DC
- SHORT for AC





- Voltage gain = 1000

Input Characteristics:

$$I_E = I_B + I_C ; I_E \approx I_C$$

$$I_E \propto I_B$$

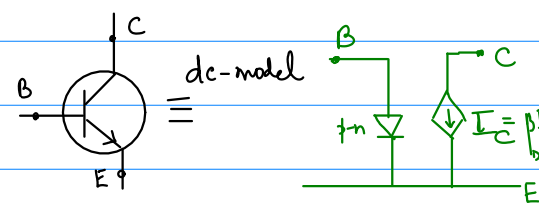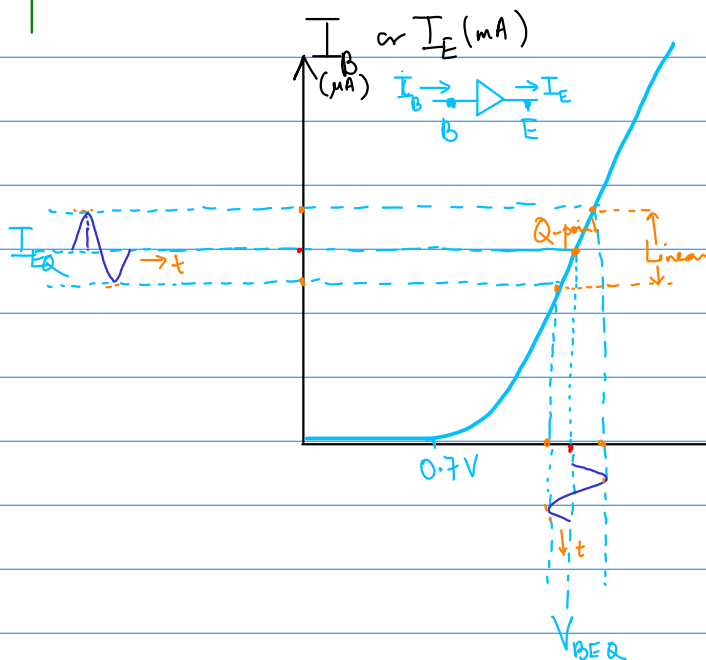

at any instant of time 't';

$$\underbrace{i_E}_{\text{Total-current}} = \underbrace{I_{EQ}}_{\text{DC-current}} + \underbrace{i_e}_{\text{ac-current}}$$

$$\underbrace{V_{BE}}_{\text{Total Base-Emitter voltage}} = \underbrace{V_{BEQ}}_{\text{DC}} + \underbrace{v_{be}}_{\text{ac}}$$

Here, we define ac-resistance of the base-emitter diode:

ac-Emitter Resistance $r_e' = \frac{v_{be} \text{ (ac-voltage)}}{i_e \text{ (ac-current)}}$ → prime indicates that the resistance is within the transistor ie, virtual.

example at instant of time $\left. \begin{array}{l} v_{be} = 5\text{mV} \\ i_e = 200\mu\text{A} \end{array} \right\} r_e' = \frac{5\text{mV}}{200\mu\text{A}} = 25\Omega$

Note: There is a standard formula to determine the value of ac-emitter resistance (r_e' , resistance of the base-emitter diode)


$$r_e' = \frac{25\text{mV}}{I_E}$$

where, I_E is the dc emitter-current.

Transistor ac circuit Model:

①

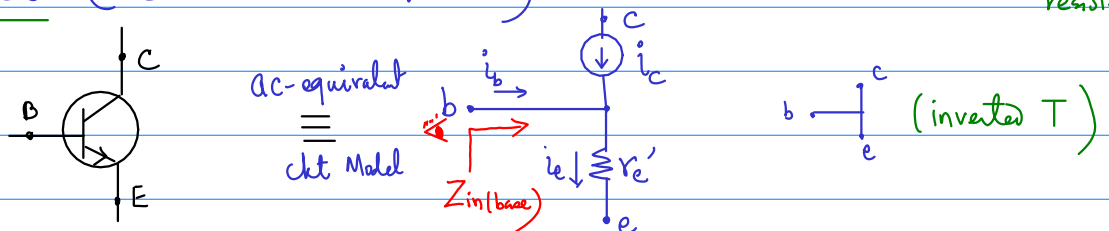T-model (Eber-Moll Model): Base-Emitter Diode \rightarrow ac-emitter resistor



$$\underline{i_e \approx i_b + i_c} \quad i_e \approx i_c = \beta i_b$$


Input impedance as seen from the base terminal

$$Z_{in(base)} = \frac{V_{be}}{i_b} = \frac{i_e r'_e}{i_b} = \frac{i_e r'_e}{i_b} = \beta r'_e$$

$$\text{where, } \beta = \frac{i_c}{i_b}$$

$$Z_{in(base)} = \beta r'_e$$

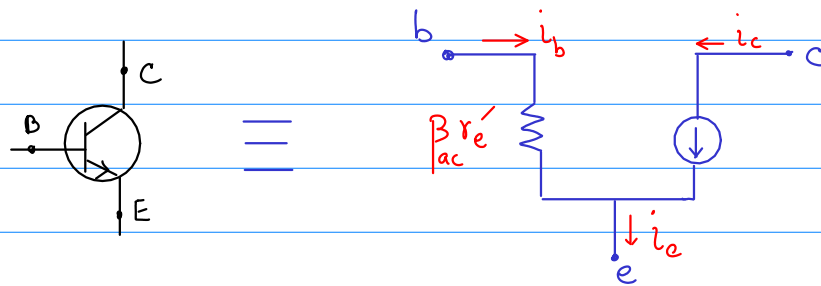② TT-Model : (Visual representation of $Z_{in(base)}$)




Note: Both the T- and π -model are equivalent circuit model of a BJT.

Analysis of a given CE Amplifier (Both DC & AC).

We apply Superposition theorem:

That is, effect of each sources acting alone is added to get the total effect of all the sources acting simultaneously.

① DC-Analysis : DC-equivalent ckt.

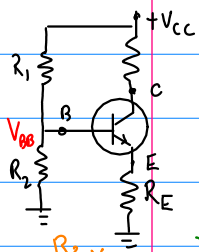

- Mentally "OPEN" all the capacitors.
- Determine the operating point (Q-point).
 - V_{CEQ} , I_{CQ}

$$V_{BB} = \frac{R_2 V_{CC}}{R_1 + R_2}$$

$$V_E = V_{BB} - V_{BE}$$

$$I_E = \frac{V_E}{R_E}$$

$$I_C \approx I_E$$

$$V_C = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$


Q-point
(V_{CEQ} , I_{CQ})

- Determine $r_e' = \frac{25mV}{I_E}$
ac-emitter resistance

② AC-Analysis :

- for all ac current, dc source acts as a 'SHORT'
- 'SHORT' all the capacitors
- Replace the BJT with equivalent ac-ckt model (ie, either T or π)!

ac-equivalent ckt. of the CE Amplifier:

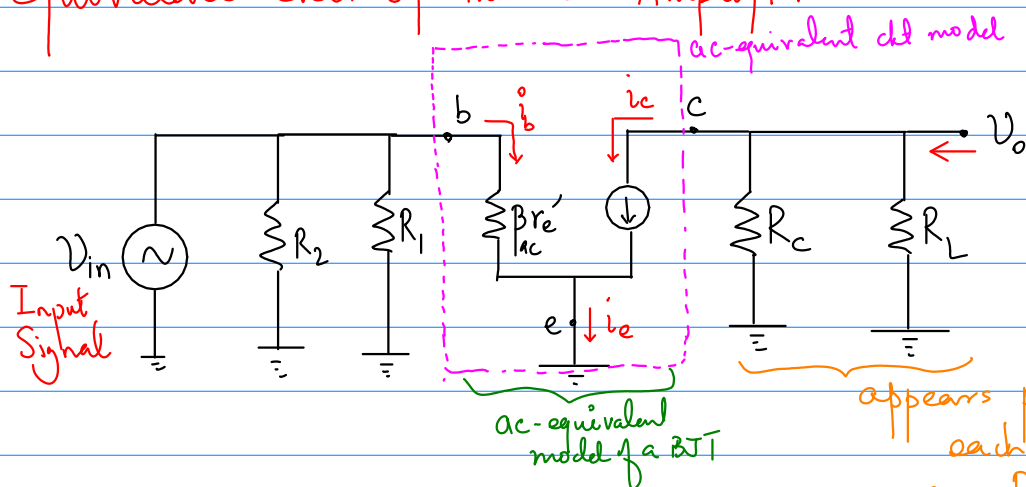

$$V_{in} = i_b \cdot Z_{in(base)} = i_b \beta r_e'$$

appears parallel to each other

$$r_c = R_L \parallel R_C = \frac{R_L R_C}{R_L + R_C}$$

$$V_o = i_c r_c$$

We define voltage gain $A_v = \frac{V_o}{V_{in}} = \frac{i_c r_c}{i_b \beta_{ac} r_e'}$

Voltage Gain

$$A_v = \frac{r_c}{r_e'}$$

$$r_c = R_c \parallel R_L$$

$$r_e' = \frac{25 \text{ mV}}{I_E}$$

From the given CE amplifier ckt.

$$r_c = \frac{R_L \cdot R_c}{R_L + R_c} = \frac{10 \text{ k}\Omega \times 3.6 \text{ k}\Omega}{10 \text{ k}\Omega + 3.6 \text{ k}\Omega}$$

$$r_c = \frac{36 (\text{k}\Omega)^2}{13.6 \text{ k}\Omega} = 2.64 \text{ k}\Omega$$

$$\text{Now, } r_e' = \frac{25 \text{ mV}}{I_E} = \frac{25 \text{ mV}}{1.1 \text{ mA}} = 22.7 \Omega$$

$$\text{Therefore, Voltage gain } A_v = \frac{r_c}{r_e'} = \frac{2.64 \text{ k}\Omega}{22.7 \Omega}$$

$$A_v = \frac{2640}{22.7} \approx 110$$

$$A_v = 110$$

\Rightarrow If the amplitude of the input signal is $1 \mu\text{V}$ then the amp. of output signal is $110 \mu\text{V}$ (0.11 mV)