


p-n Diode : Applications

Since p-n diodes are unidirectional element, meaning it has ability to conduct currents in one direction and block in other direction.

- Diodes are used in circuits called rectifiers that convert ac voltage into dc voltage.
- Rectifier ckt. are found in all dc power supply that operates from an ac source.

A) Rectifier Operation:

(i) Half-Wave Rectifier:

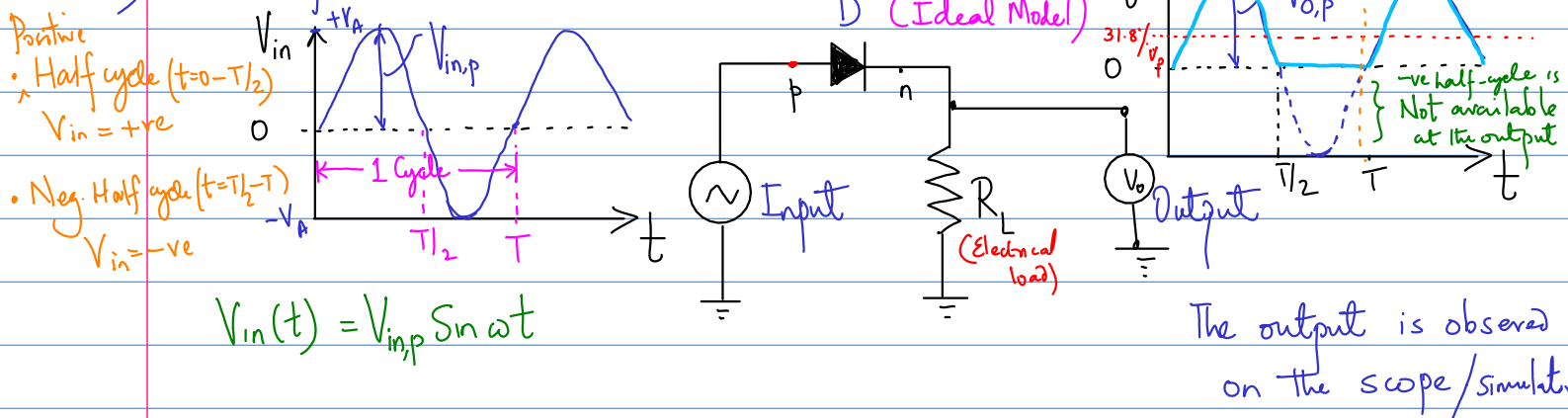

What would be voltage across R_L when a DC voltmeter is connected across it?

- It measures the average value of the output signal.

Mathematically, it is the area under the output signal over a full (one) cycle and then divided by 2π , the number of radians in a full cycle.

$$V_{ave.} = \frac{1}{2\pi} \int_{t=0}^{t=T/2} V_{o,p} \sin \omega t \, d(\omega t) + \frac{1}{2\pi} \int_{t=T/2}^{t=T} V_{o,p} \sin \omega t \, d(\omega t)$$


+ve half-cycle -ve half-cycle = 0

$$\Rightarrow \boxed{V_{ave.} = \frac{V_{o,p}}{\pi}} \approx 31.8\% \text{ of } V_{o,p}$$

In order to incorporate the effect of barrier potential in p-n diode on half-wave rectifier,

We use "Modified Ideal Diode Model":



For practical p-n diode:

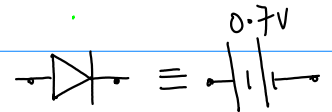

$$V_{o,p} = V_{in,p} - 0.7V$$

$$\boxed{V_{ave} = \frac{V_{o,p}}{\pi} = \frac{(V_{in,p} - 0.7V)}{\pi}}$$

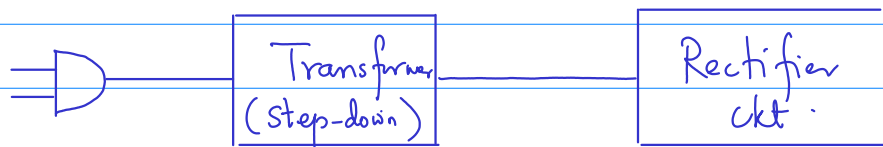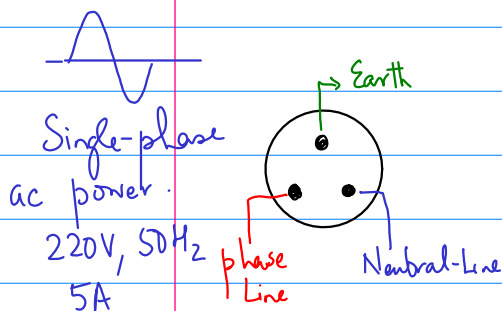
$V_{in,p}$ = Amplitude of the input signal.



In practice, the rectifier ckt. is connected with the step-down transformer at the input terminal.

Advantages:

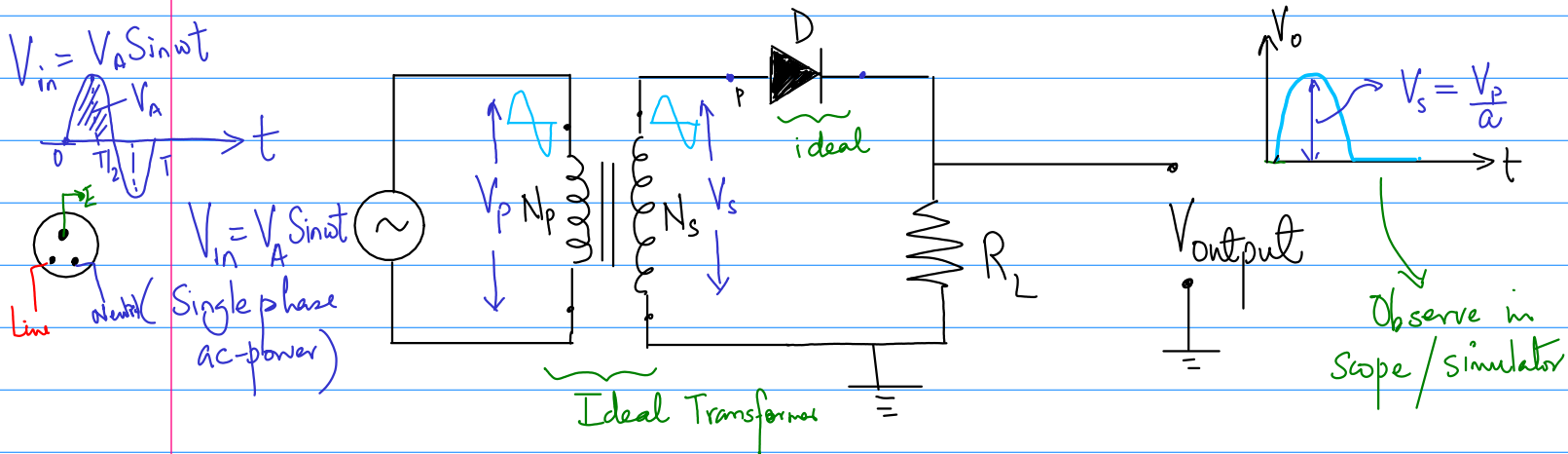- i) Allows the source voltage to step-down
- ii) Prevents rectifier ckt. with any electrical hazard.



In transformer, we define

$$\text{Turn ratio, } a = \frac{N_p}{N_s} = \frac{V_p}{V_s}$$

$$a > 1 \Rightarrow V_p > V_s \Rightarrow \text{Step-down}$$

$$a < 1 \Rightarrow V_p < V_s \Rightarrow \text{Step-up}$$

$$V_p = a V_s ; N_p = a N_s ; I_p = \frac{1}{a} I_s$$

If you connect dc voltmeter across the R_L

$$V_{ave} = \frac{V_s}{\pi} = \frac{V_p/a}{\pi} = \frac{V_{in}/a}{\pi}$$


$$\left(V_{ave.} \right)_{\text{Transformer Coupled Rectifier}} = \frac{V_{in}/a}{\pi}$$

For practical diodes :

$$\left(V_{ave.} \right)_{\text{Tran. Coupled}} = \frac{(V_{in}/a) - 0.7V}{\pi}$$

V_{in} = amplitude of the input voltage.

Full-Wave Rectifier:

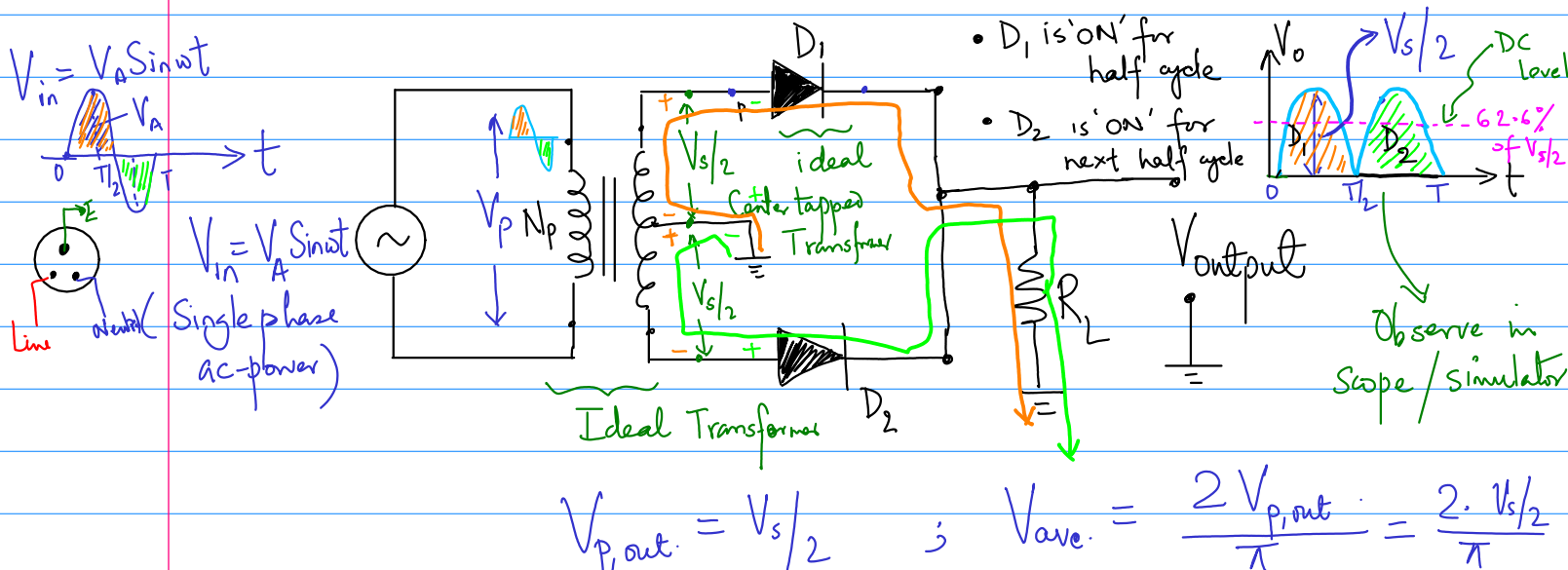


For practical diode;

$$V_{P,out} = \left(\frac{V_s}{2} - 0.7V \right)$$

$$\Rightarrow V_{ave.} = \frac{2V_{P,out}}{\pi} = \frac{2}{\pi} \left(\frac{V_s}{2} - 0.7V \right)$$

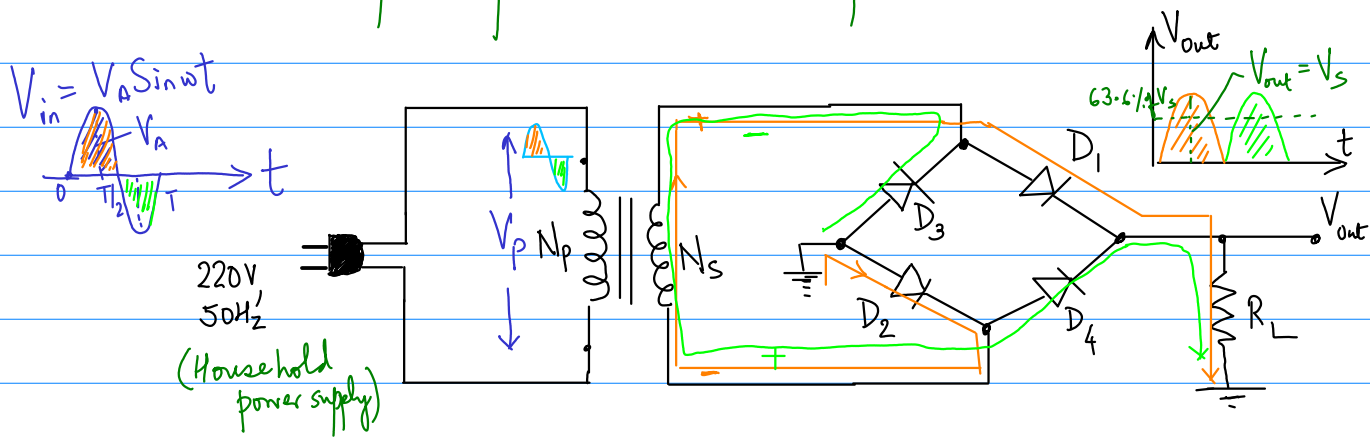Alternate circuit for full-wave rectifier:



for +ve half cycle: D_1 & D_2 - ON ; D_3 & D_4 - OFF

for -ve half cycle: D_3 & D_4 - ON ; D_1 & D_2 - OFF

$$V_s = V_p / a = V_{app} / a$$

$$V_{out} = V_s \quad (\text{considering diodes to be Ideal})$$

$$V_{ave.} = \frac{2V_{out}}{\pi}$$



For practical circuit:

$$V_{out} = V_s - 1.4V$$

Since two diodes are replaced with two voltage sources of $0.7V$ each.

$$V_{ave} = \frac{2}{\pi} (V_s - 1.4V)$$

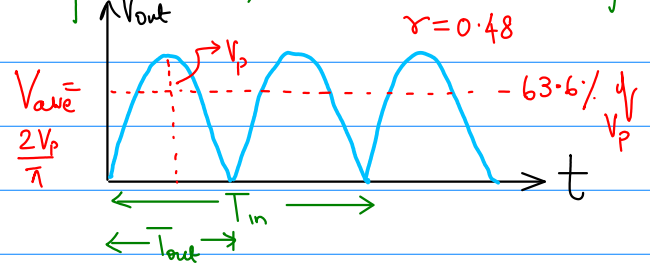
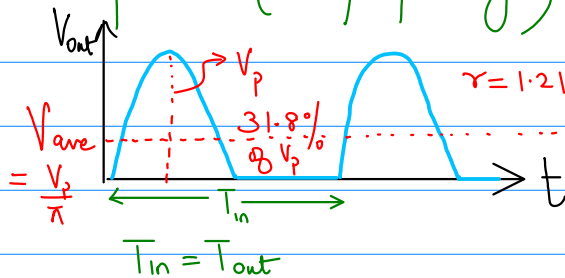
Time-period (or frequency) of Half-wave / Full-wave rectifier




- For half-wave rectifier: Time-period of output voltage is same as input voltage. That is, if input frequency is 50Hz then output frequency is also 50Hz .
- For full-wave rectifier, the time-period of output voltage is half of the input voltage. That is, the frequency of output voltage will be 100Hz for 50Hz input frequency.

Remember: Output of the rectifier ckt. is time-varying

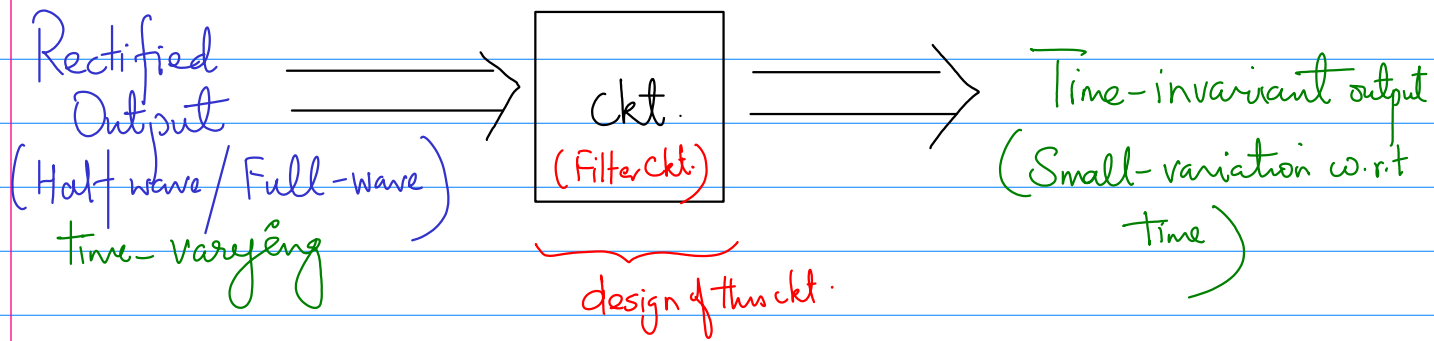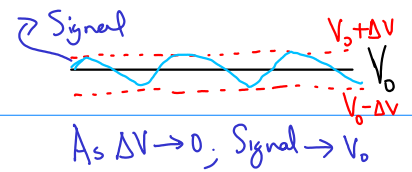⇒ To get time-invariant output, we need another circuit
→ Filter circuit:




RC circuit : (a) charging

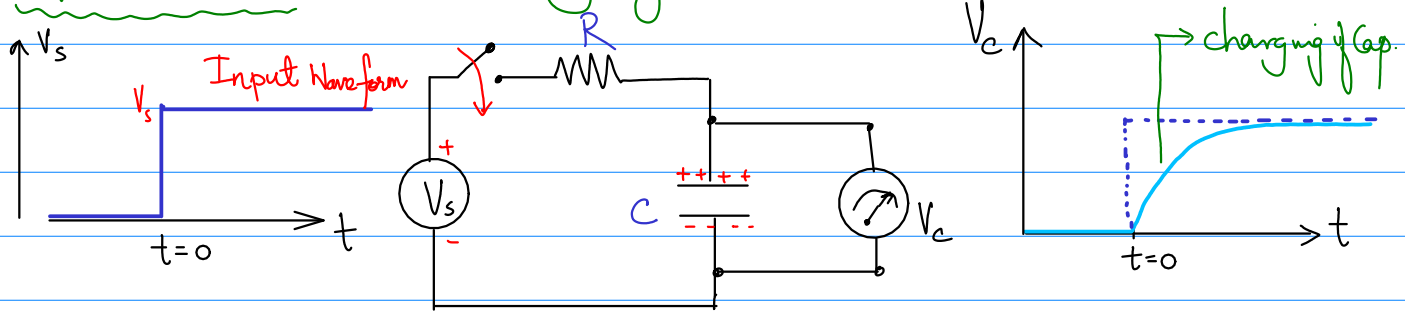

$$V_c(t) = V_s (1 - e^{-t/\tau})$$

Time constant: $\tau = RC$; $t = 5\tau$; $V_c(t) \approx V_s$



b) Discharging :

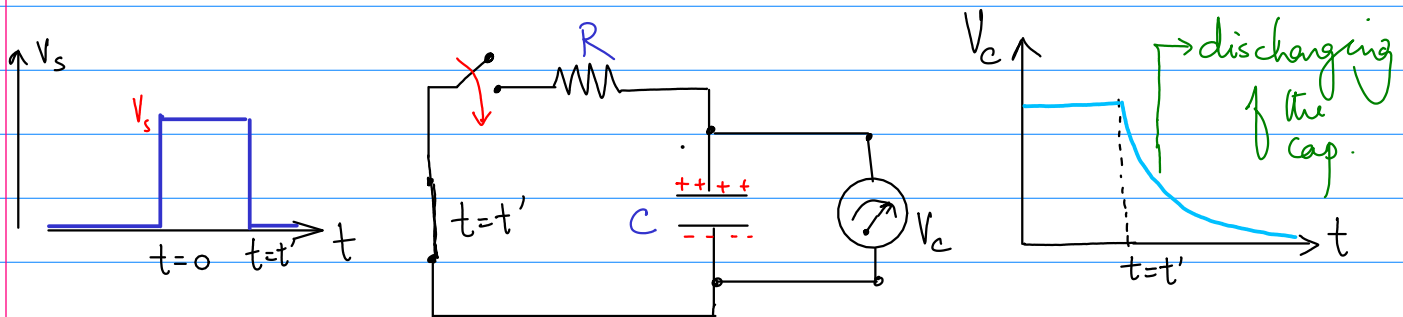


$$V_c(t) = V_s e^{-t/\tau}$$

$$\tau = RC$$


when $t = 5\tau$, then $V_c \approx 0$

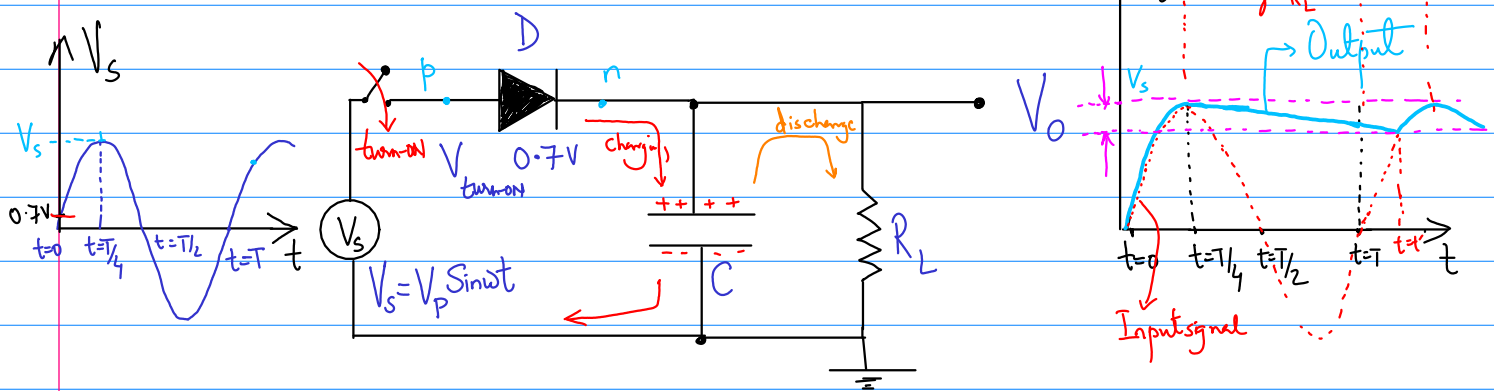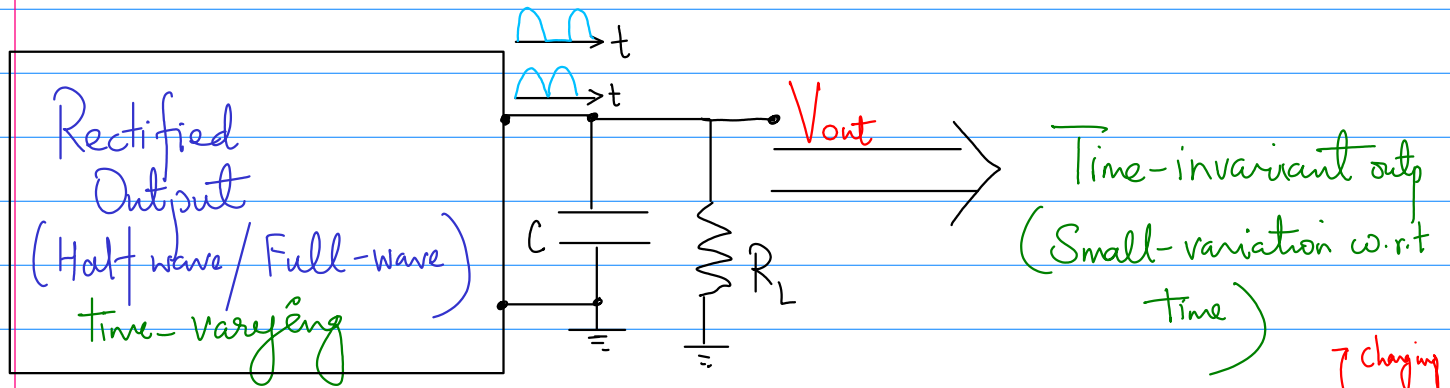

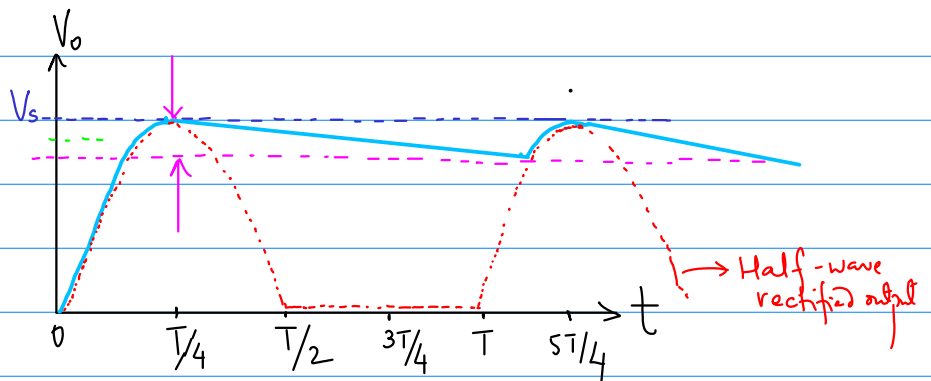
In half-wave rectifier with filter circuit, we get the following output:



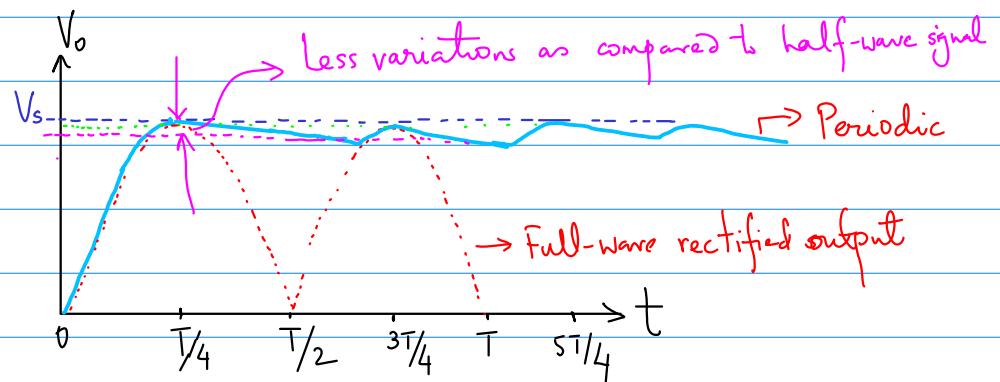In full-wave rectifier with filter circuit, we get the following output



Ripple & Ripple factor :

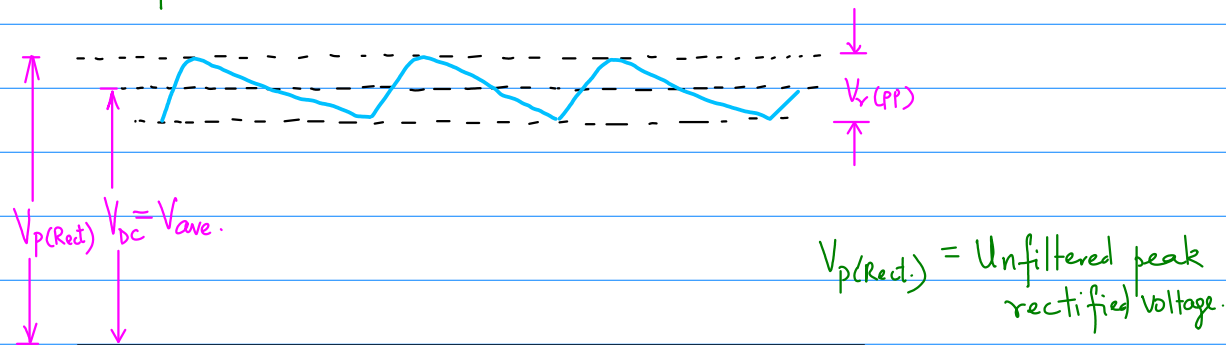

here, $V_{r(pp)} = \text{Ripple voltage peak-to-peak}$

$V_{DC} = \text{Average value of the filtered output voltage (DC voltage)}$


$$\text{Ripple factor, } r = \frac{V_{r(pp)}}{V_{DC}}$$

$$\text{where, } V_{r(pp)} \sim \left(\frac{1}{f R_L C} \right) V_{P(\text{Rect.})}$$

$$V_{DC} \sim \left(1 - \frac{1}{2 f R_L C} \right) V_{P(\text{Rect.})}$$


The lower the ripple factor 'r', better is the filter design.

Voltage-Regulator :

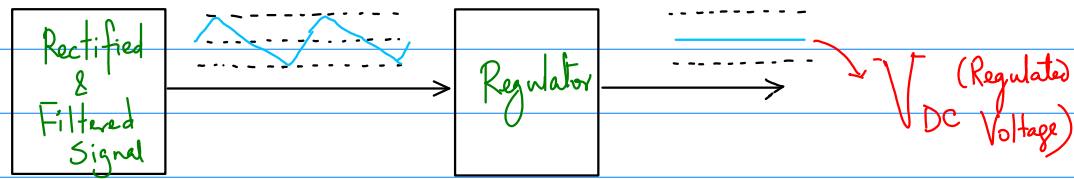

- Zener Diode in reverse bias
- IC 7805

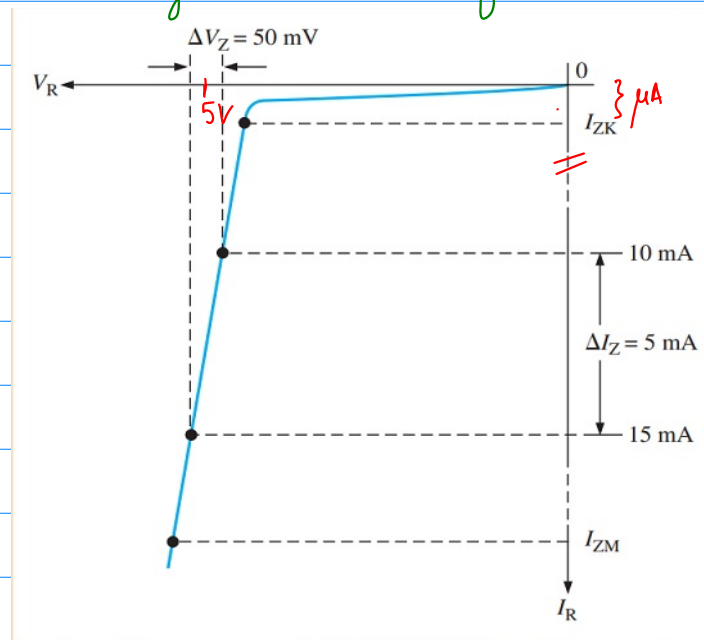Current-Voltage Characteristics of Zener Diode :




Circuit Model of Zener Diode :


ie, for $V_R \geq V_Z$; \equiv V_Z

for $V_R < V_Z$; \equiv open

Working of Zener Regulator:

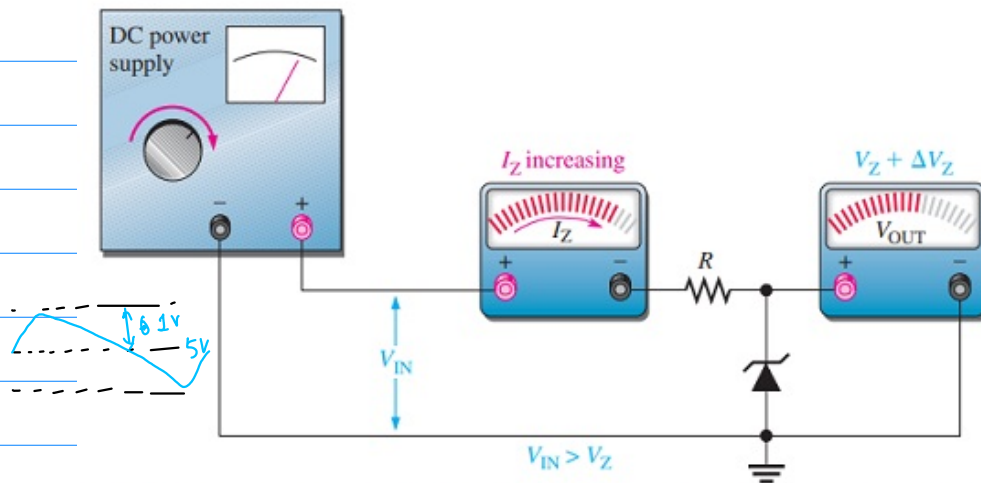

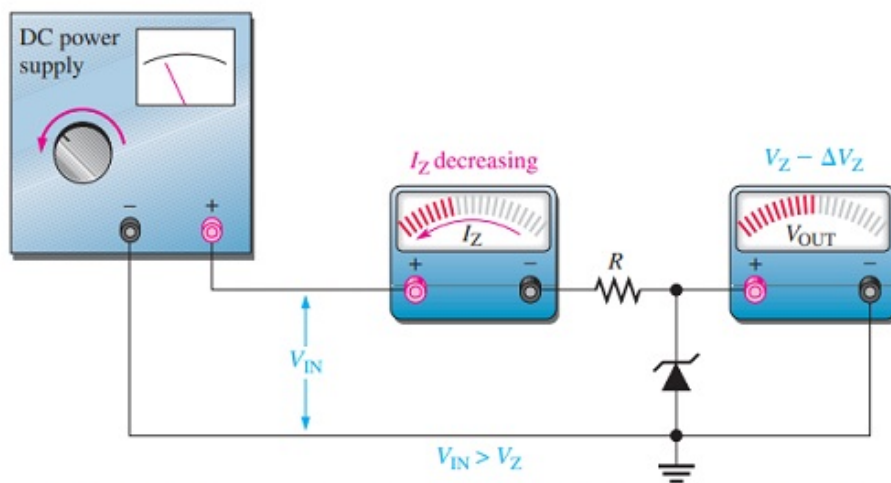(a) As the input voltage increases, the output voltage remains nearly constant ($I_{ZK} < I_Z < I_{ZM}$).



(b) As the input voltage decreases, the output voltage remains nearly constant ($I_{ZK} < I_Z < I_{ZM}$).

Percentage of Voltage Regulation :

— It is a figure of merit that specifies the performance of the voltage regulator.

(a) Line Regulation :
(Any variation in inputs)

$$\text{Line Reg.} = \frac{\Delta V_{out}}{\Delta V_{in}} \times 100$$

(b) Load Regulation :

$$\text{Load Reg.} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$$