

Indian Institute of Information Technology Vadodara (Gandhinagar Campus)

End Semester Examination | Semester-I | Autumn 2021-22

Course: EC100 Basic Electronic Circuits

Full Marks: 80

Date: 07/04/2022

Time: 11:35 AM-1:15 PM

Instructions:

1. Attempt part (a) OR (b) of Q2 and Q7. All other questions are compulsory.
2. Only scientific calculators are allowed to be used.
3. Each question carries ten marks.

✓ Q1. For the given input waveform to the diode circuit shown in Fig. 1, draw the output waveform.

✓ Q2. (a) The energy level diagrams of the isolated p -type and n -type doped silicon are shown in Fig. 2(a) and 2(b), respectively. (i) Draw the equilibrium energy-level diagram when they are physically joined. (ii) Show the directions of diffusion and drift currents. (iii) Calculate the value of built-in potential.

OR

✓ (b) Find the value of V_{out} in the circuit shown in Fig. 9. Assume the given Op-Amps are ideal, i.e., $A_{OL} = \infty$.

✓ Q3. Calculate the value of dc current gain β_{DC} of the given bipolar junction transistor in Fig. 3.

✓ Q4. Sketch an ideal family of output characteristics for the circuit shown in Fig. 4. The characteristics should be sketched for the base current $I_B = 5\mu A$ to $25\mu A$ with the increments of $5\mu A$. Assume $\beta_{DC} = 100$ and that collector-emitter voltage V_{CE} does not exceed the breakdown region. Label the saturation and active regions of operation. Draw the dc load line for $V_{CE(cutoff)} = 30V$ and collector resistance $R_C = 4.7k\Omega$. Indicate the operation point for each of the curves in the family.

✓ Q5. Determine how much the operating point (Q-point) for the circuit in Fig. 5 will change over a temperature range where β_{DC} increase from 100 to 200. [Assume base-emitter voltage $|V_{BE}| = 0.7V$]

✓ Q6. For the given voltage amplifier circuit in Fig. 6, (i) draw the dc equivalent circuit and determine ac-emitter resistance r'_e , (ii) draw the ac equivalent circuit using a π -model of transistor and determine the voltage gain A_V , (iii) determine the minimum value for the emitter by-pass capacitor for the amplifier to operate over a frequency range of 200 Hz to 10 kHz.

✓ Q7. (a) Determine the critical frequencies associated with the low-frequency response of the BJT amplifier in Fig. 7. What is the dominant critical frequency? Show it on the A_V (dB) versus f curve.

OR

(b) (i) Explain Pinch-off in an n -channel JFET with proper diagram. Why does the drain current (I_D) become almost constant at Pinch-off? What is the impact on the depletion layer if we increase V_{DS} after pinch-off for a specific value of V_{GS} ? (ii) The device parameters for n -channel JFET are: Maximum drain current $I_{DSS} = 15$ mA; Pinch-off voltage $|V_p| = |V_{GS(off)}| = 4V$. Calculate the I_D for $V_{GS} = 0$ V, -2 V and -4 V.

✓ Q8. For the given input waveform to the operational amplifier shown in Fig. 8, draw the output waveform.

Please turn-over for the figures.

Fig. 1

 


Fig. 2(a)

 


Fig. 2(b)

 


Fig. 3

 


Fig. 4

 


Fig. 5

 


Fig. 6

 


Fig. 7

 


Fig. 8

 


Fig. 9

