


Bipolar Junction Transistors (BJTs)

- 1951, William Shockley

Bipolar : Both electrons & holes are participating in device operation.

Junction : p-n / n-p (Barrier potential associated with junction).

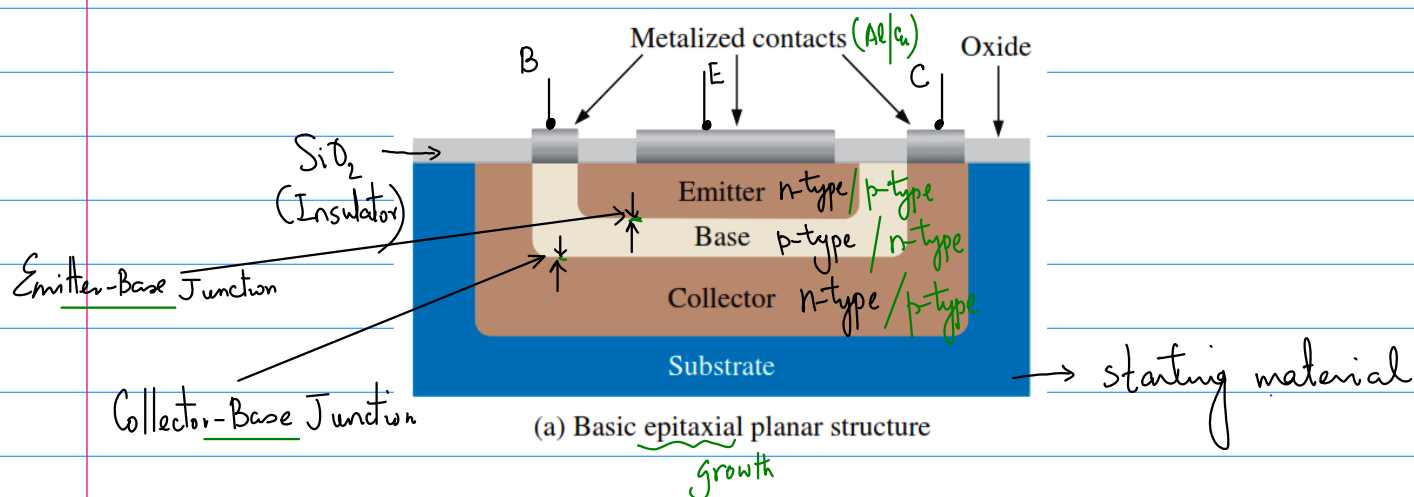
Transistor : Transfer of resistor (ie, transfer of current levels)



Fabrication of a BJTs.




Thickness :

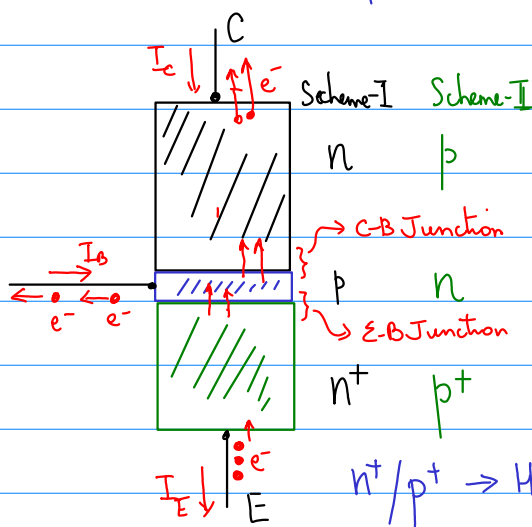C : Thickest layer
B : Thinnest layer
E : Moderate thickness



Doping levels :

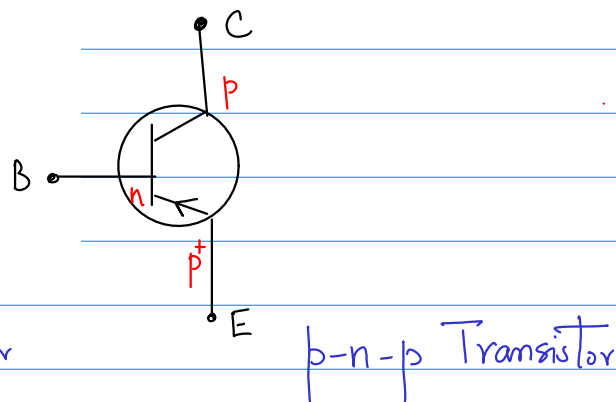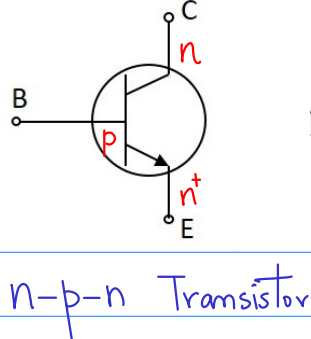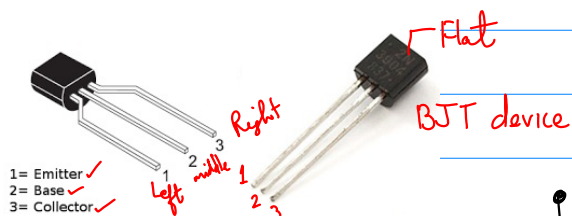
C : Moderately doped ($\sim 10^{14-15} \text{ cm}^{-3}$ dopant)
B : Lightly doped ($10^{12-13} \text{ cm}^{-3}$)
E : Heavily doped ($10^{16-18} \text{ cm}^{-3}$)



Basic BJT operation :

(i) Emitter-Base Junction : Forward-Bias

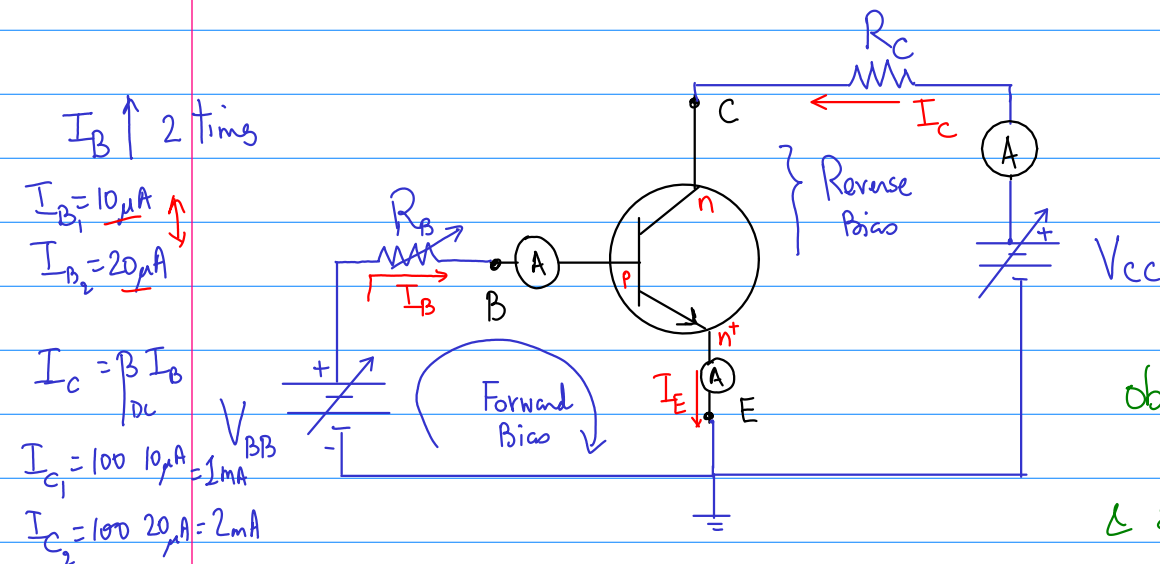(ii) Collector-Base Junction : Reverse-Bias



We are trying to observe the current levels in the collector, Base & Emitter terminal.

- Any change in the Base-Emitter terminals, the change is directly appearing in the collector terminal.

$$I_E = I_B + I_C$$

$$I_E; I_C \sim \text{mA}$$

$$I_B \sim \mu A$$


We define a parameter, $\beta_{DC} = \frac{I_C}{I_B} = \frac{\sim \text{mA}}{\sim \mu\text{A}} \approx 100$ (typical)

β_{DC} = typically varies b/w 50-300

- "Current gain"


$$\beta_{DC} = \frac{I_C}{I_B} \Rightarrow I_C = \beta_{DC} \cdot I_B$$

Transistor DC Model:

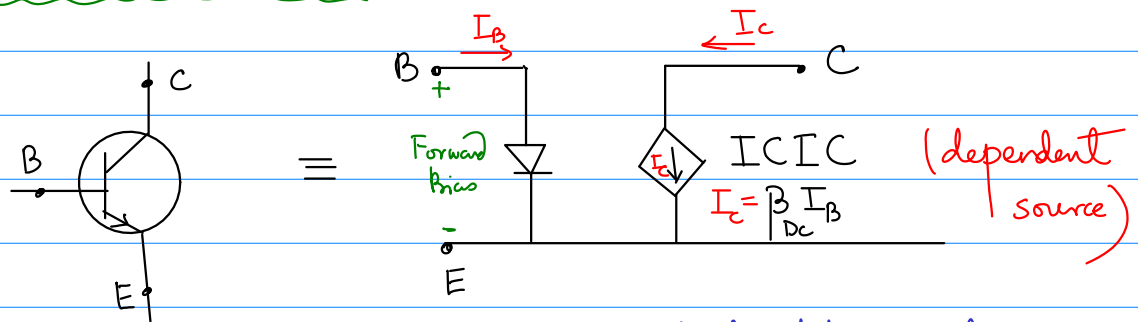

Equivalent ckt model.

Biasing BJT:

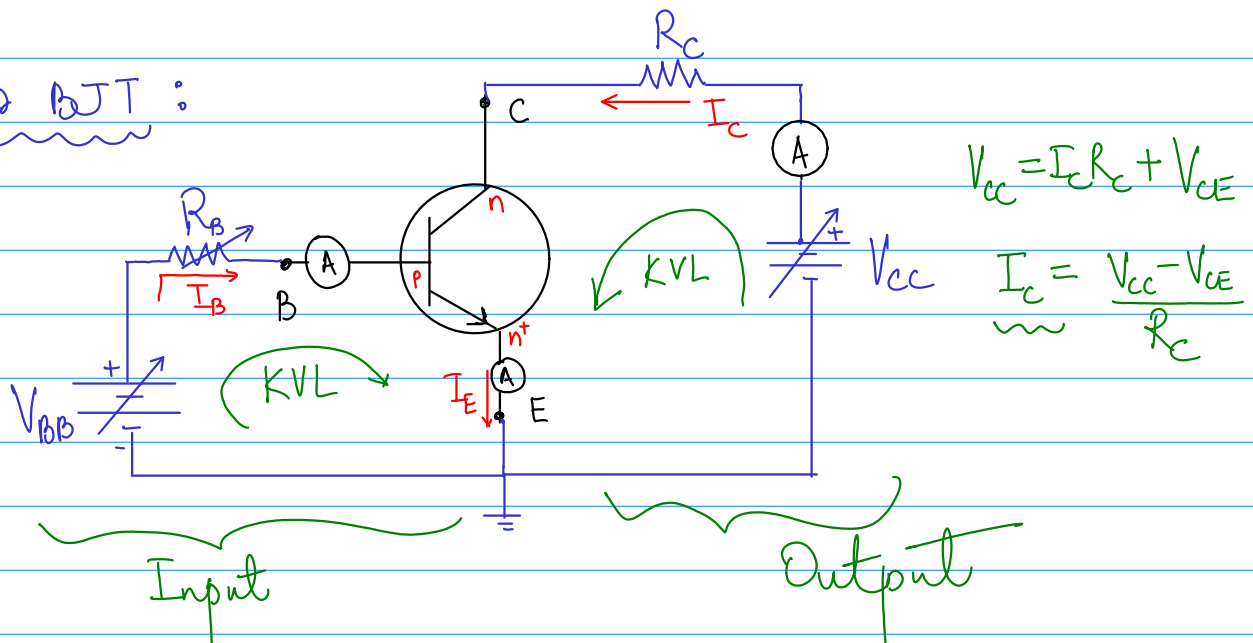

$$V_{BB} = I_B \cdot R_B + V_{BE} \Rightarrow I_B = \frac{V_{BB} - V_{BE}}{R_B}$$