

Assignment # 04

$$3.3 \sim \frac{10}{3}$$

Transistor Biasing:

1. For the given circuit in Fig.1,

- Draw the load line,
- Calculate $I_{C(sat.)}$,
- Calculate $V_{CE(cutoff)}$,

What happens to the load line if (i) V_{CC} enhanced to 25V, (ii) R_C increased to 4.7k Ω and (iii) R_B reduced to 500 k Ω . In each of these cases, other parameters of the circuit remain the same.

- For $\beta_{DC} = 200$, determine V_C . (wrt grd.)
- If β_{DC} varies between 25 to 300 then determine $V_{C(max)}$ and $V_{C(min)}$.
- Determine whether the transistor is saturated for each of these changes: (i) $R_B = 33$ k Ω , $\beta_{DC} = 100$. (ii) $V_{BB} = 5V$, $\beta_{DC} = 200$, (iii) $R_C = 10$ k Ω , $\beta_{DC} = 50$ and (iv) $V_{CC} = 10V$, $\beta_{DC} = 100$.

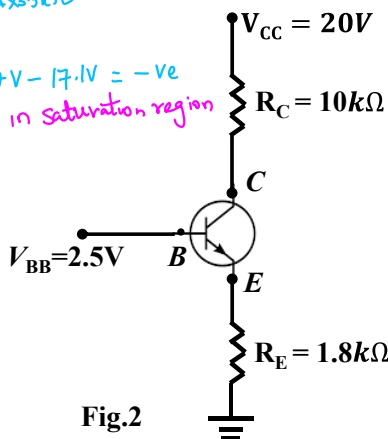


Fig.2

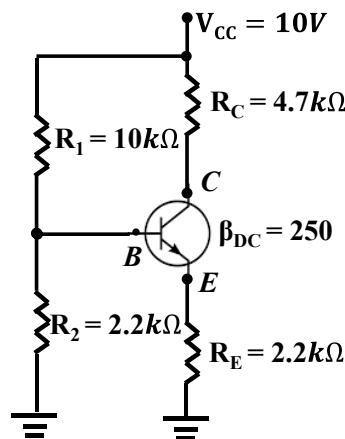


Fig.3

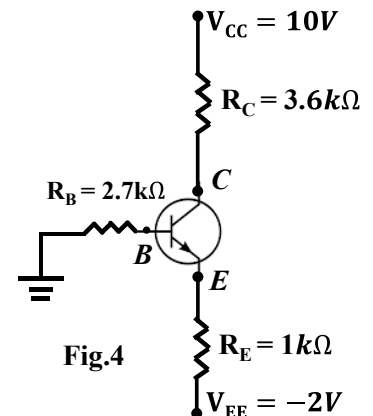


Fig.4


2. For the given circuit in Fig.2,

- Determine V_C and V_E .
- If $R_E = 3.6$ k Ω then determine V_{CE} .
- If $V_{CC} = 15$ V then determine V_C .
- If the base supply voltage V_{BB} decreases by 10%, what happens to the base current, collector current, and collector voltage?

3. For a given voltage-divider bias circuit in Fig.3

- Is the voltage divider stiff?
- Determine the operating point Q on the load line.
- What will happen to this Q-point when β_{DC} varies between 50-300?
- What will happen to this Q-point when R_E is doubled?

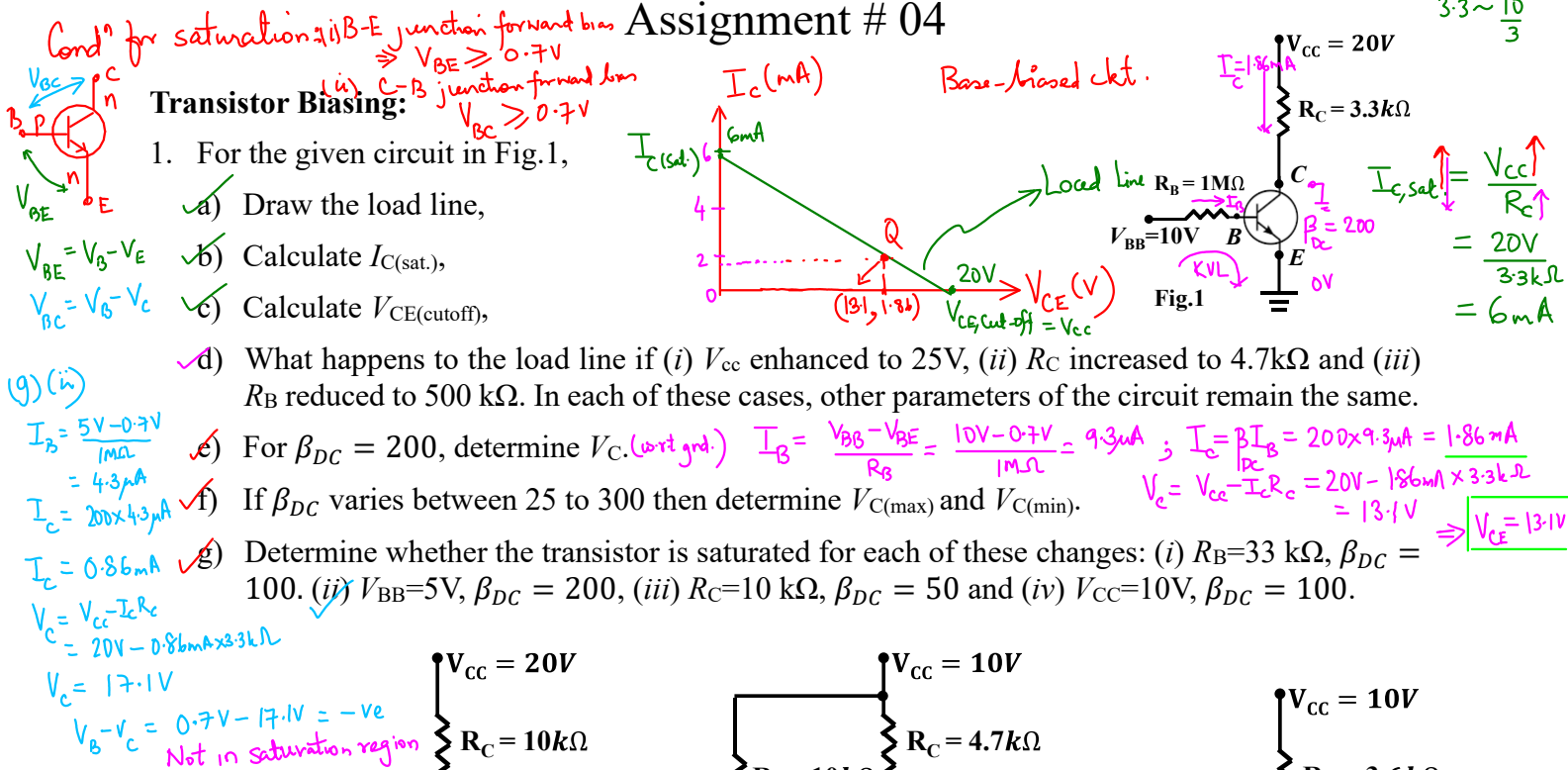4. For the circuit shown in Fig.3, determine the resistor values (i.e., R_1 , R_2 , R_E and R_C) to meet these specifications: $V_{CC} = 10V$; V_{CE} @ midpoint, $I_C = 10mA$ and $\beta_{DC} = 100-300$.



- Analyse the circuit in Fig.4 to locate the Q-point on the load-line.
- Analyse the given emitter-feedback circuit in Fig.5. How does the operating point change when β_{DC} varies from 100 to 300?
- Analyse the given collector-feedback circuit in Fig.6. How does the operating point change when β_{DC} varies from 100 to 300? Compare the results of Ques 5 and 6 and suggest which circuit gives better stability of Q-point?
- Analyse the circuit in Fig.7 and locate the Q-point on the load-line.

