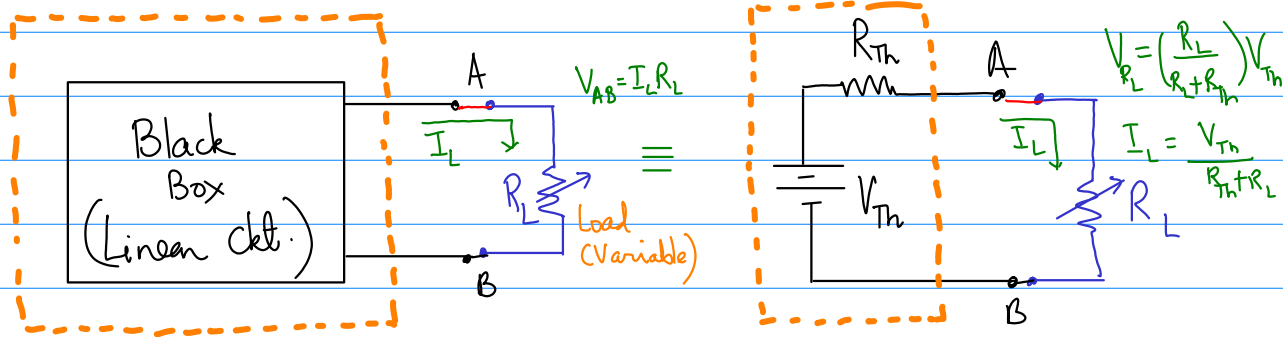


Circuit Theorems

Recap:


- 1) Superposition Theorem
- 2) Thevenin Theorem

Response
(each source should be looked at separately)
⇒ Add all effects.



Black Box \equiv replaced with a single voltage source V_{Th} & a series resistance R_{Th} .


3) Norton Theorem :

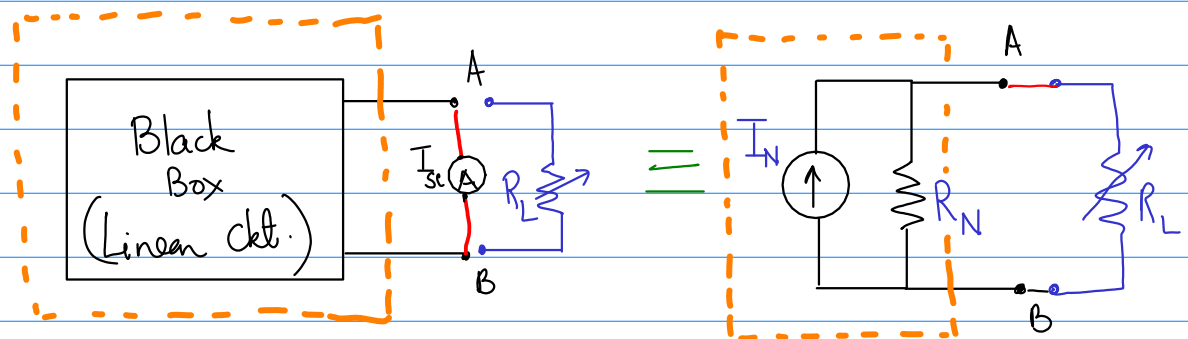

here, $I_N = I_{sc}$ in Thevenin's equivalent ckt.

$$I_N = \frac{V_{Th}}{R_{Th}}$$


$$R_N = R_{Th}$$

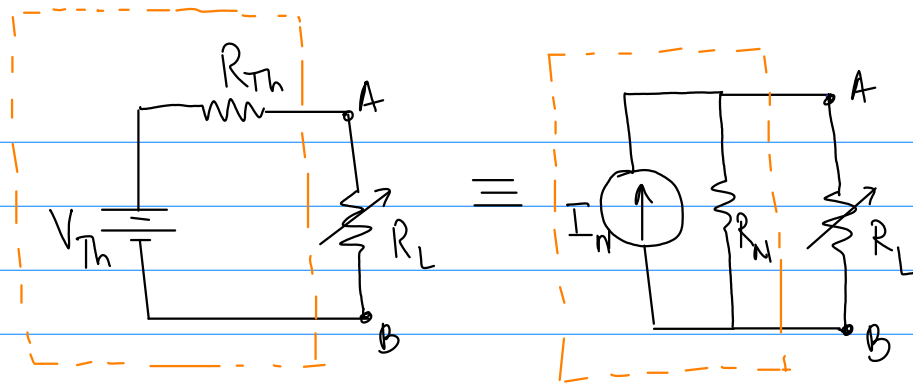

Thevenin's voltage $V_{Th} = V_{oc}$ (open ckt. voltage)

Norton's Current $I_N = I_{sc}$ (short ckt. current)

Example:

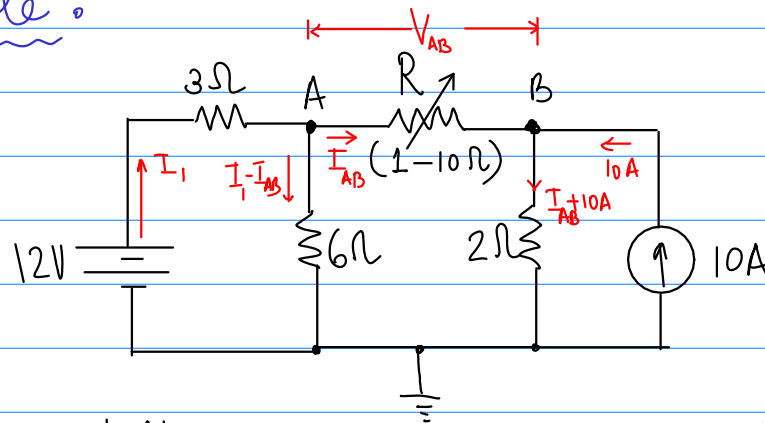


Fill this table :

$$V_{AB} = \left(\frac{R}{R+4\Omega} \right) 12V$$

$$I_{AB} = \frac{12V}{R+4\Omega}$$

R (in Ω)	V_{AB} (in V)	I_{AB} (in A)
1 Ω	2.4 V	2.4 A
2 Ω	4.0 V	2.0 A
3 Ω	\vdots	\vdots
4 Ω	\vdots	\vdots
\vdots	\vdots	\vdots
10 Ω		

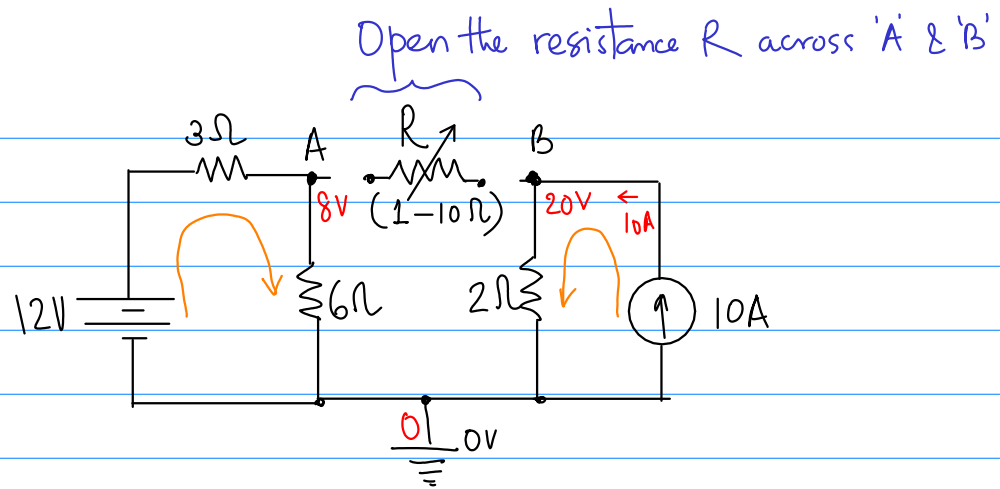Here we make use of Thevenin's theorem :
ie Thevenize the ckt. across the terminals A & B



$$V_{AB} (\text{open ckt.}) = V_A - V_B$$

$$V_B = 2\Omega \cdot 10A = 20V$$


$$V_A = \frac{6\Omega}{3\Omega + 6\Omega} \cdot 12V = 8V$$

$$V_{AB} = V_A - V_B = 8V - 20V = -12V$$

$$V_{Th} = V_{AB} = -12V$$

Determination of R_{Th} :

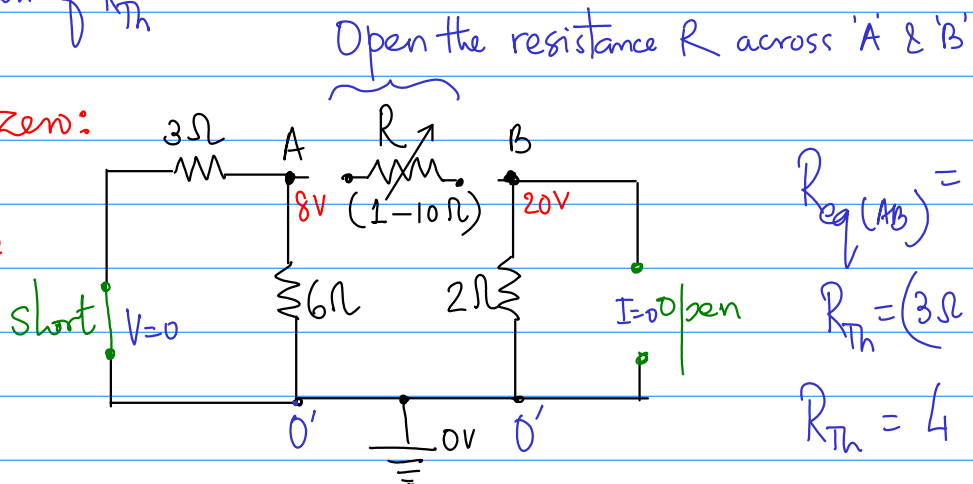
- To make the source zero:
- short voltage source
 - open current source



$$R_{eq(AB)} = R_{Th}$$


$$R_{Th} = (3\Omega \parallel 6\Omega) + 2\Omega$$

$$R_{Th} = 4\Omega$$

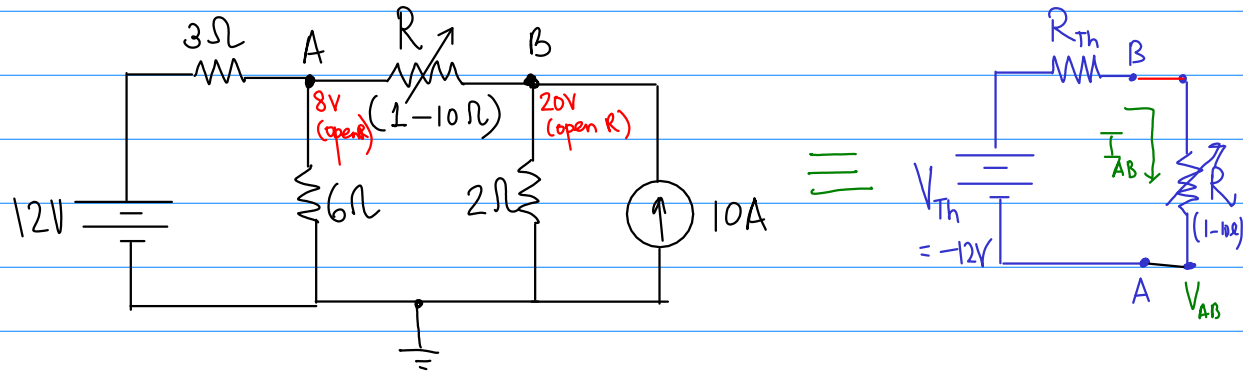


$$I_{AB} = \frac{V_{Th}}{R_{Th} + R} = \frac{12V}{4\Omega + R}$$
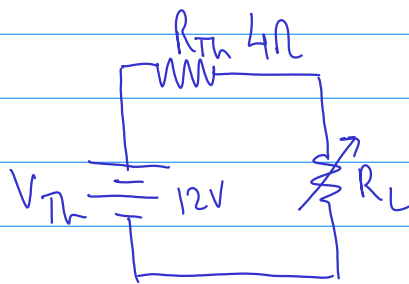
$$V_{AB} = I_{AB} \cdot R = \left[\frac{12V}{4\Omega + R} \right] \cdot R$$



\equiv

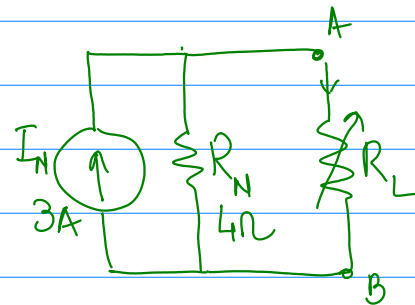


$$I_{AB} =$$

$$V_{AB} =$$

$$I_N = I_{sc} = \frac{V_{Th}}{R_{Th}} = \frac{12V}{4\Omega} = 3A$$


Semiconductors

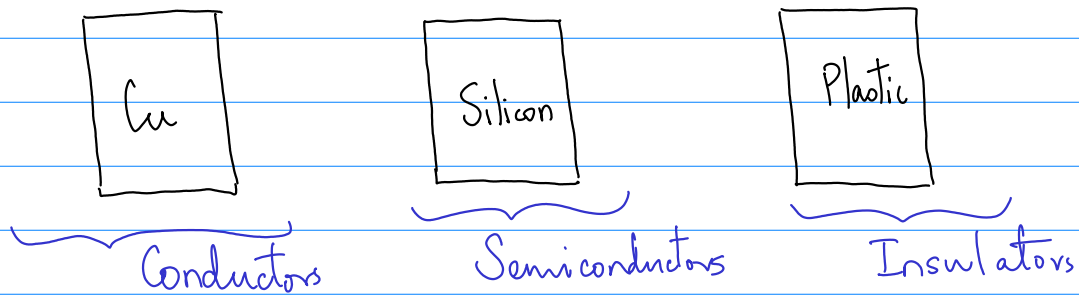

In terms of Energy gap : $E_g(\text{semiconductors}) \sim 1-3 \text{ eV}$ (typical)

$E_g(\text{Insulators}) \sim > 3 \text{ eV}$ (typical)

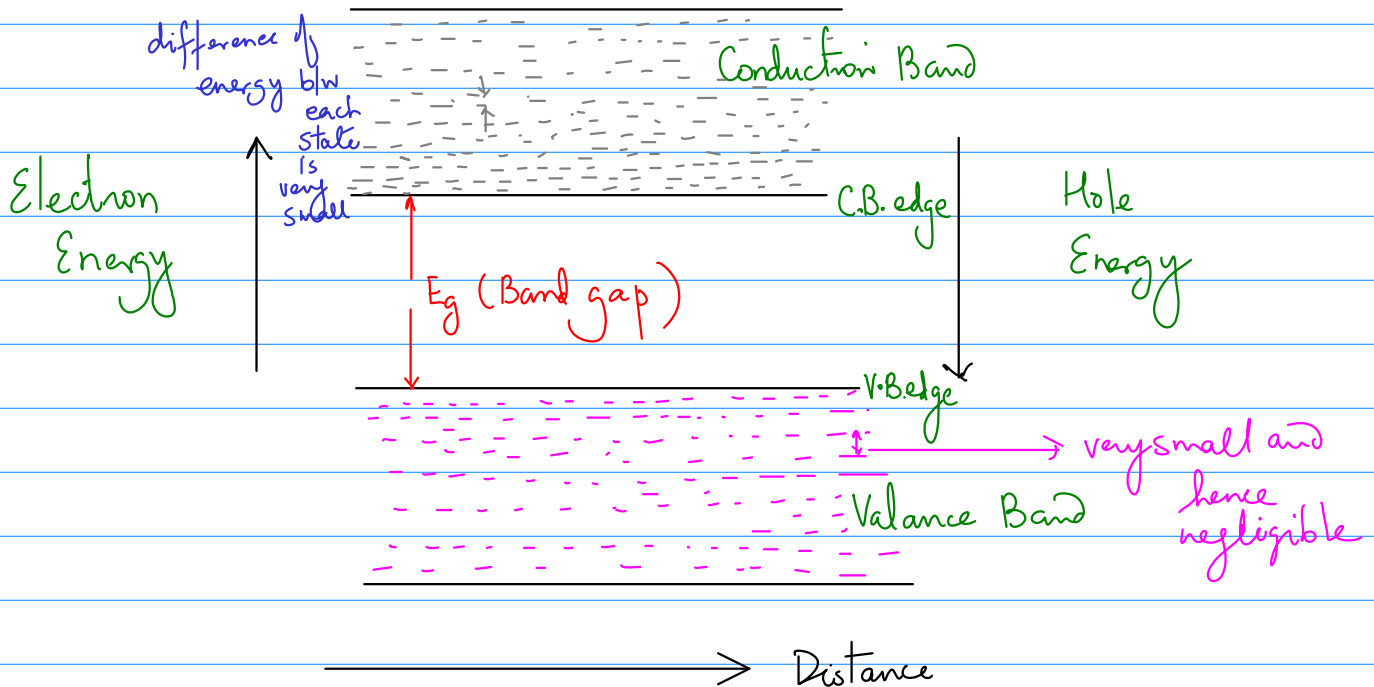Simplified Band Diagram of a Semiconductor:



In each energy band, we have discrete energy states, however, the ^{energy} separation b/w them is very small and hence assumed negligible. Therefore,

We visualize each band is having continuum energy states.

Typically, at room temperature (300K)

$$E_g(\text{Silicon}) = 1.12 \text{ eV}$$

$$E_g(\text{Ge}) = 0.66 \text{ eV}$$

$$E_g(\text{GaAs}) = 1.42 \text{ eV}$$


Band gap depends on temperature

$$E_g(T) = E_g(0) - \frac{\alpha T^2}{(T + \beta)}$$

where $E_g(0)$ = Band gap at $T = 0 \text{ K}$


α, β are the parameters

T = temperature in Kelvin.

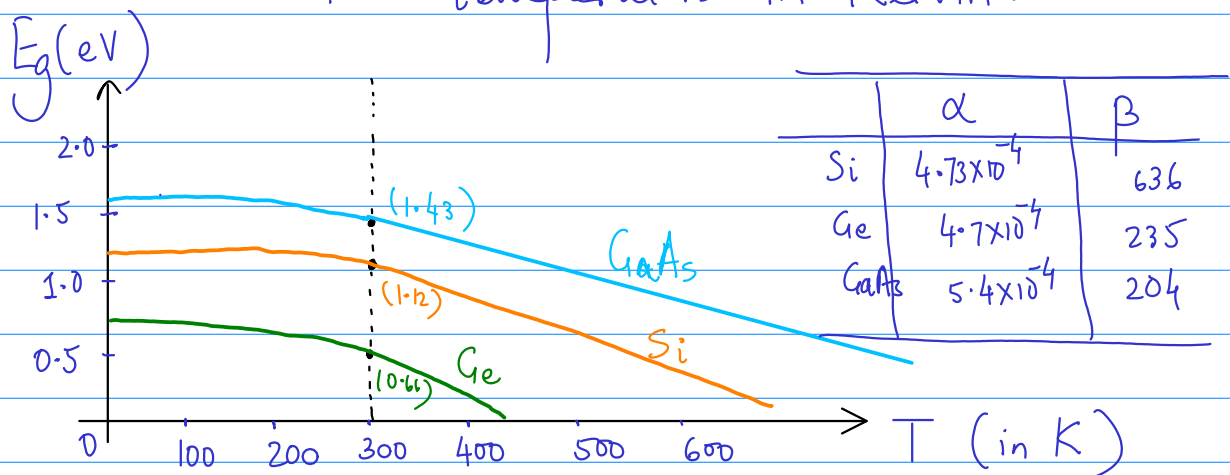


Charge-carrier density in Conductors, Semiconductors & Insulation.

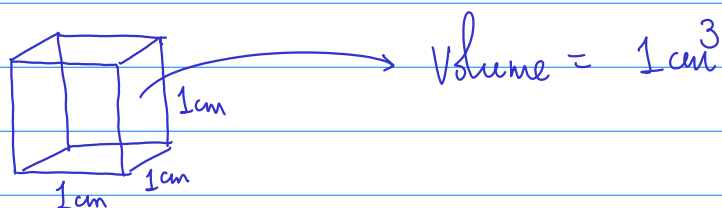
Charge-carrier density \equiv No. of electrons/holes per unit volume (cm^{-3})




In any solid; atomic density $\sim 10^{22} \text{ cm}^{-3}$

Let take specific example:

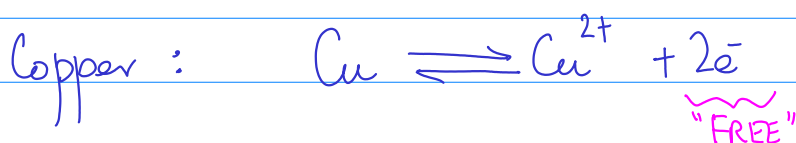

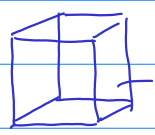 $1 \text{ cm}^3 \equiv 10^{22} \text{ atoms} = 2 \times 10^{22} \text{ electrons}$
"FREE"

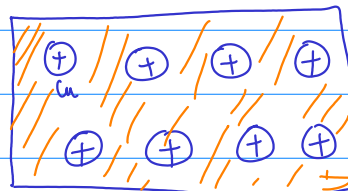
In metals (conductors), we have $\sim 10^{22}$ "FREE" electrons cm^{-3} which are available for the conduction of electrical energy.



Drude's Model

Sea of "FREE" charge carriers

What about semiconductors? (say silicon)

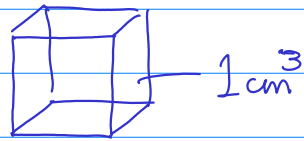


$$\# \text{ atoms} = 10^{22}$$

at $T = 0\text{K}$; "FREE" electrons/holes $\approx 0 \text{ cm}^{-3}$

at $T = 300\text{K}$ (RT) "FREE" electron/holes $\sim 10^{10} \text{ cm}^{-3}$

Thermal Energy at RT $= k_B T \approx 25 \text{ meV}$

Insulators :

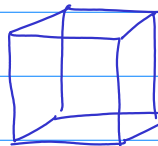

1 cm^3 atom $\sim 10^{22}$

at RT (300K); "FREE" electron $\ll 10^5 \text{ cm}^{-3}$