

## Tutorial #07

### Junction Field Effect Transistors.

- Q1. The device parameters of n-channel JFETs are :

$$I_{DSS} = 10 \text{ mA} ; V_{P_{\text{pinch-off}}} = 4.0 \text{ V}$$

Calculate the drain current  $I_D$  for  $V_{GS} = 0 \text{ V}$  ;  $-1.0 \text{ V}$  and  $-4.0 \text{ V}$

- Q2. A JFET produces gate current of  $2 \text{ nA}$  when gate is reverse biased with  $8 \text{ V}$ . Determine the resistance between gate and source.

- Q3. A JFET is self biased with  $V_{DD} = 20 \text{ V}$  and  $I_{DSS} = 12 \text{ mA}$ . The value of drain - and gate - resistance is  $2 \text{ k}\Omega$  and  $1 \text{ M}\Omega$  respectively. Determine the value of source-resistance for which the operating point lies at the middle of the load-line.

- Q4. Determine the operating point corresponding to the voltage-divider biased circuit shown below :

