

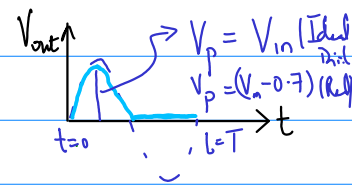
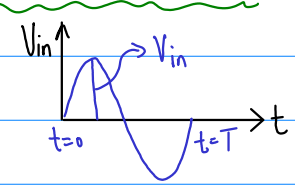


# Rectifier and Filter Circuits


Recap: Half-wave rectifier circuit

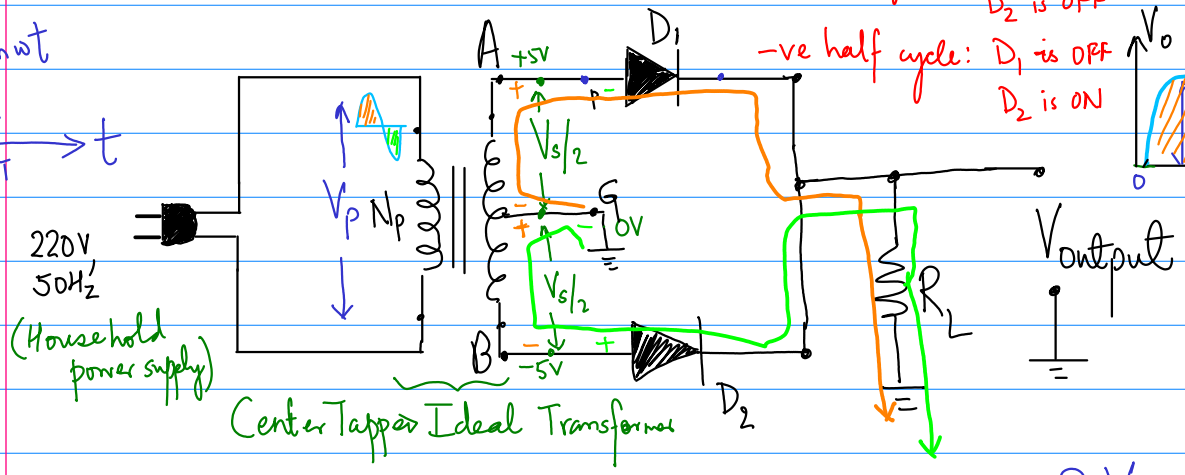

Full wave rectifier circuit:

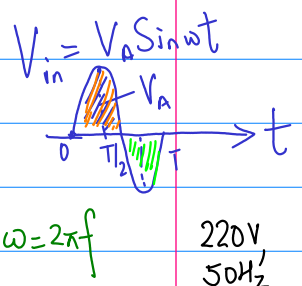

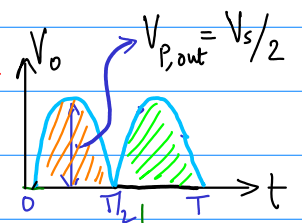+ve half cycle:  $D_1$  is ON  
 $D_2$  is OFF  
-ve half cycle:  $D_1$  is OFF  
 $D_2$  is ON



Observe in Scope/simulator

$$V_{p,out} = V_s/2 \quad ; \quad V_{ave} = \frac{2 V_{p,out}}{\pi} = \frac{2 \cdot V_s/2}{\pi}$$




Ideal Diodes

For practical diode;

$$V_{p,out} = \left( \frac{V_s}{2} - 0.7V \right)$$

$$\Rightarrow V_{ave} = \frac{2 V_{p,out}}{\pi} = \frac{2}{\pi} \left( \frac{V_s}{2} - 0.7V \right)$$

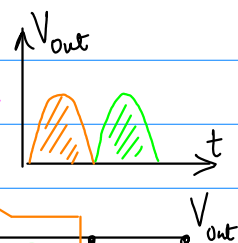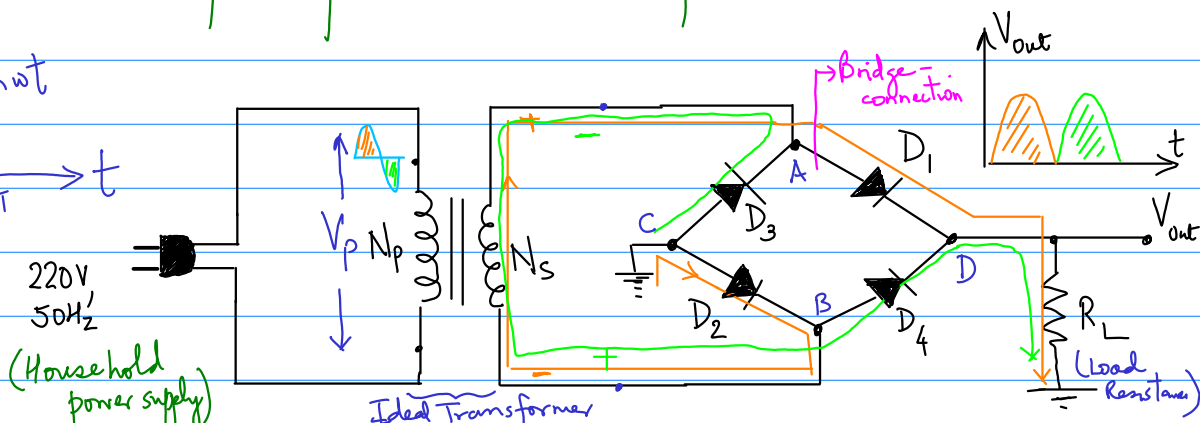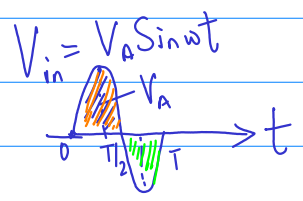Alternate circuit for full-wave rectifier:



for +ve half cycle:  $D_1$  &  $D_2$  - ON ;  $D_3$  &  $D_4$  - OFF

for -ve half cycle:  $D_3$  &  $D_4$  - ON ;  $D_1$  &  $D_2$  - OFF

As a result, we observed time-varying output voltage across the  $R_L$ .

$$V_s = n V_p = n V_A$$

$$V_{out} = V_s \quad (\text{considering diodes to be Ideal})$$

$$V_{ave.} = \frac{2 V_{out}}{\pi}$$



For practical circuit:

$$V_{out} = V_s - 1.4 V$$

Since two diodes are replaced with two voltage sources of 0.7V each.

$$V_{ave} = \frac{2}{\pi} (V_s - 1.4 V)$$

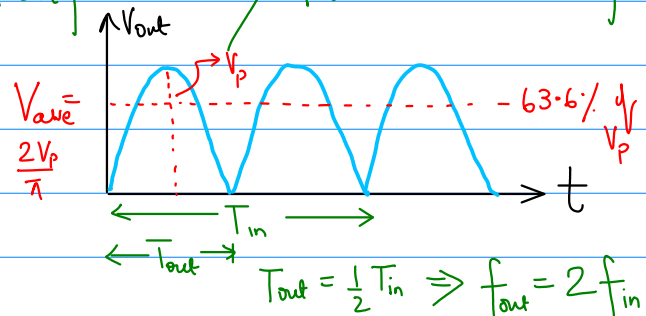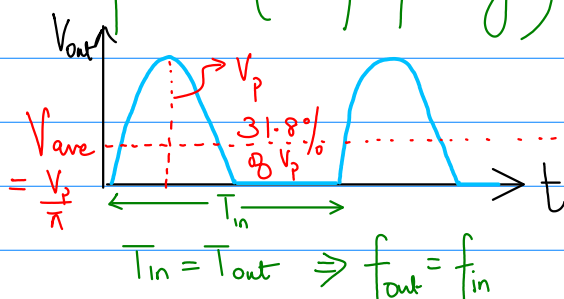Time-period (or frequency) of Half-wave / Full-wave rectifier




- For half-wave rectifier: Time-period of output voltage is same as

input voltage. That is, if input frequency is 50 Hz then output frequency is also 50 Hz.


- For full-wave rectifier, the time-period of output voltage is half of the input voltage. That is, the frequency of output voltage will be 100 Hz for 50 Hz input frequency.

Remember: Output of the rectifier ckt. is time-varying

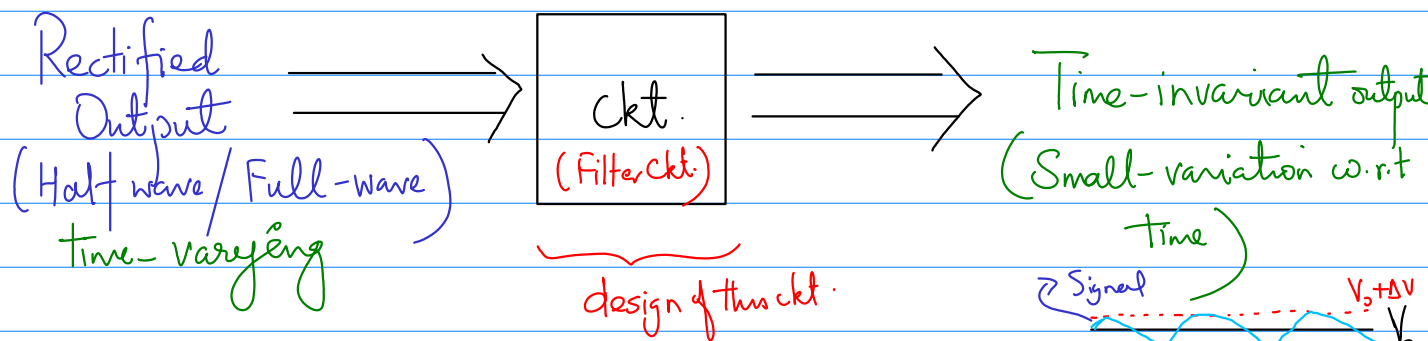⇒ To get time-invariant output, we need another circuit  
→ Filter circuit:




RC circuit: (a) charging

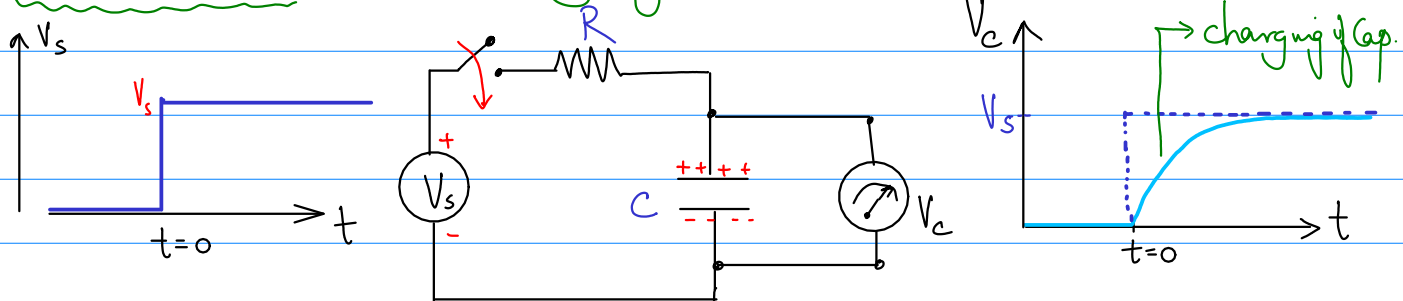

$$V_c(t) = V_s (1 - e^{-t/\tau})$$

Time constant:  $\tau = RC$  ;  $t = 5\tau$  ;  $V_c(t) \approx V_s$



## b) Discharging :

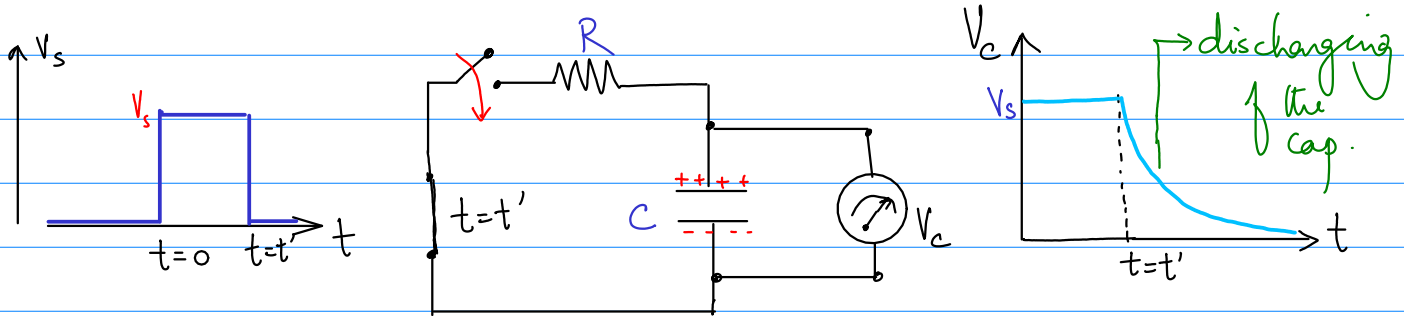

$$V_c(t) = V_s e^{-t/\tau}$$


$$\tau = RC$$

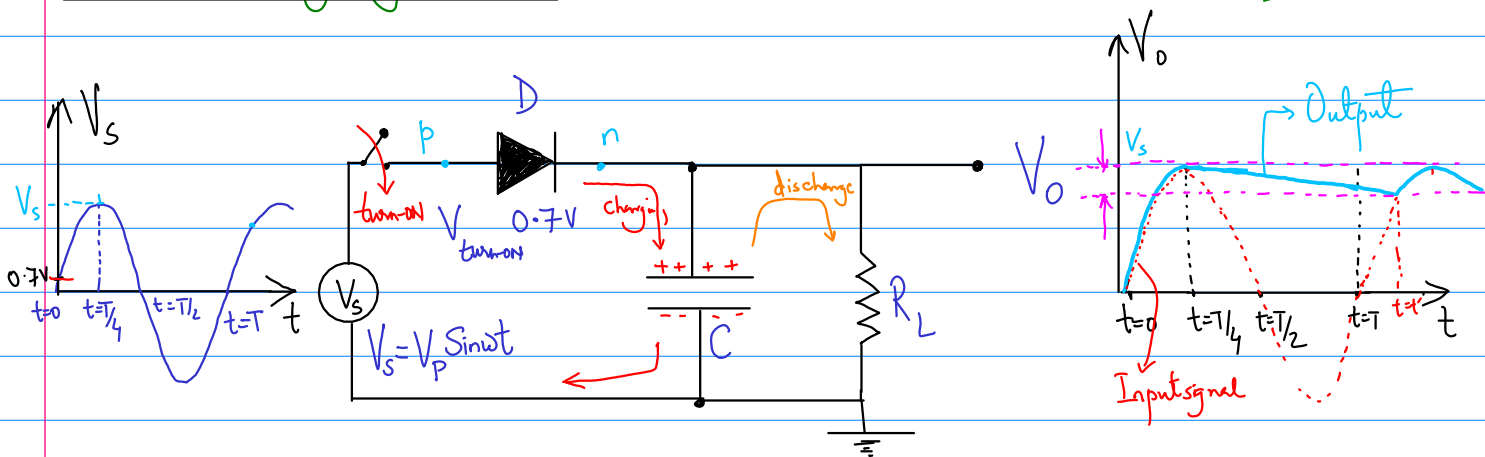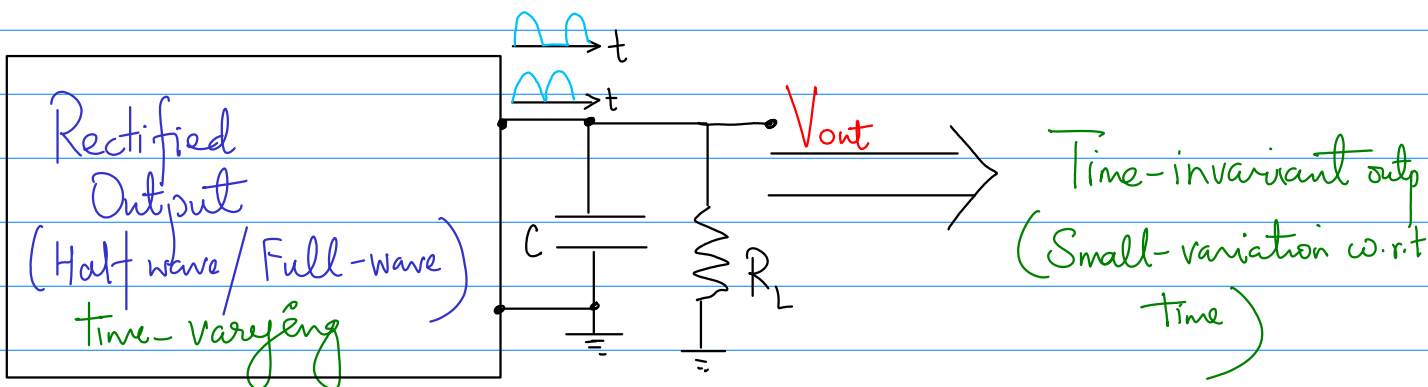When  $t = 5\tau$ , then  $V_c \approx 0$



at  $t = T/4$  and beyond : p-side becomes negative w.r.t n-side  
 $\Rightarrow$  the diode goes into <sup>the</sup> reverse bias cond<sup>n</sup>.  
 i.e., the <sup>input</sup>ckt. is "OPEN".

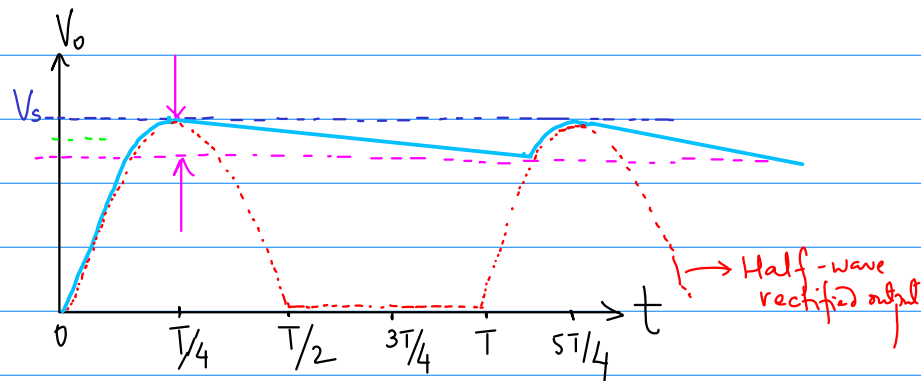In half-wave rectifier with filter circuit, we get the following output :



In full-wave rectifier with filter circuit, we get the following output :

