


Op-Amp. : Negative Feedback

Recap: (i) Ideal & Practical Op-Amp. Parameters



(ii) Differential & Common mode Operation

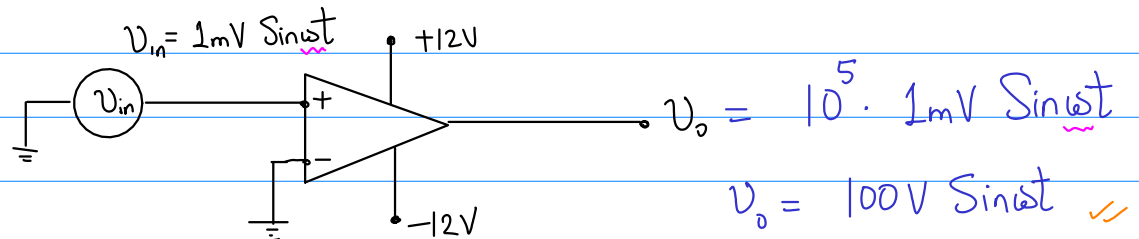(iii) Inverting Op-Amp. $(A_{CL(IN)} = -\frac{R_2}{R_1})$
Tune the gain as per the choice of the external resistors R_1 & R_2

Q: Let's understand what will happen when we connect the ckt. as per the following:



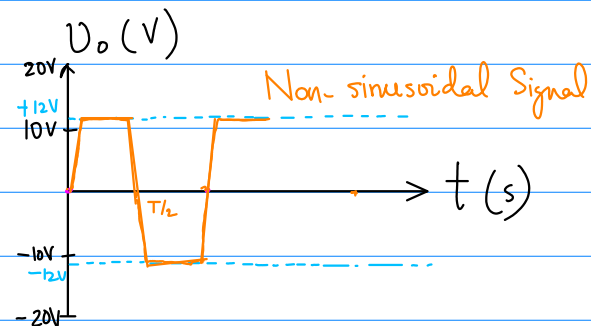
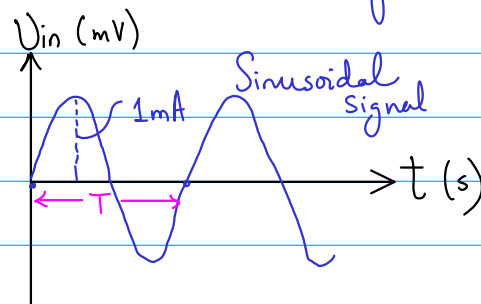
Assuming practical value of $A_{OL} = 10^5$



Negative Feedback:

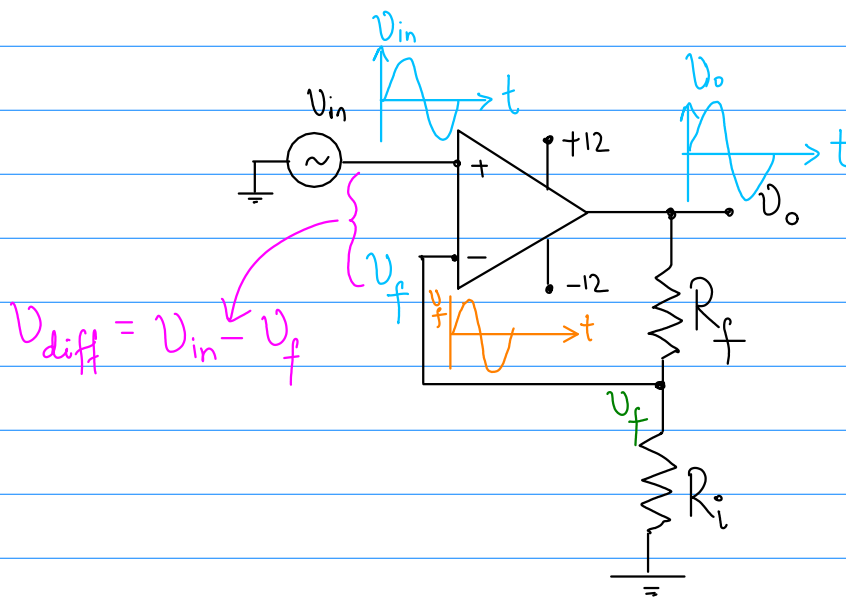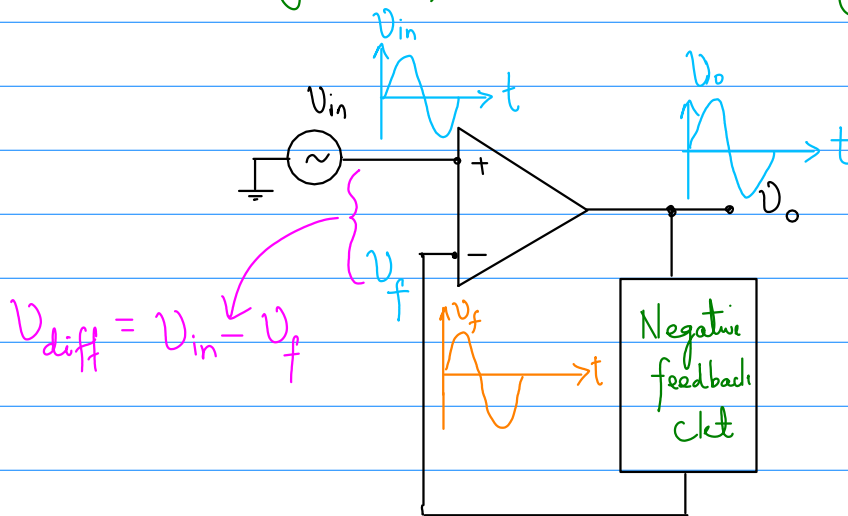1. Tune the gain of the op-amp with help of external ckt. element (Resistor).
2. By tuning the gain, we can restrict the op-amp to operate in linear regime. (Not to go into saturation regime).

Non-inverting Amp. ckt. with negative feedback:



$$V_f = \frac{R_i}{R_i + R_f} V_o$$

$$V_f = B V_o$$

$$\text{where } B = \frac{R_i}{R_i + R_f}$$

Now, with the negative feedback ckt, the op-amp have effective differential input voltage;

$$V_{\text{diff (input)}} = \underbrace{V_{\text{in}}}_{\text{applied to NI input}} - \underbrace{V_f}_{\text{applied to inverting input}}$$

$$V_{\text{diff (input)}} = V_{\text{in}} - BV_o \quad \text{where } B = \frac{R_i}{R_i + R_f}$$

If we have open-loop gain A_{OL}

$$V_o = A_{OL} \cdot V_{\text{diff (input)}} \quad \text{where } A_{OL} = \text{Open-loop gain.}$$

$$\Rightarrow V_o = A_{OL} \cdot (V_{\text{in}} - BV_o)$$

$$\Rightarrow V_o + A_{OL} \cdot B \cdot V_o = A_{OL} \cdot V_{\text{in}}$$

$$\Rightarrow V_o (1 + A_{OL} \cdot B) = A_{OL} \cdot V_{\text{in}}$$

$$\Rightarrow \frac{V_o}{V_{\text{in}}} = \frac{A_{OL}}{1 + A_{OL} \cdot B}$$

$$\Rightarrow A_{CL(NI)} = \frac{V_o}{V_{\text{in}}} = \frac{A_{OL}}{1 + A_{OL} \cdot B}$$

$$\Rightarrow \boxed{A_{CL(NF)} = \frac{A_{OL}}{1 + A_{OL} \cdot B}}$$

As we know; $A_{OL} \sim 10^4 - 10^6$ & $B = \frac{R_i}{R_i + R_f}$

the product $A_{OL} \cdot B \gg 1$

Under this condⁿ:

$$A_{CL(NI)} = \frac{A_{OL}}{A_{OL} \cdot B}$$

$$\Rightarrow A_{CL(NI)} = \frac{1}{B} = \frac{R_i + R_f}{R_i}$$

$$\Rightarrow A_{CL(NI)} = 1 + \frac{R_f}{R_i} \quad \text{under the cond}^n \quad A_{OL} \cdot B \gg 1$$

Conclusion: • Closed loop gain is independent of the value of the open loop gain.

OR


Closed loop gain is dependant on the external ckt element. (R_i & R_f)

	VOLTAGE GAIN	INPUT Z	OUTPUT Z	BANDWIDTH
1.) Without negative feedback	A_{OL} is too high for <u>linear</u> amplifier applications $10^4 - 10^6$	Relatively high (see Table 12-1) $\sim M\Omega$	Relatively low $\sim \text{few } \Omega$	Relatively narrow (because the gain is so high) 1Hz
2.) With negative feedback	A_{CL} is set to desired value by the feedback circuit (R_i & R_f) dependent	Can be increased or reduced to a desired value depending on type of circuit (R_i & R_f) dependent	Can be reduced to a desired value (R_i & R_f) dependent	Significantly wider dependent

Voltage-Follower ckt :

High-impedance Source \longrightarrow Low-impedance load.

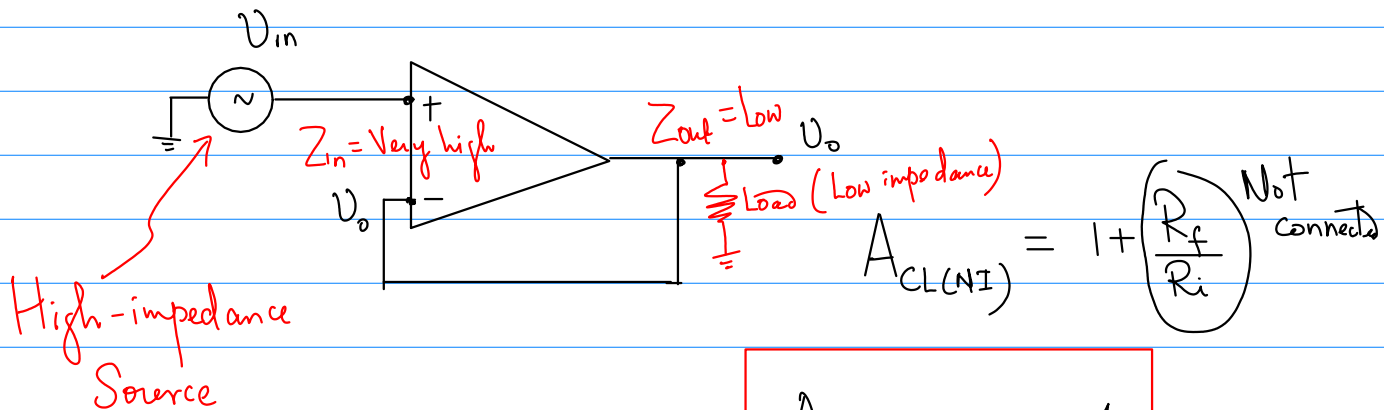\Rightarrow in voltage-follower ckt : $A_V = 1$ (unity)



$$A_{CL(NI)} \approx 1$$