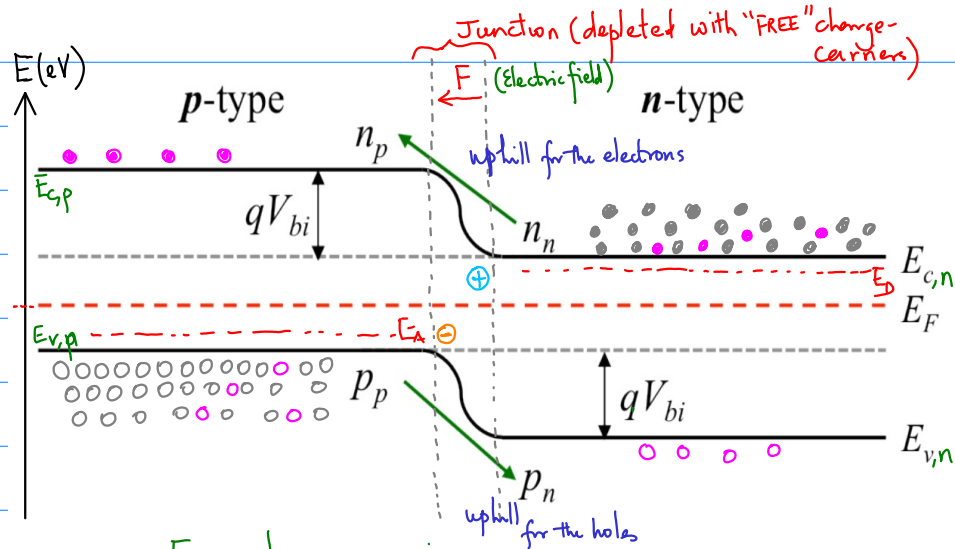


p-n Homojunction Diode

1. Unbiased at 300K.



Dopants:

\oplus : Donor atoms

\ominus : Acceptor atoms

Bound charges within the junction region

$$n_n \approx N_D \approx 10^{15} \text{ cm}^{-3}$$

$$p_p \approx N_A \approx 10^{15} \text{ cm}^{-3}$$

$$n_p \approx 10^5 \text{ cm}^{-3}$$

$$p_n \approx 10^5 \text{ cm}^{-3}$$

Majority carriers
"Extrinsic" source

Minority carriers
"Intrinsic" carriers

Free charge-carriers:

$\bullet \equiv$ Electrons from the donor atoms

$\circ \equiv$ Holes from the acceptor atoms

$\bullet \equiv$ Electrons due to excitation

$\circ \equiv$ Holes due to excitation of electrons

PARTICLE FLOW

Hole diffusion

$p \rightarrow n$

Hole drift

$p \leftarrow n$

Electron diffusion

$p \leftarrow n$

Electron drift

$p \rightarrow n$

CURRENT


$I_p(\text{Diffusion})$

$I_p(\text{Drift})$

$I_n(\text{diffusion})$

$I_n(\text{drift})$

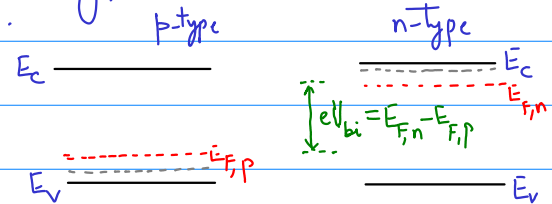Built-in voltage V_{bi} is simply the difference of the Fermi-levels in p- and n-type semiconductors before they are joined.




$$I_{NET} = 0$$

$$\Rightarrow qV_{bi} = E_{F,n} - E_{F,p}$$

at any temperature T ,

$$E_{F,n} = E_{F,i} + k_B T \ln\left(\frac{N_D}{n_i}\right) \quad \uparrow \text{Towards } E_c$$
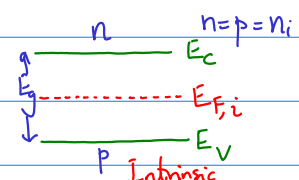
$$E_{F,p} = E_{F,i} - k_B T \ln\left(\frac{N_A}{n_i}\right) \quad \downarrow \text{Towards } E_v$$



Subtract the two, we get

$$V_{bi} = \frac{k_B T}{q} \ln \left(\frac{N_A \cdot N_D}{n_i^2} \right)$$

Let's estimate
for Silicon:
 $T = 300K$
 $\frac{k_B T}{q} = 25mV$
 $N_A = N_D = 10^{15} cm^{-3}$
 $n_i = 10^{10} cm^{-3}$
 $V_{bi} = 25mV \ln \left(\frac{10^{15}}{10^{10}} \right)$
 $V_{bi} = 0.6V$


In steady-state,

Diffusion current = Drift current



\Rightarrow Net current is "ZERO"

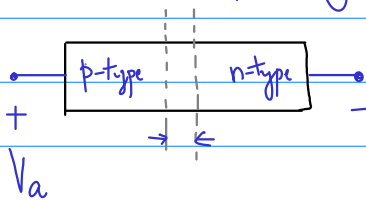2. Biased at 300K.

p-type = +ve terminal of the source
 \rightarrow forward bias p-n junction



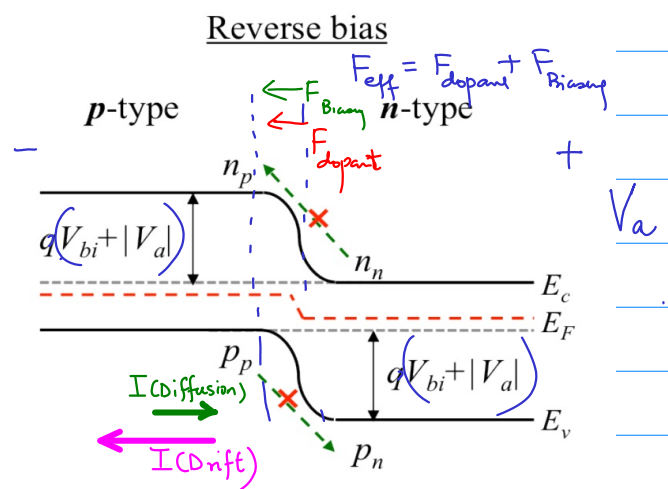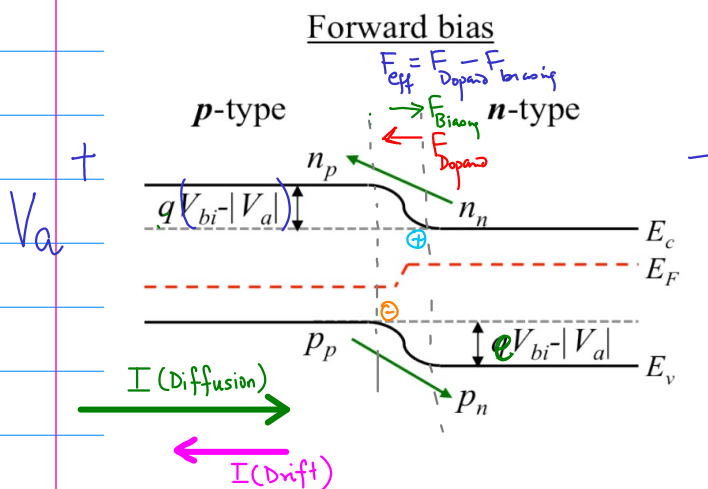= -ve terminal of the source
 \rightarrow Reverse bias p-n junction.




Current-Voltage Characteristics :


$$I(V, T) = I_s \left[\exp\left(\frac{qV}{\eta k_B T}\right) - 1 \right]$$

where, I_s = Reverse saturation current

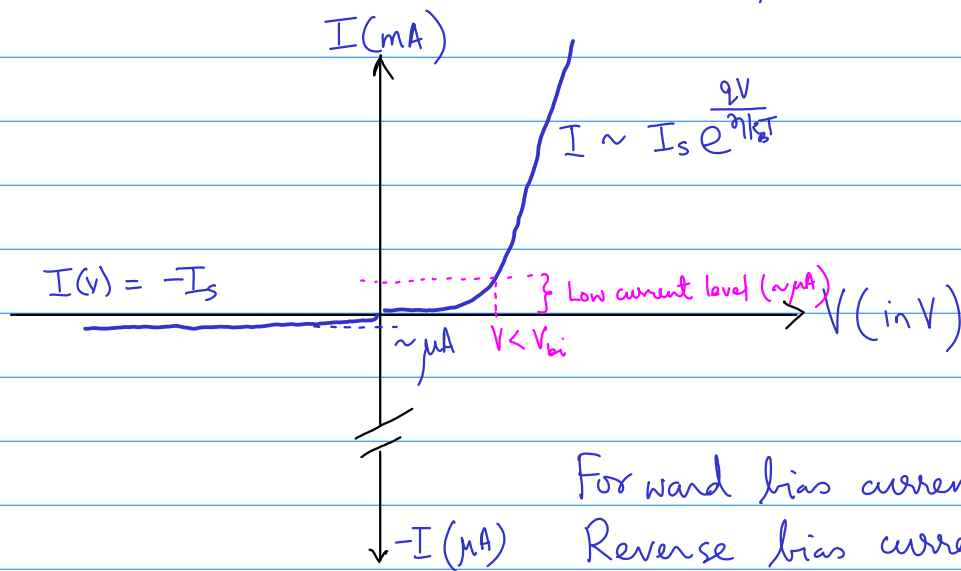η = Ideality factor ; for ideal diode ; $\eta = 1$
for real diode ; $1 < \eta < 2$




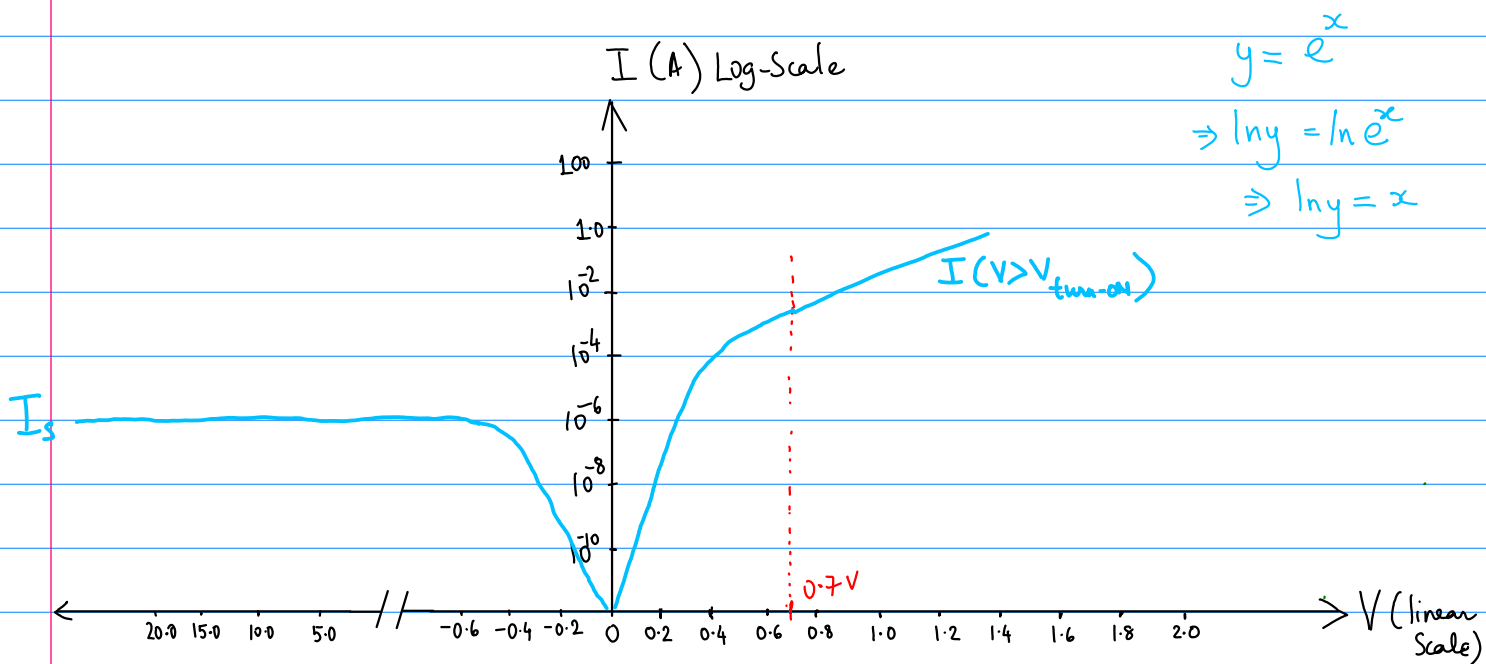Forward bias current $\sim \text{mA}$
Reverse bias current $\sim \mu\text{A}$



p-n Diode : Circuit Models

1. Current-Voltage Characteristics:

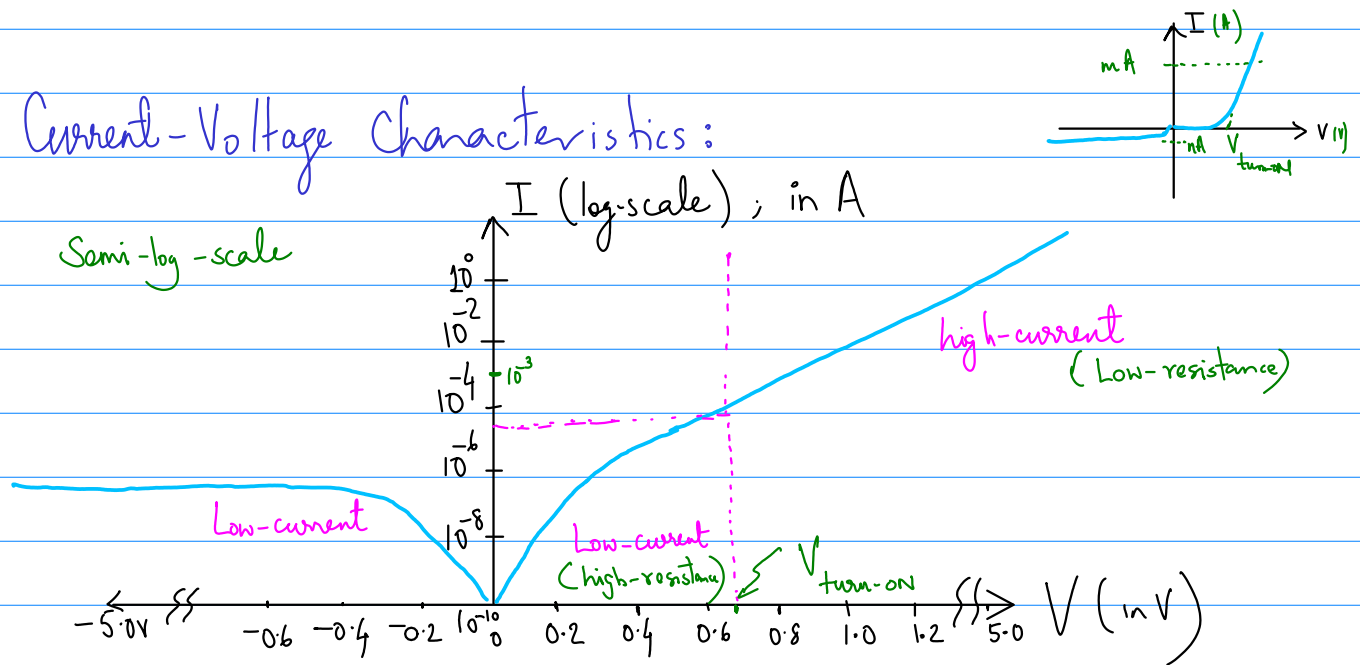


Conclusion: The current-voltage characteristics show two current levels:

(i) Low (nA) when $V \leq V_{turn-on}$

(ii) high (mA) when $V > V_{turn-on}$.


2) Circuit Model of a p-n diode:

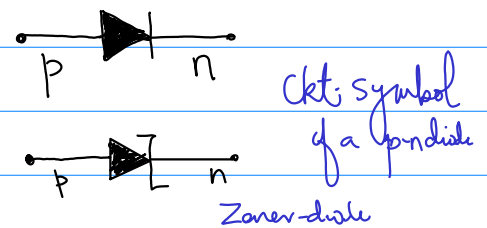

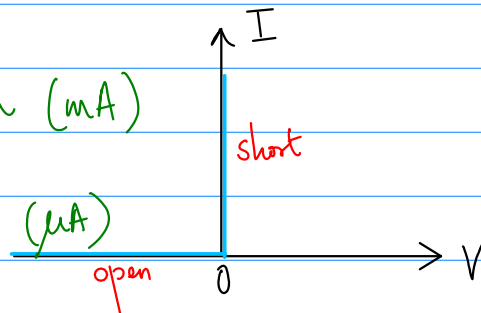
a) Ideal diode Model :

(+ve Bias) $V > 0$; $I \rightarrow$ high (mA)


(-ve Bias) $V < 0$; $I \rightarrow$ Low (μA)



(i) Forward bias

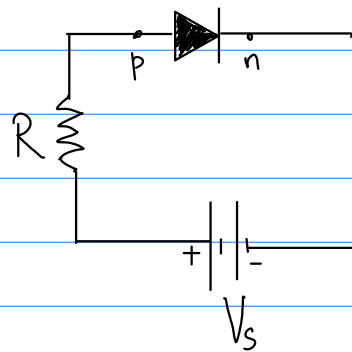


\equiv

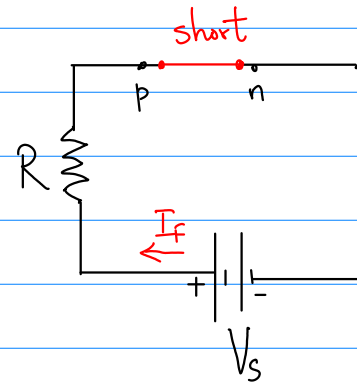


$$I_F = \frac{V_s}{R}$$

(ii) Reverse-bias:

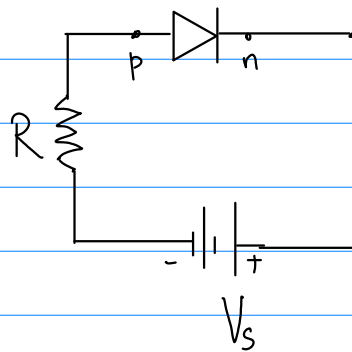


\equiv

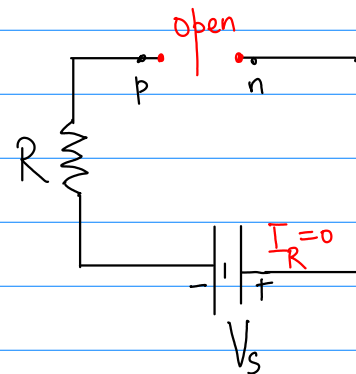


$$I_R = 0$$

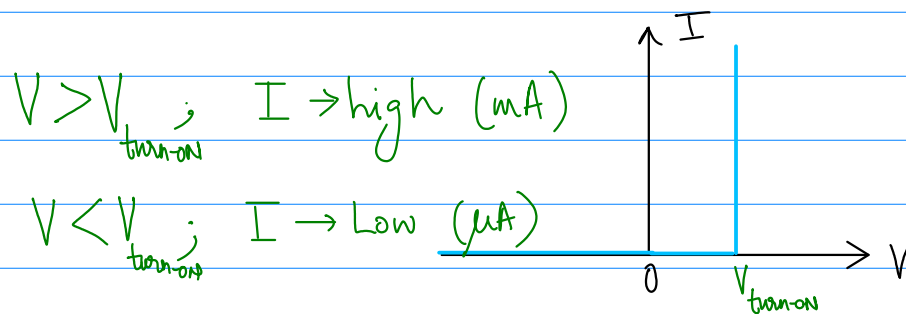b) Modified Ideal Diode Model (Practical Model):




(i) Forward bias

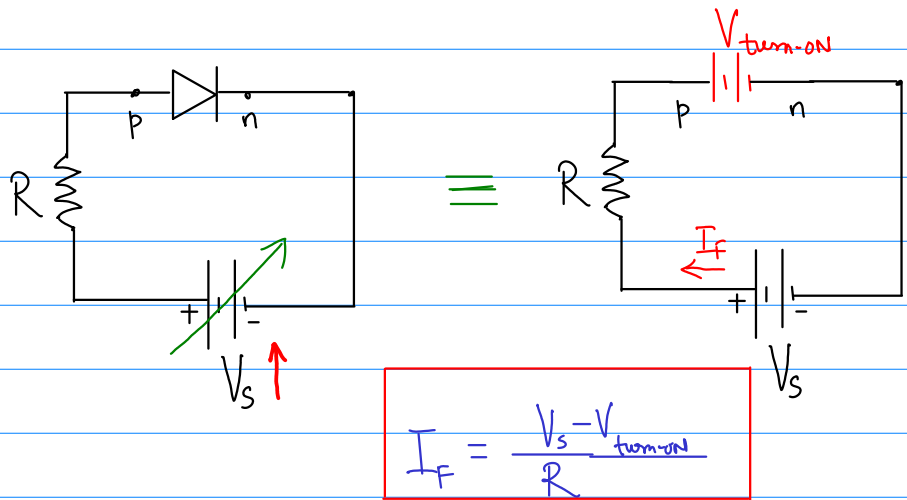



typically, for Silicon diode, $V_{\text{turn-on}} \sim 0.7V$

$$I_F = \frac{V_s - 0.7V}{R}$$


(ii) Reverse-bias:

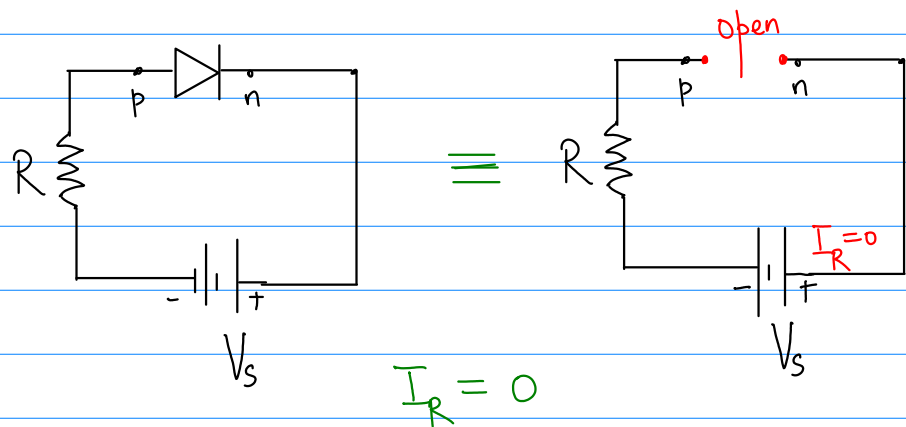


3) Complete (Real) diode Model :

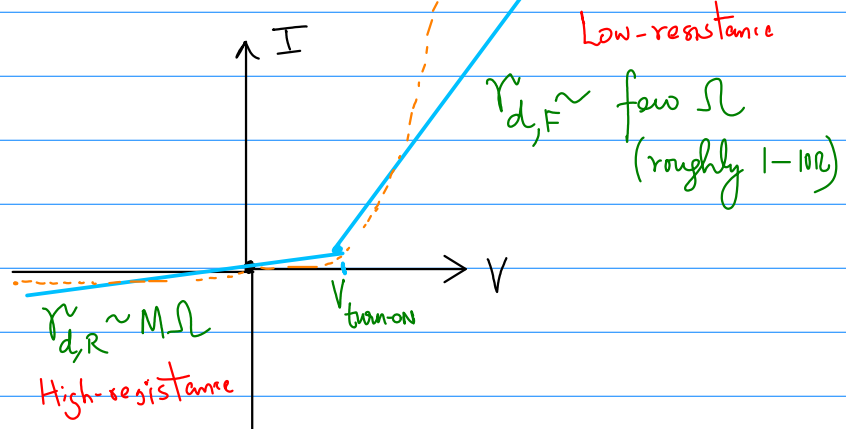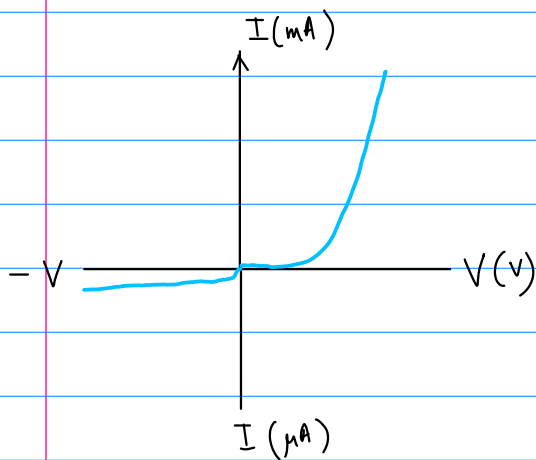

(i) Forward bias

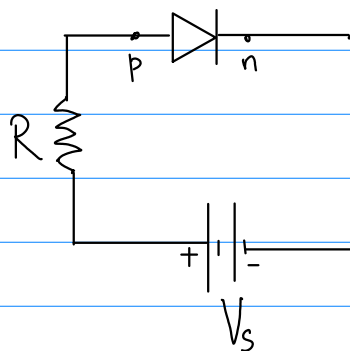


\equiv

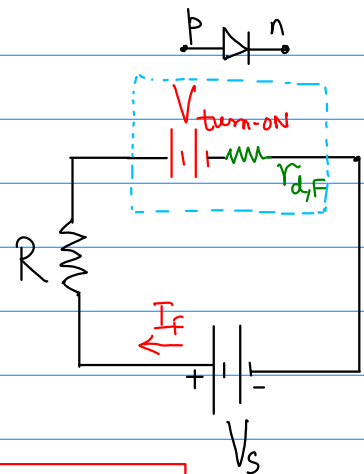


$$I_F = \frac{V_s - V_{\text{turn-on}}}{R + r_{d,F}}$$

(ii) Reverse-bias:

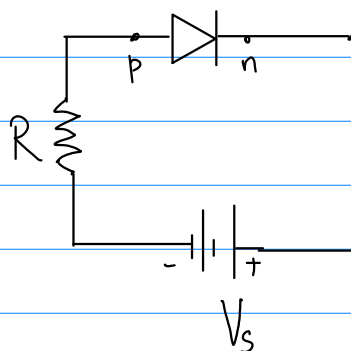

\equiv

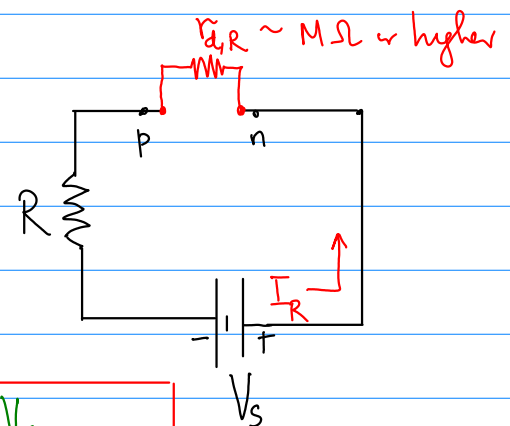

$$r_{d,R} \sim 1M\Omega$$


$$R = 1k\Omega$$

$$V_s = 1V$$

$$\Rightarrow I_R = \frac{1V}{1k\Omega + 1M\Omega} \approx 1\mu A$$

$$I_R = \frac{V_s}{R + r_{d,R}}$$

Example Problem:

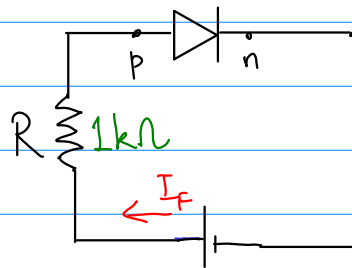

$$V_s = 10V$$

Specification of the diode

$$V_{\text{turn-on}} = 0.6V$$

$$r_{d,F} = 10\Omega$$

$$r_{d,R} = 100k\Omega$$

Let see forward-current (I_F) assuming the three models:

(i) Ideal model: Diode is replaced with "short".

$$I_F = \frac{V_s}{R} = \frac{10V}{1k\Omega} = \underline{10mA}$$


(ii) Modified Ideal Model: Diode is replaced with a "Voltage source" $= V_{\text{turn-on}}$

$$I_F = \frac{V_s - V_{\text{turn-on}}}{R} = \frac{10V - 0.6V}{1k\Omega} = \underline{9.4mA}$$

(iii) Real diode model: Diode is replaced with a voltage-source and a resistor $r_{d,F}$

$$I_F = \frac{V_s - V_{\text{turn-on}}}{R + r_{d,F}} = \frac{10V - 0.6V}{1k\Omega + 10\Omega}$$

$$I_F = \underline{9.3mA}$$

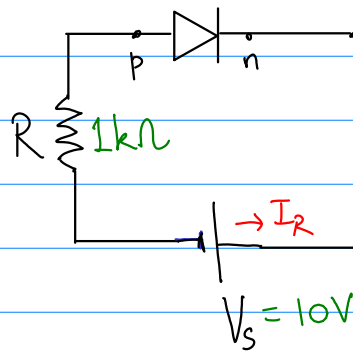

(i) Ideal Model : $I_R = 0$ (diode \equiv open)

(ii) M.I.M. : $I_R = 0$ (open)

(iii) Real Model :



Diode is replaced
with a resistor
' $r_{d,R}$ '

$$I_R = \frac{V_s}{R + r_{d,R}} = \frac{10V}{1k\Omega + 100k\Omega}$$

$$I_R = 100\mu A = 0.1mA$$

$$\frac{I_F}{I_R} = \frac{9.3mA}{0.1mA} \sim 93$$
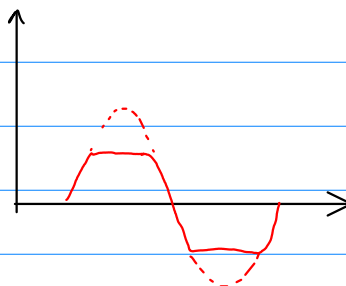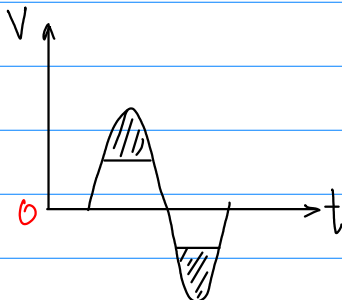
$$I_F = 93 I_R \quad \&, \quad I_F \sim 100 I_R$$



Applications.

- Switch
- Rectifier (Half wave Full wave)
- Clipper
- Clamper