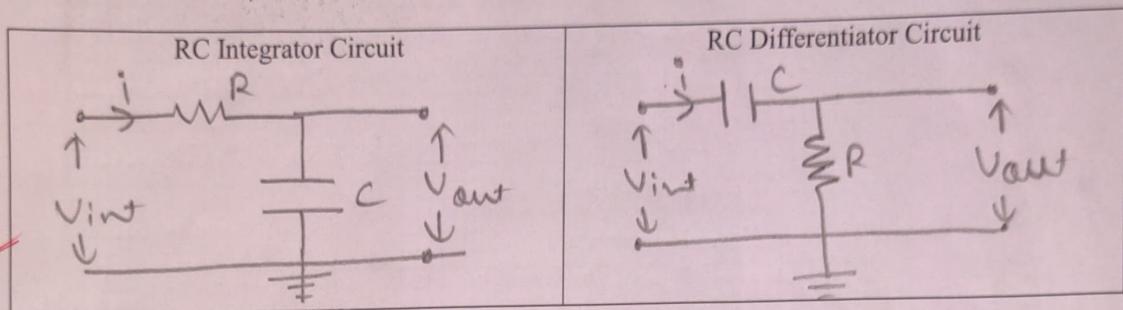


Laboratory Report (to be submitted on the same day)


Objective: Study of Time and Frequency response of RC circuit.


1. Circuit Diagram:



✓ 2. Chosen $R = 1000 \Omega$, $C = 10^{-4} \mu F$, τ (theoretical) = 10^{-4} sec

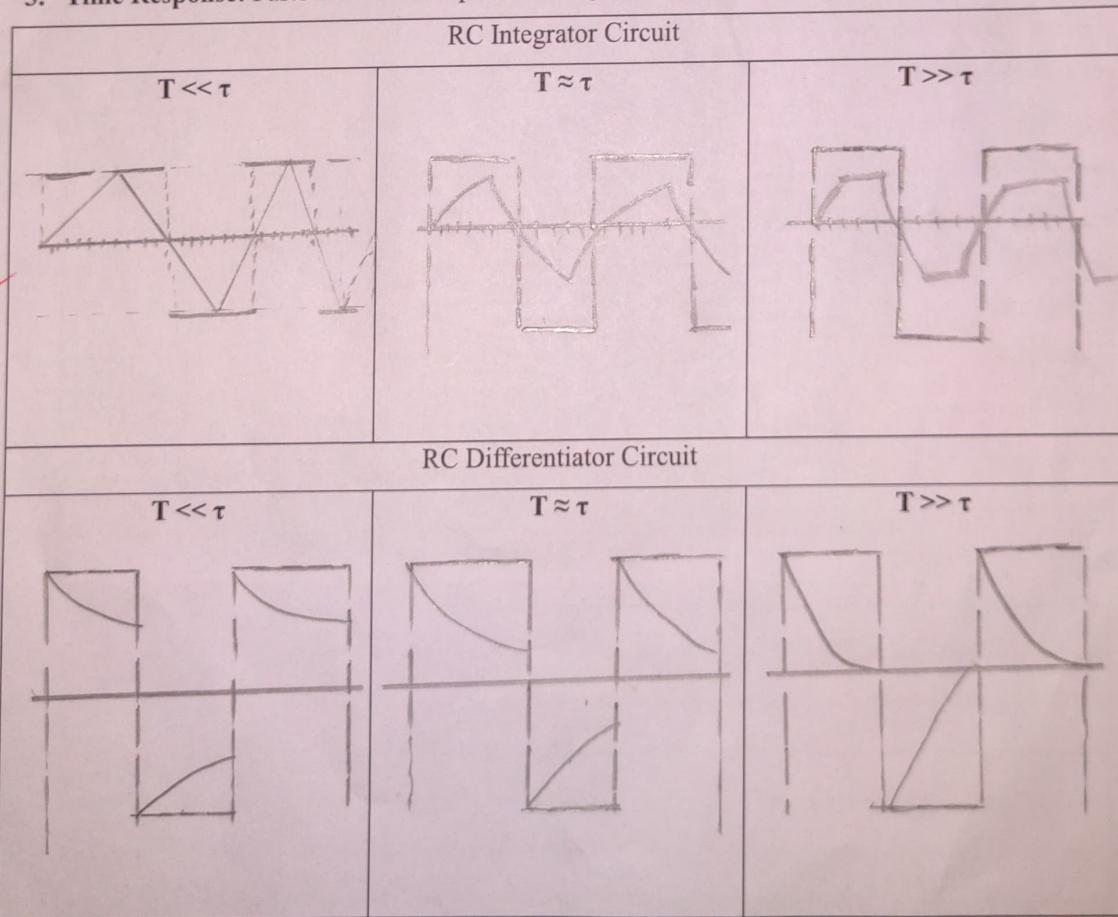3. Time Response: Paste the traced response for a given square wave of $\pm 5V$.



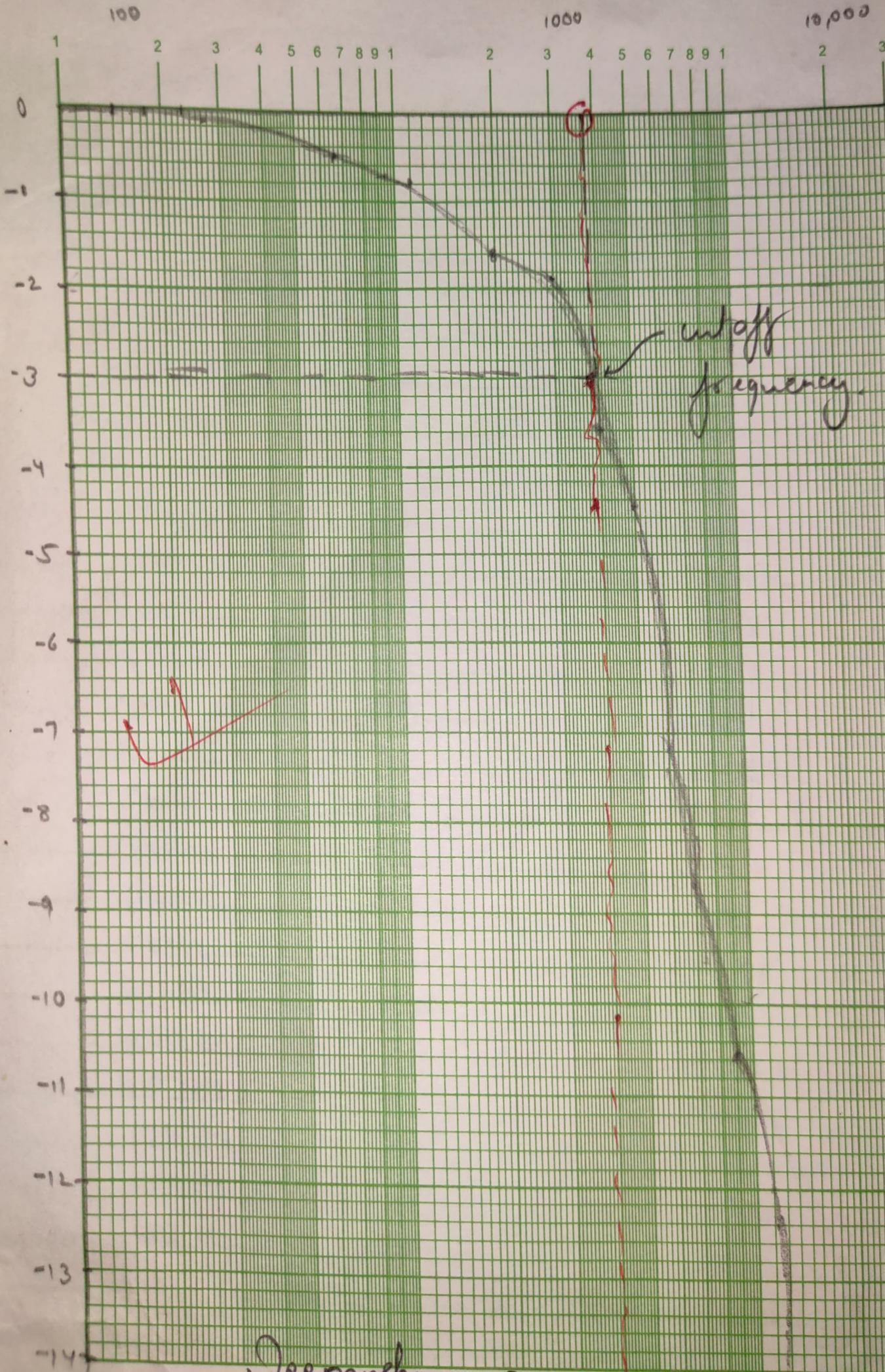

4. Frequency Response of low pass filter:

5. Plot Gain (in dB) vs Frequency: (Attach the plot drawn on semi-log graph paper)
6. Results: Discuss the results obtained in the experiment.

From this experiment, we find impedance ($X_C = \frac{1}{\omega C}$) not the voltage.

We analysed the frequency response of a low pass filter circuit with $1k\Omega$ resistance and $10^{-7}F$ capacitor. We get cut off frequency corresponding to -3dB voltage gain which is approximately 3.8 k Ω . The circuit is most efficient in this bandwidth.

Laboratory Report

Experiment-5: Study of Normal and Zener Diode Characteristics.

Code Number of Diode: (i) Normal Diode: 9.(IN4003) ✓ Resistance: 1K Ω
(ii) Zener Diode: 9.(IN4798A)

A. Table-I: For Normal Diode

Applied Voltage (in V)	Current (in mA)
0.1V	0
0.2V	0
0.4V	0.01
0.6V	0.14
0.8V	0.32
1.3V	0.77
1.8V	1.26
2.0V	1.49
2.2V	1.63
2.6V	2.07
3.3V	2.75
3.9V	3.30
4.4V	3.84
5.2V	4.65
5.8V	5.19
6.6V	6.08
7.8V	7.21
8.3V	7.81
9.0V	8.49
9.8V	9.34
10.5V	10.02
11.2V	10.77
11.8V	11.37
12.4V	12.01
12.8V	12.42
13.5V	13.12
14.2V	13.88
15.0V	14.62

B. Table-II: For Zener Diode

Applied Voltage (in V)	Current (in A)
Forward: 0V	0
0.4V	0
0.5V	0
0.6V	0.02
0.9V	0.17
1.3V	0.59
1.9V	1.07
2.4V	1.57
3.0V	2.19
3.8V	2.97
4.5V	3.58
5.2V	4.37
6.0V	5.29
6.6V	5.83
7.3V	6.49
7.9V	7.18

8.9V	8.17
9.08V	9.05
10.7V	9.91
11.5V	10.71
12.4V	11.67
13.5V	12.80
14.4V	13.73
15.0V	14.32.

Reverse bias:-

✓

1	0
2	0
3	0
4	0
5	0
6	0
6.8	0.01
7.4	0.13
7.9	0.58
8.4	1.04
9.0	1.62
9.7	2.04
10.7	2.34.
11.8	4.43
12.9	5.58
13.8	6.41
14.4	7.01
15.0	7.66.

Graphs: Plot I-V characteristics for both the diodes and estimate the required parameters.**Results: Table-III**

Threshold voltage of Normal Diode (in V)	0.4V ✓
Static resistance of Normal Diode (in Ω)	1.02 k Ω . ✓ 3
Dynamic resistance of Normal Diode (in Ω)	0.95 k Ω ✓
Threshold voltage of Zener diode (in V)	0.5V ✓
Zener breakdown voltage (in V)	8V ✓

$\uparrow I$


Normal

Diode:

Scale:

X-axis: 1V

Y-axis: 1mA

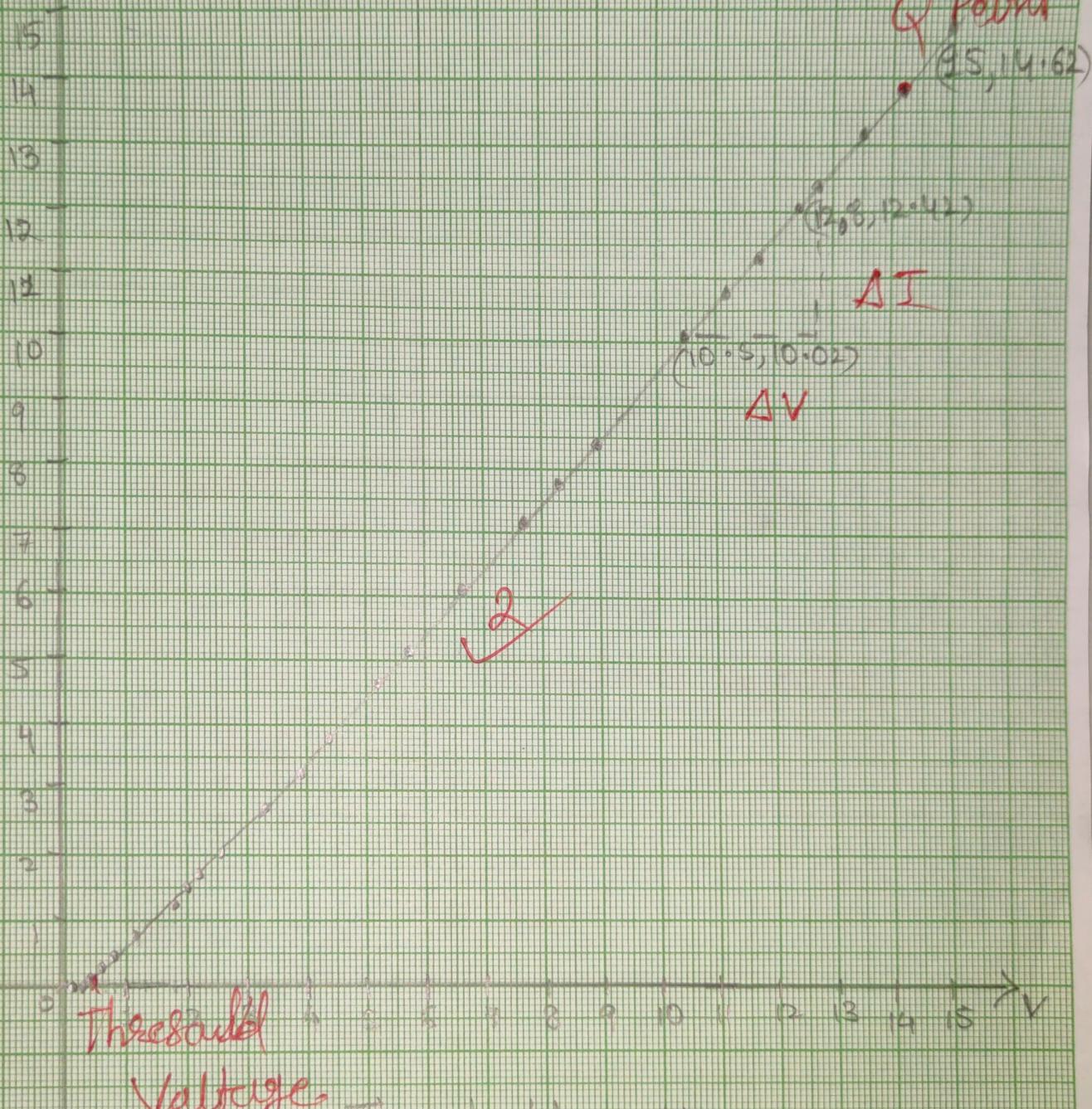

Threshold
Voltage


$$\text{Threshold} = 0.4\text{V}$$

$$\text{Step voltage} = \frac{15}{14.62\text{mA}} = 1.02\text{k}\Omega$$

$$\text{Dynamic } \alpha = \frac{12.8 - 10.5}{12.42 - 10.02} = \frac{2.3}{2.4} = 0.958\text{k}\Omega$$

Zener diode

Scale is
x-axis = 1V
y-axis = 1mA




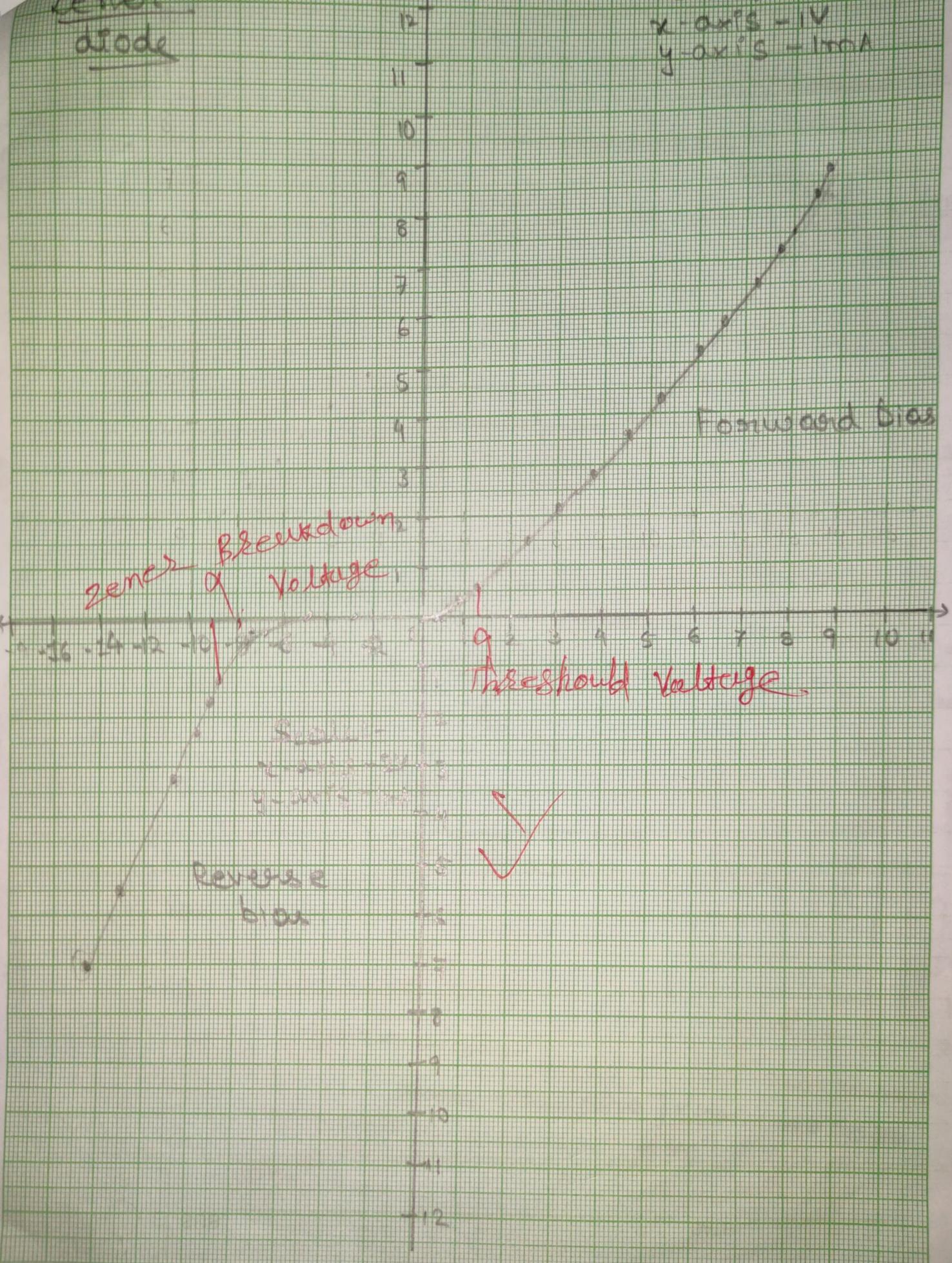


Exp. 1: DESIGN OF REGULATED POWER SUPPLY

Observations:

$$V_{rms} = 15 \text{ V}; \text{ Frequency} = 50 \text{ Hz}$$


Volt/div = 20V Time/div = 10ms

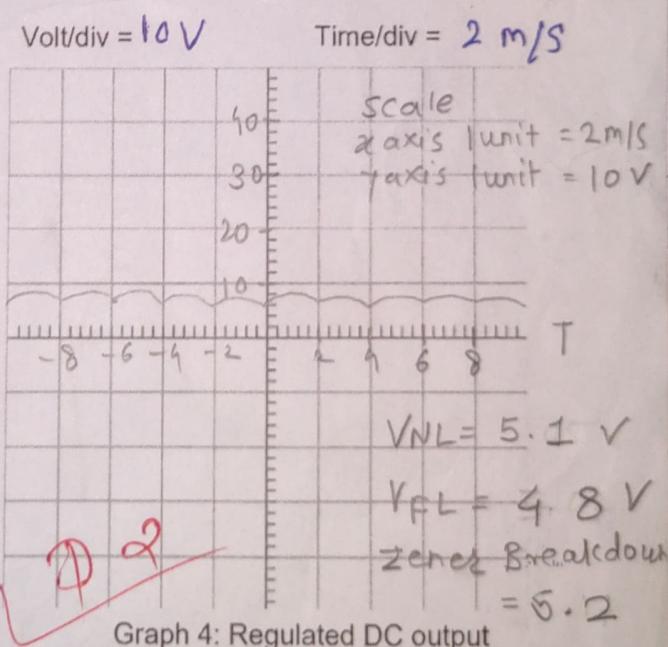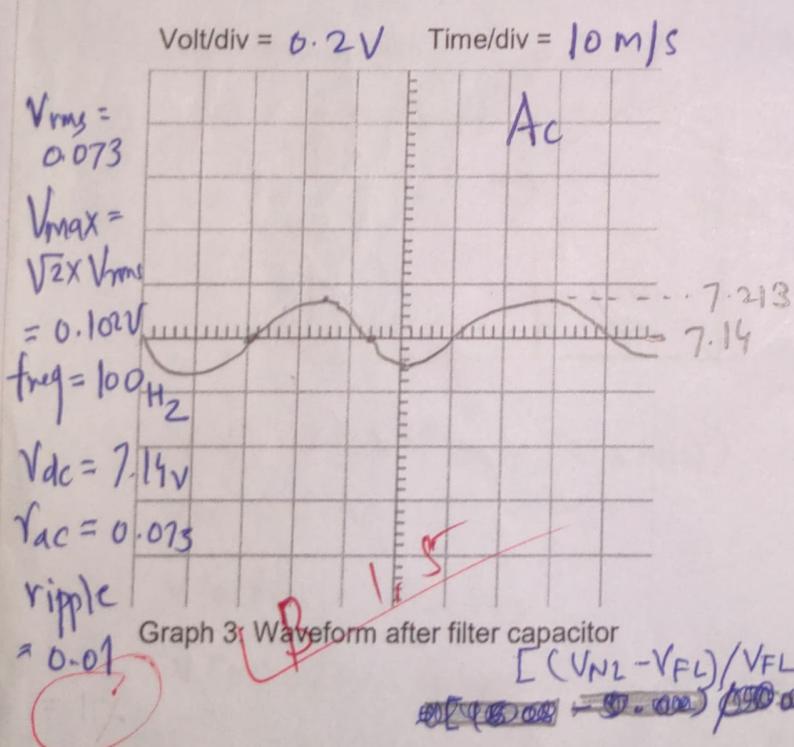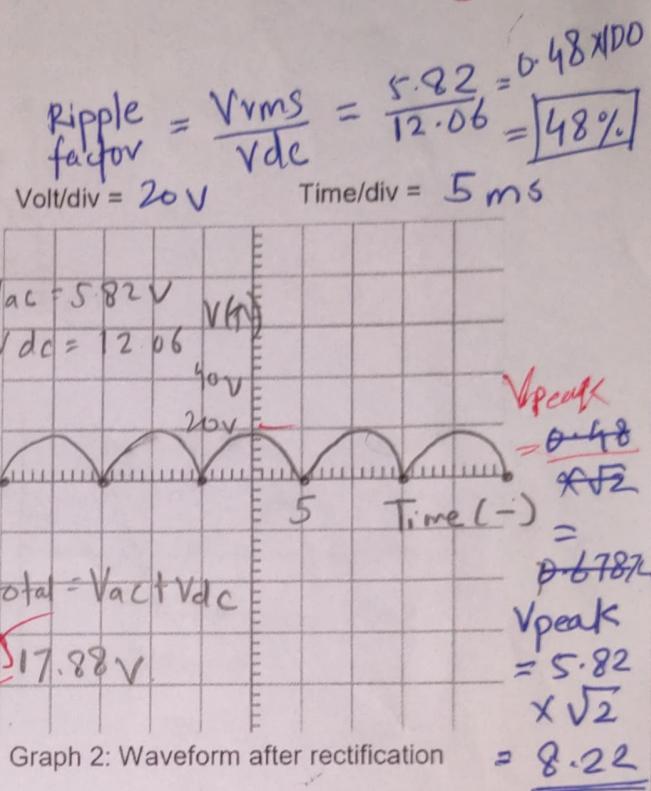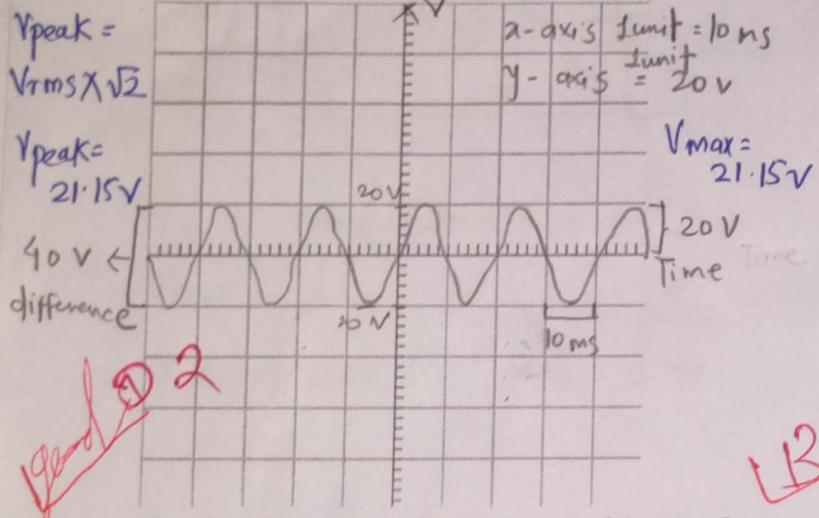

clamping circuit & clipper circuit:

Clamper circuit: To study +ve and -ve clamper circuits

Circuit diagram:

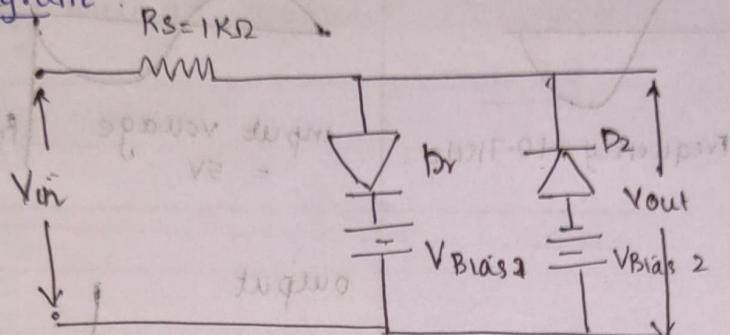


$$V_{in} = \pm 10V (\sin(2\pi 2kHz))$$

$$V_{Bias_1} = 0.9V$$

$$V_{Bias_2} = 3.6V$$


$$V_{D1} = 0.7V$$

$$V_{D2} = 0.7V$$

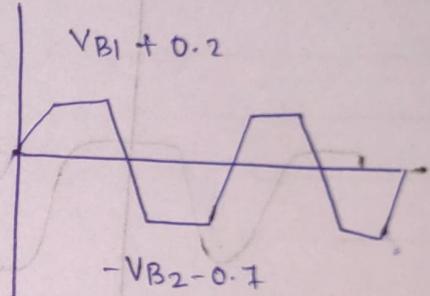

① Aim: to study the +ve clamper circuit

Circuit diagram:

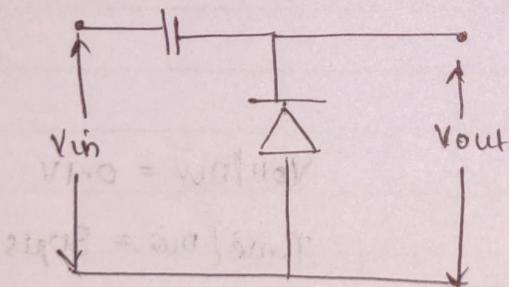


$$V_{in} = \pm 10V (\sin(2\pi 2kHz))$$

$$V_D = 0.7V$$

$$V_{DC} = -4.72V$$


$$V_{out} = 4.58V$$

Range: 0 to 5mV

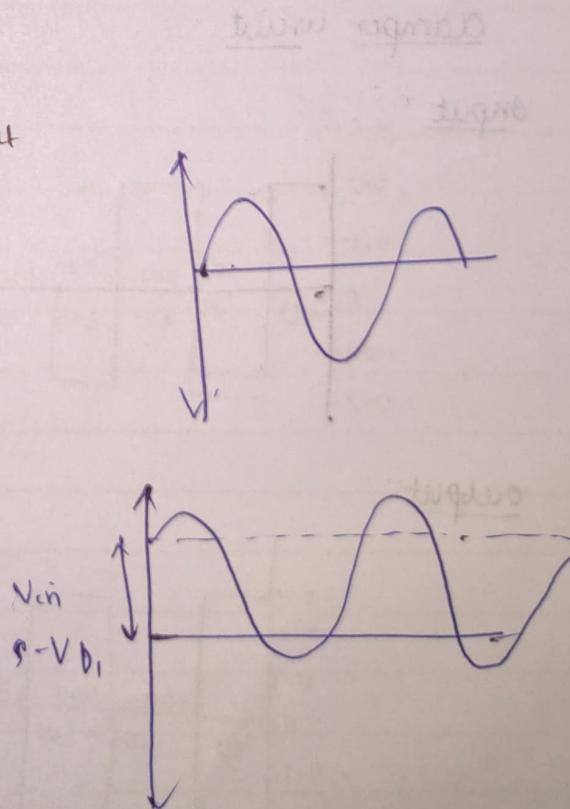


Coupler circuit

Forward Bias

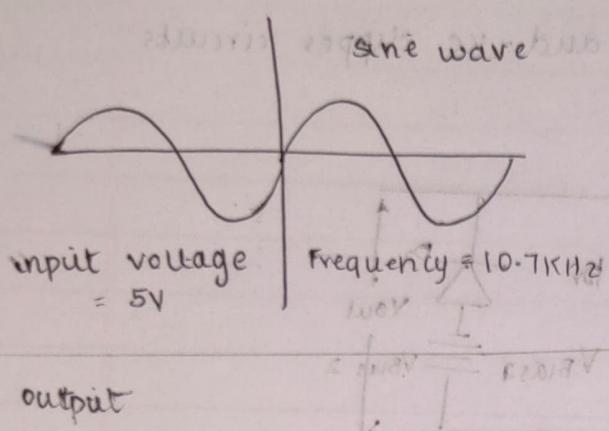


Reverse Bias

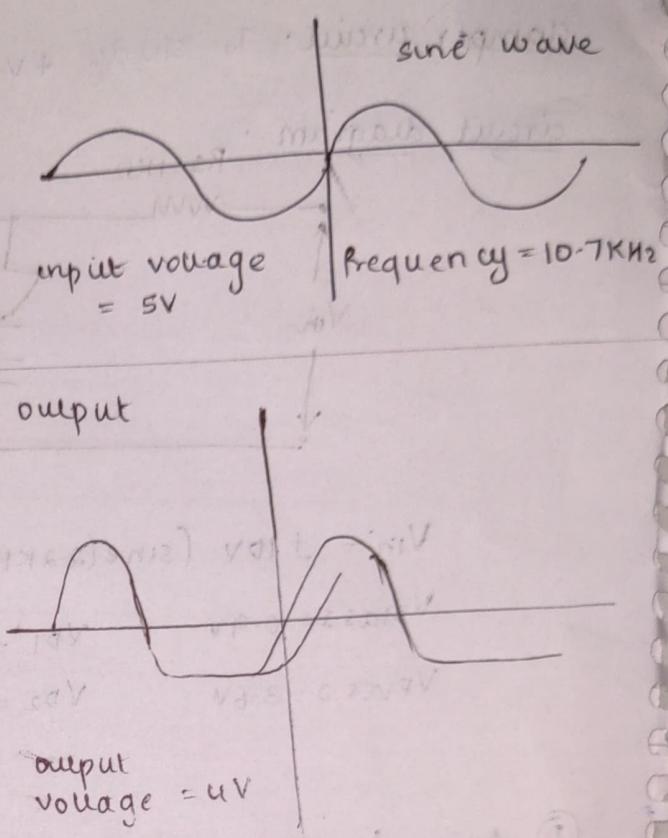

Clamper circuit


Input

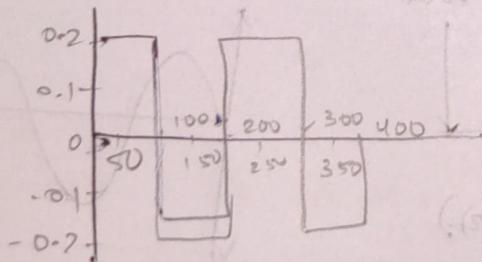

$$V_{O1}/DIV = 0.1V$$

$$\text{Time/DIV} = 50\mu s$$

Output:

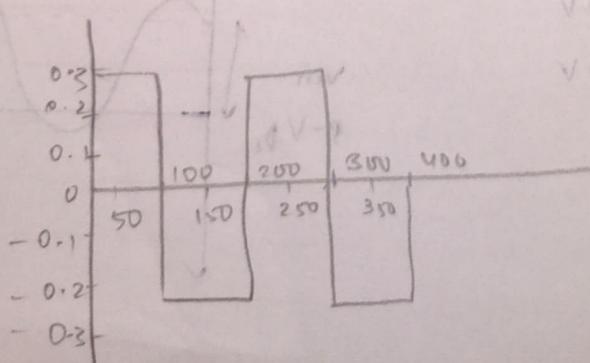

$$V_{O2}/DIV = 0.1V$$

$$\text{Time/DIV} = 50\mu s$$

damping voltage ΔU :

$$\text{Peak voltage before damping} = 0.2V$$

$$\text{Peak voltage before damping} = 0.3V$$

$$\text{damping voltage difference} = 0.3 - 0.2$$

$$= \underline{0.1V}$$

Aim :- To understand the characteristics of a Light Dependent Resistor (LDR) and use it to design a light dependent electronic switch.

A] Measurement of Resistance of the given LDR :-

Resistance (in ohm) of LDR measured under following cond'	
In Dark (placed within black box)	30.1×10^6
Under Laboratory Lighting	16.8×10^3
Under Solar Radiation	276.075 Ω

B] Study of the characteristics of the given LDR .

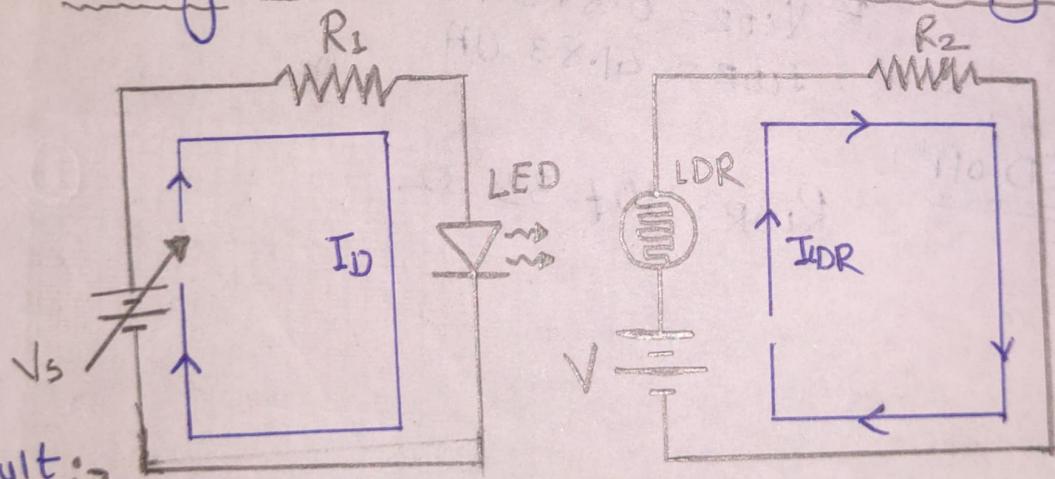



Fig. Circuit design to study the characteristics of LDR .

Result:

Voltage	I_{LDR} (mA)	I_D (mA)
2.7	0.35	0.0685
3	0.484	0.2065
3.5	0.68	0.4465
4	0.829	0.681
4.2	0.887	0.7805
4.5	0.960	0.9345
4.7	0.992	1.019
5	1.068	1.182

C] Application of LDR : Design and analyze light dependent electronic switches

circuit dia:-

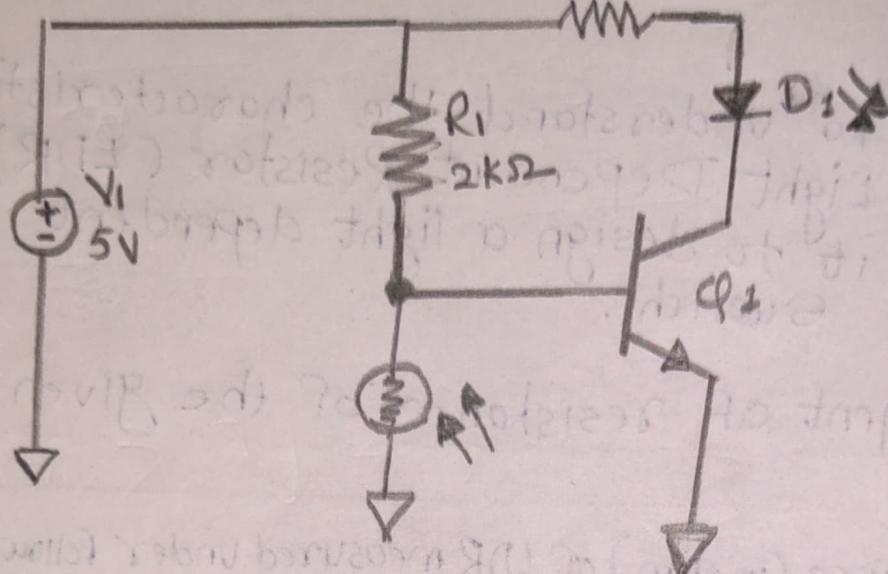

Application of LDR as light sensor to design an electronic switch

Readings:-

LED ON :

$$R_{LDR} = \frac{V_{LDR}}{I_{LDR}}$$


$$R_{LDR} = 20.75 \text{ k}\Omega$$

$$V_{LDR} = 0.868 \text{ V}$$

$$I_{LDR} = 41.83 \text{ nA}$$

LED off :

$$R_{LDR} = 107.33 \Omega$$

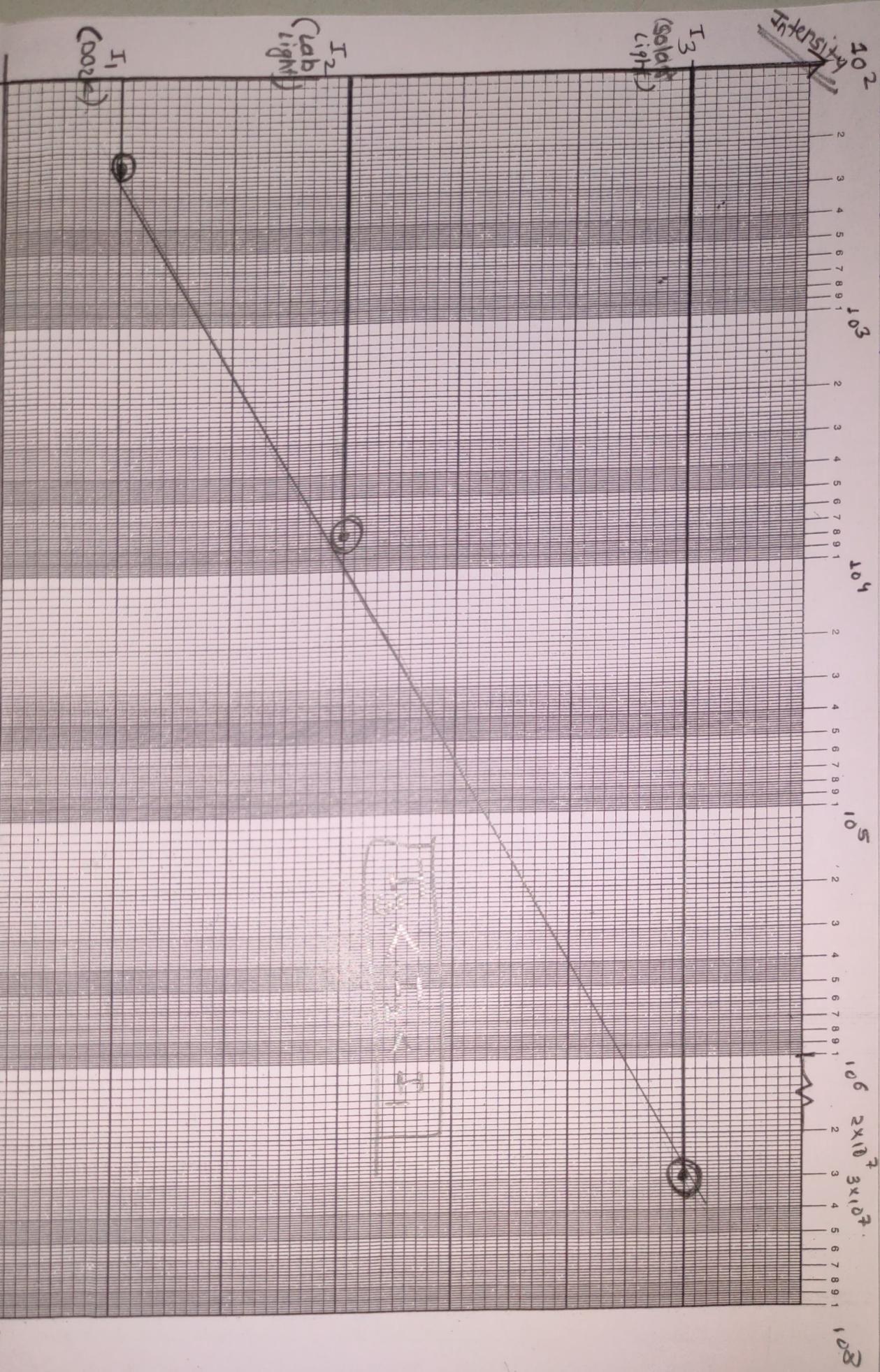


ght
ches
iv Kailas Rathod

SEMI-LOG PAPER (5 CYCLES X 1/10ⁿ)

AMUL RC22

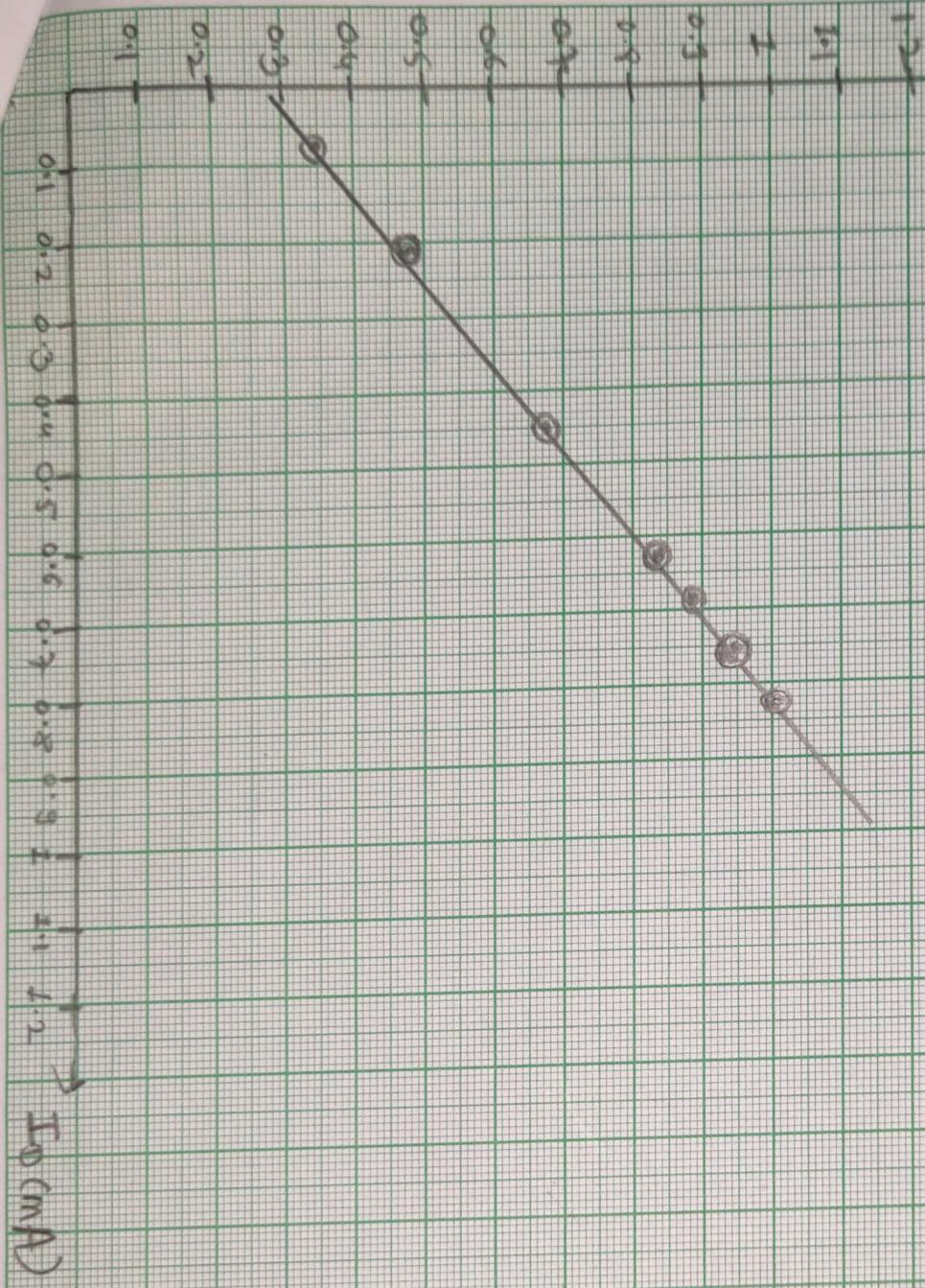Scale:
X axis 1 unit = 0.1mA
Y axis: 1 unit = 0.1mA



Laboratory Report

Experiment-08: (i) To design a Common-Emitter Transistor (*n-p-n*) Amplifier Circuit. (ii) To obtain the frequency response curve of the amplifier and to determine the mid-frequency gain, A_{mid} , lower and higher cut-off frequency of the amplifier circuit.

Observations:

(30 k Ω) (4.6 k Ω) (4.4 k Ω) (1 k Ω)

$\beta = 100$, $R_1 = 27 \text{ k}\Omega$, $R_2 = 5 \text{ k}\Omega$, $R_C = 4 \text{ k}\Omega$, $R_E = 1 \text{ k}\Omega$, $R_L = \dots$,

~~C₁ = 1 μF~~, $C_2 = 1 \mu\text{F}$, $C_E = 100 \mu\text{F}$.

value 1 → value from ideal resistors

Value 2 → Value from actual gives resistors

Table-I: D.C. Analysis of the circuit (For $V_{CC} = 12\text{V}$)

Parameter	Computed Value (Theoretical)	Observed Value (Experimental)
V_B (in V)	1.94 (1.6)	1.5 V
V_E (in V)	1.24 (0.9)	0.8 V
$I_C \sim I_E$ (in mA)	1.24 (0.9)	0.8 mA
V_{CE} (in V)	5.8 (7.85)	7.9 V

DC Q-point is at (.....V,mA)

Table-II: A.C. Analysis of the circuit.

Parameter	Computed Value (Theoretical)	Observed Value (Experimental)
r'_e (in Ω)		
$Z_{in(base)}$ (in Ω)		
$Z_{in(stage)}$ (in Ω)		
r_c (in Ω)		
A_v		

Q point
when no input signal is applied then, I_C & V_{CE} should be measured

$$\text{Gain} = 20 \log_{10} \left| \frac{V_o}{V_{in}} \right| \text{dB}$$

Table-II: Frequency response: $V_{i(pp)} = \dots$ mV

S. No	Frequency, f (in Hz)	$V_{o(pp)}$ (V)	Gain, $A_v = V_{o(pp)}/V_{i(pp)}$	Gain (in dB)
1.	100	0.15	3.75	11.4
2.	120	0.15	3.75	11.4
3.	150	0.16	4.0	12.0
4.	200	0.16	4.0	12.0
5.	500	0.17	4.25	12.6
6.	10^3	0.18	4.5	13
7.	1.2×10^3	0.19	4.7	13.5
8.	1.5×10^3	0.19	4.7	13.5
9.	5×10^3	0.19	4.7	13.5
10.	10^4	0.20	5.0	14
11.	20×10^3	0.24	6.0	15.6
12.	50×10^3	0.245	6.2	15.8
13.	10^5	0.22	5.5	14.8
14.	500×10^3	0.19	4.75	13.5
15.	10^6	0.19	4.75	13.5
16.	2×10^6	0.18	4.5	13
17.	5×10^6	0.18	4.5	13
18.	10×10^6	0.18	4.5	13

$\frac{V_o}{V_{sig}}$

scale
X-axis: unit = $\times 10^4$ Hz
Y-axis: unit = 1 dB

17
16
15
14
13
12
11
10
9
8
7
6
5
4
3
2
1

Low frequency band

→

High frequency band

→

Passband

Cliping

a minor change of value between C and C_{out} of the BJT.

