

Field Effect Transistors (FETs)

1. They are unipolar devices — operation depends on only one type of charge-carriers (free electrons & holes).
2. It means FET has majority charge-carriers (No minority carriers).
Majority charge-carrier devices.
3. FETs are preferred devices for most switching applications.
(No stored minority charge has to be removed from the junction area.)
4. FETs are voltage-controlled devices. (Field)
(BJTs are current-controlled devices)
5. Drift Transport of majority charge-carriers.


Reasons for popularity of FETs:

1. Operation of FETs is very simple.
2. Fabrication of FETs requires few steps.
3. FET requires $\frac{1}{5}$ th space as compared to BJTs.
(High density of the devices on the chip).


Types of FETs :

1. Junction Field effect transistor (JFETs) or simply FETs
2. Metal-Oxide Semiconductor field effect transistors (MOSFETs)


JFETs :

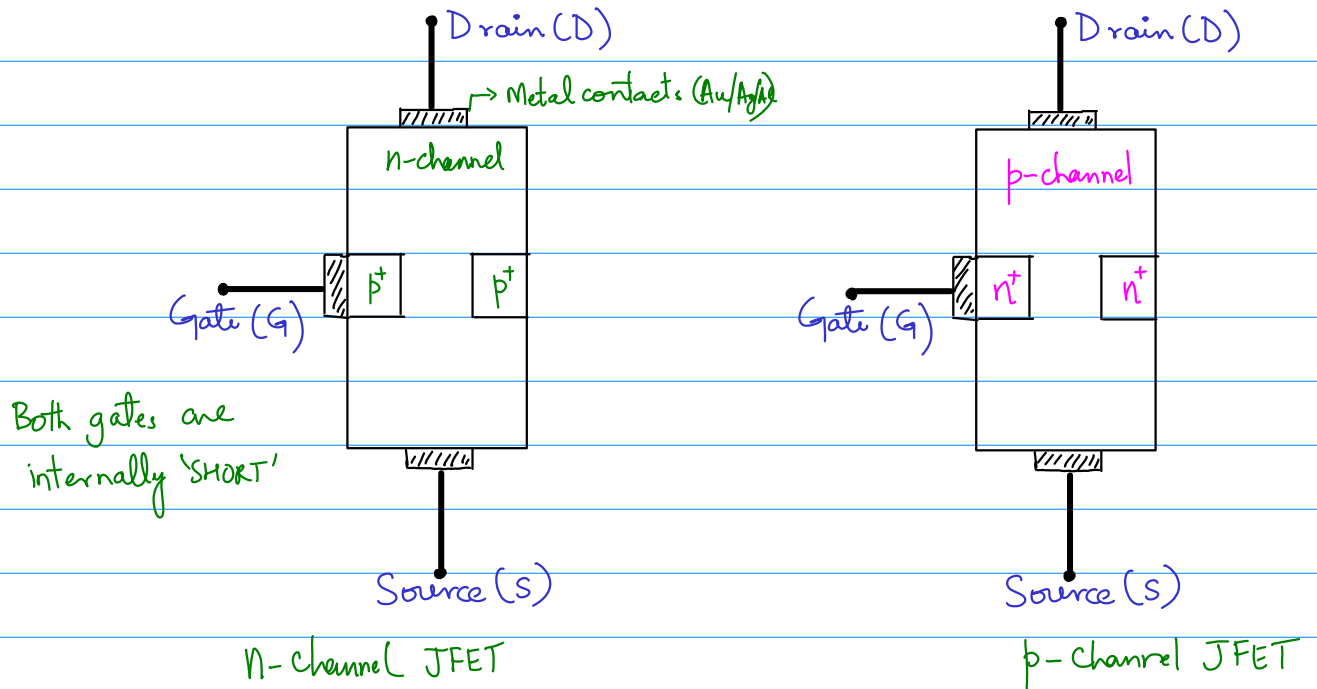


Basic Operation :

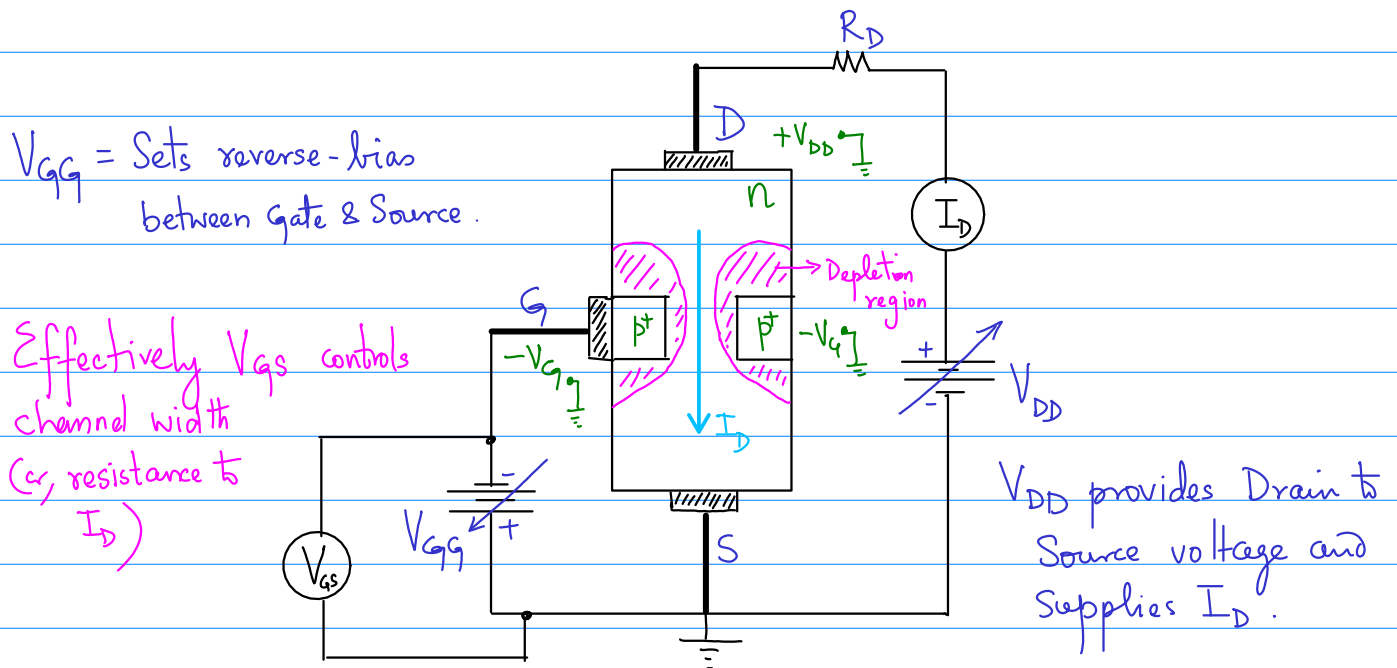


JFET characteristics and parameter:

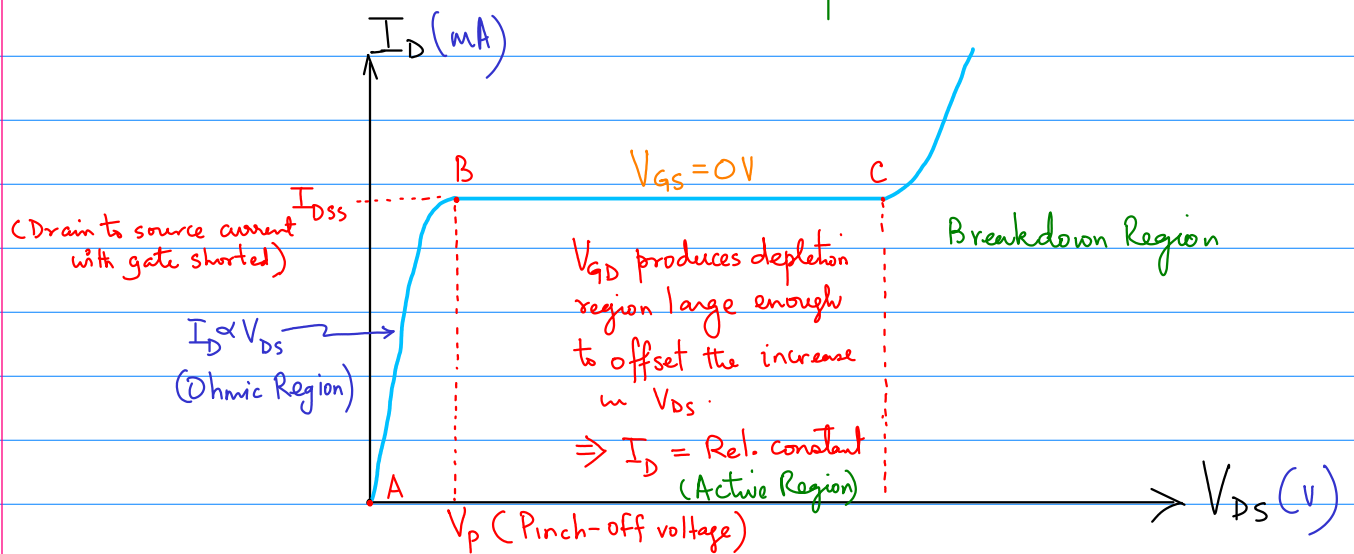

Full-Characteristics Curves:

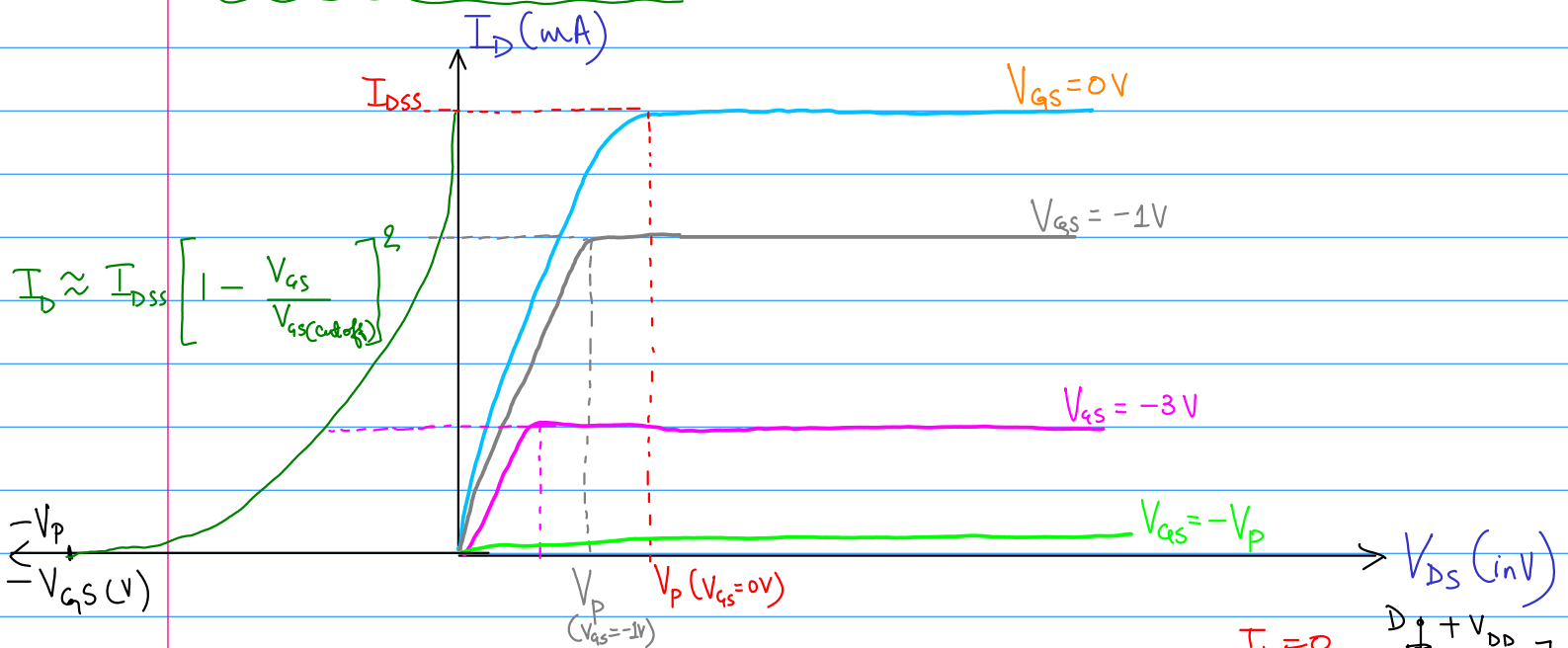
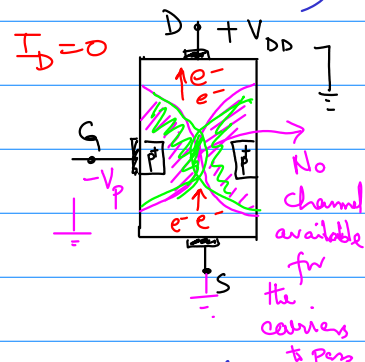
$$V_{GS(cut-off)} = -V_P \quad \text{where } I_D = 0$$



A JFET transfer characteristic curve is expressed approximately as:

$$I_D \approx I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(cut-off)}} \right)^2$$

Input Resistance and Capacitance:

- We have seen that JFETs operates with its Gate-Source junction in reverse biased.

⇒ High input resistance: Advantage of JFETs over BJTs.

$$\text{here } R_{in} = \left| \frac{V_{GS}}{I_{GSS}} \right|$$


Also, the input capacitance C_{iss} is a result of JFET operating in reverse-bias pn junction. Typically, $C_{iss} = \text{pF}$.

AC Drain to Source Resistance:


$$r'_{ds} = \frac{\Delta V_{DS}}{\Delta I_D}$$

Circuit Symbols:

Gate-Source is in Reverse bias

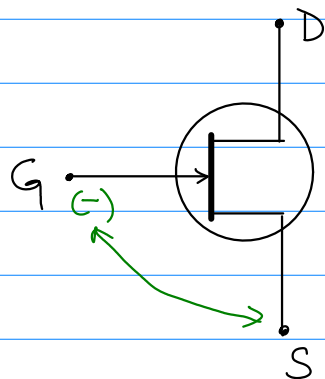

n-channel JFETs

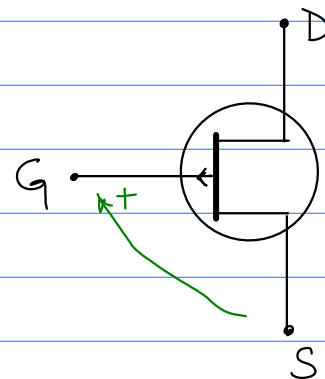


p-channel JFETs

Biasing of JFET :

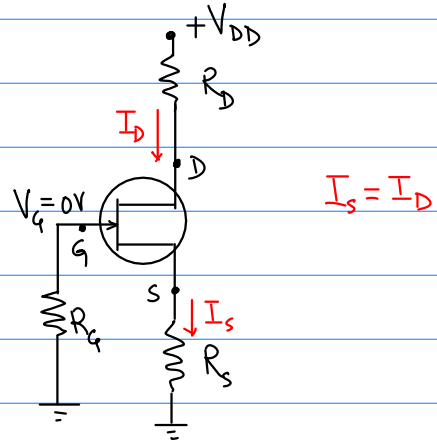(a) Self-Biasing

$$V_{GS} = V_G - V_S = 0V - I_D R_S = -I_D R_S$$

$$\Rightarrow \boxed{V_{GS} = -I_D R_S}$$



$$\text{Also, } V_D = V_{DD} - I_D R_D$$

$$\text{Hence, } V_{DS} = V_D - V_S = V_{DD} - I_D R_D - I_D R_S = V_{DD} - I_D (R_D + R_S)$$

$$\Rightarrow \boxed{V_{DS} = V_{DD} - I_D (R_D + R_S)} \quad \Rightarrow I_D = \frac{V_{DD}}{R_D + R_S} - \frac{V_{DS}}{R_D + R_S}$$

$$\Rightarrow I_D = \left(\frac{-1}{R_S + R_D} \right) \cdot V_{DS} + \frac{V_{DD}}{R_S + R_D}$$

Voltage-Divider Bias Ckt:

$$\Rightarrow Y = MX + C$$