

## Op-Amp. : Negative Feedback


Recap: (i) Ideal & Practical Op-Amp. Parameters

(ii) Differential & Common mode Operation


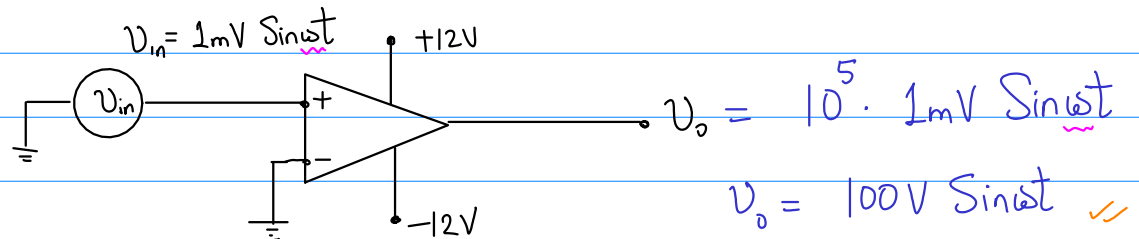
(iii) Inverting Op-Amp.  $(A_{CL(IN)} = -\frac{R_2}{R_1})$

Tune the gain as per the choice of the external resistors  $R_1$  &  $R_2$

Q: Let's understand what will happen when we connect the ckt. as per the following:



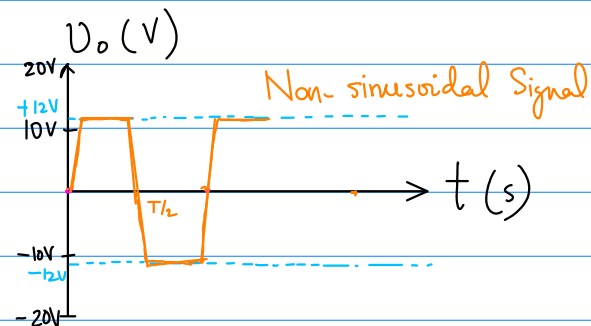
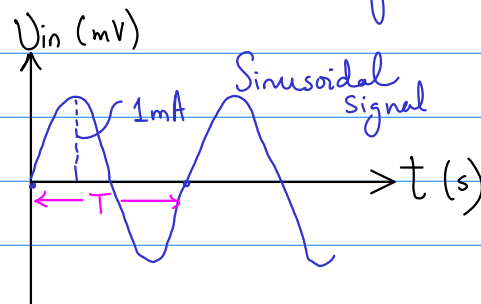
Assuming practical value of  $A_{OL} = 10^5$



## Negative Feedback:

1. Tune the gain of the op-amp with help of external ckt. element (Resistor).
2. By tuning the gain, we can restrict the op-amp to operate in linear regime. (Not to go into saturation regime).
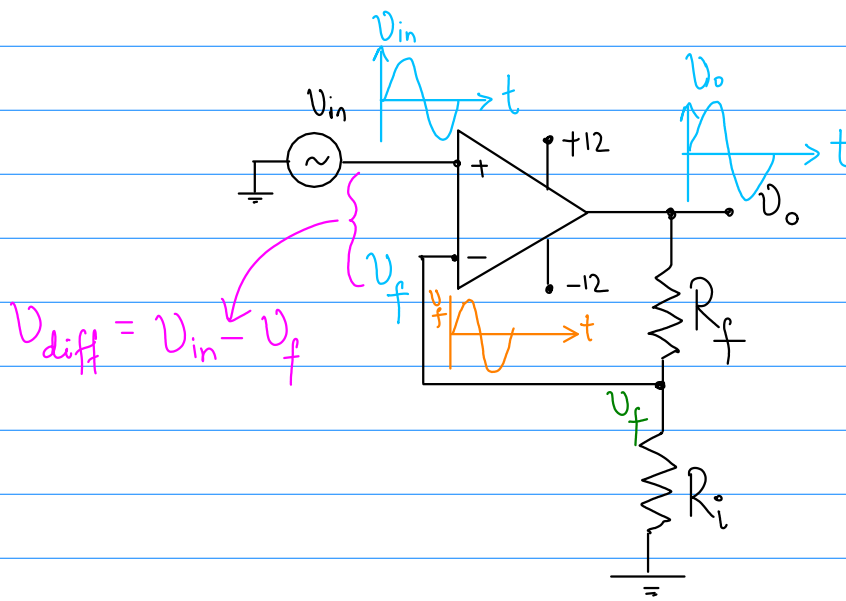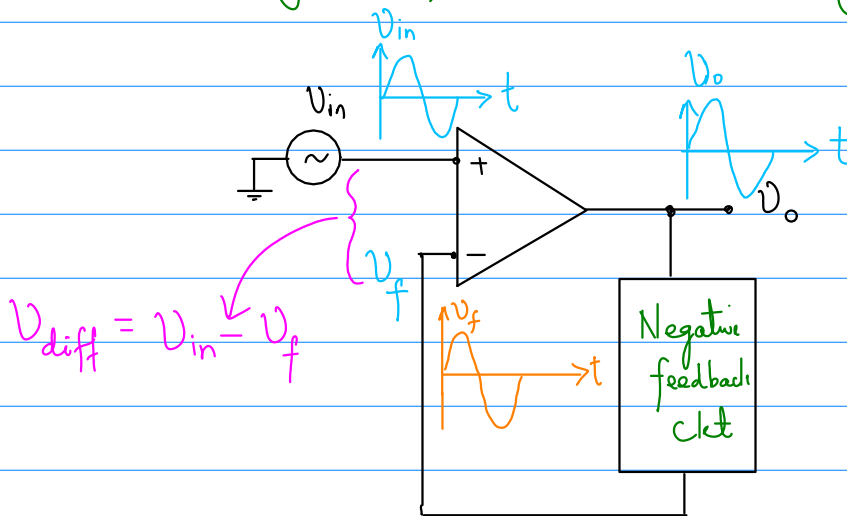
## Non-inverting Amp. ckt. with negative feedback:



$$V_f = \frac{R_i}{R_i + R_f} V_o$$

$$V_f = B V_o$$

$$\text{where } B = \frac{R_i}{R_i + R_f}$$

Now, with the negative feedback ckt, the op-amp have effective differential input voltage;

$$V_{\text{diff (input)}} = \underbrace{V_{\text{in}}}_{\text{applied to NI input}} - \underbrace{V_f}_{\text{applied to inverting input}}$$

$$V_{\text{diff (input)}} = V_{\text{in}} - B V_o \quad \text{where } B = \frac{R_i}{R_i + R_f}$$

If we have open-loop gain  $A_{OL}$

$$V_o = A_{OL} \cdot V_{\text{diff (input)}} \quad \text{where } A_{OL} = \text{Open-loop gain.}$$

$$\Rightarrow V_o = A_{OL} \cdot (V_{\text{in}} - B V_o)$$

$$\Rightarrow V_o + A_{OL} \cdot B \cdot V_o = A_{OL} \cdot V_{\text{in}}$$

$$\Rightarrow V_o (1 + A_{OL} \cdot B) = A_{OL} \cdot V_{\text{in}}$$

$$\Rightarrow \frac{V_o}{V_{\text{in}}} = \frac{A_{OL}}{1 + A_{OL} \cdot B}$$

$$\Rightarrow A_{CL(NI)} = \frac{V_o}{V_{\text{in}}} = \frac{A_{OL}}{1 + A_{OL} \cdot B}$$

$$\Rightarrow \boxed{A_{CL(NI)} = \frac{A_{OL}}{1 + A_{OL} \cdot B}}$$

As we know;  $A_{OL} \sim 10^4 - 10^6$  &  $B = \frac{R_i}{R_i + R_f}$

the product  $A_{OL} \cdot B \gg 1$

Under this cond<sup>n</sup>:

$$A_{CL(NI)} = \frac{A_{OL}}{A_{OL} \cdot B}$$

$$\Rightarrow A_{CL(NI)} = \frac{1}{B} = \frac{R_i + R_f}{R_i}$$

$$\Rightarrow A_{CL(NI)} = 1 + \frac{R_f}{R_i} \quad \text{under the cond}^n \quad A_{OL} \cdot B \gg 1$$

Conclusion: • Closed loop gain is independent of the value of the open loop gain.

OR


Closed loop gain is dependant on the external ckt element. ( $R_i$  &  $R_f$ )

	VOLTAGE GAIN	INPUT Z	OUTPUT Z	BANDWIDTH
1.) Without negative feedback	$A_{OL}$ is too high for <u>linear</u> amplifier applications $10^4 - 10^6$	Relatively high (see Table 12-1) $\sim M\Omega$	Relatively low $\sim \text{few } \Omega$	Relatively narrow (because the gain is so high) $1\text{Hz}$
2.) With negative feedback	$A_{CL}$ is set to desired value by the feedback circuit ( $R_i$ & $R_f$ ) dependent	Can be increased or reduced to a desired value depending on type of circuit ( $R_i$ & $R_f$ ) dependent	Can be reduced to a desired value ( $R_i$ & $R_f$ ) dependent	Significantly wider dependent

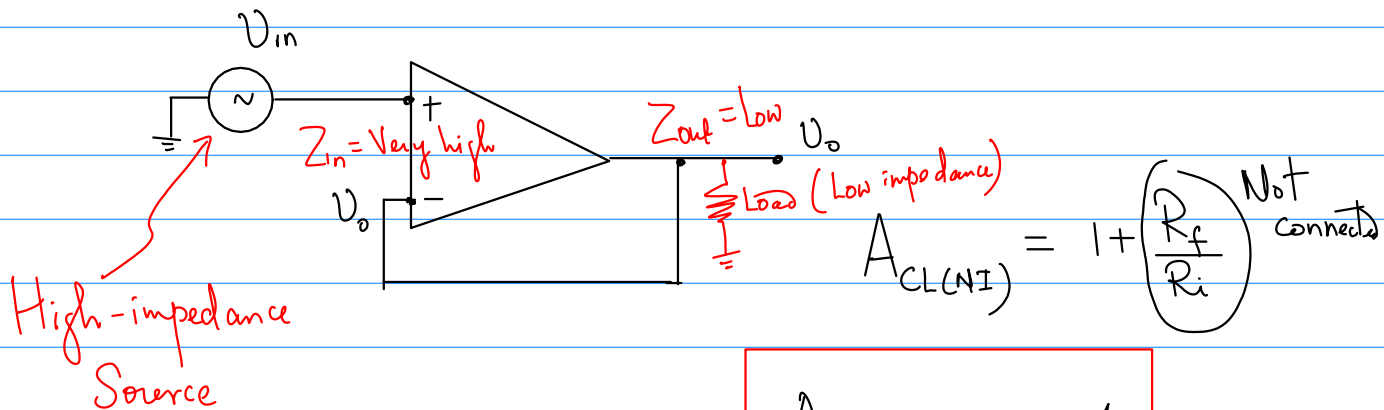
## Voltage-Follower ckt :

High-impedance Source  $\longrightarrow$  Low-impedance load.

$\Rightarrow$  in voltage-follower ckt :  $A_V = 1$  (unity)




$$A_{CL(NI)} \approx 1$$

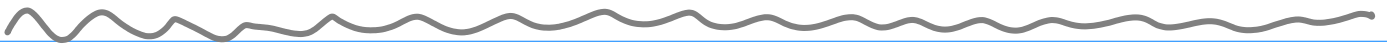

# Op-Amp : Applications
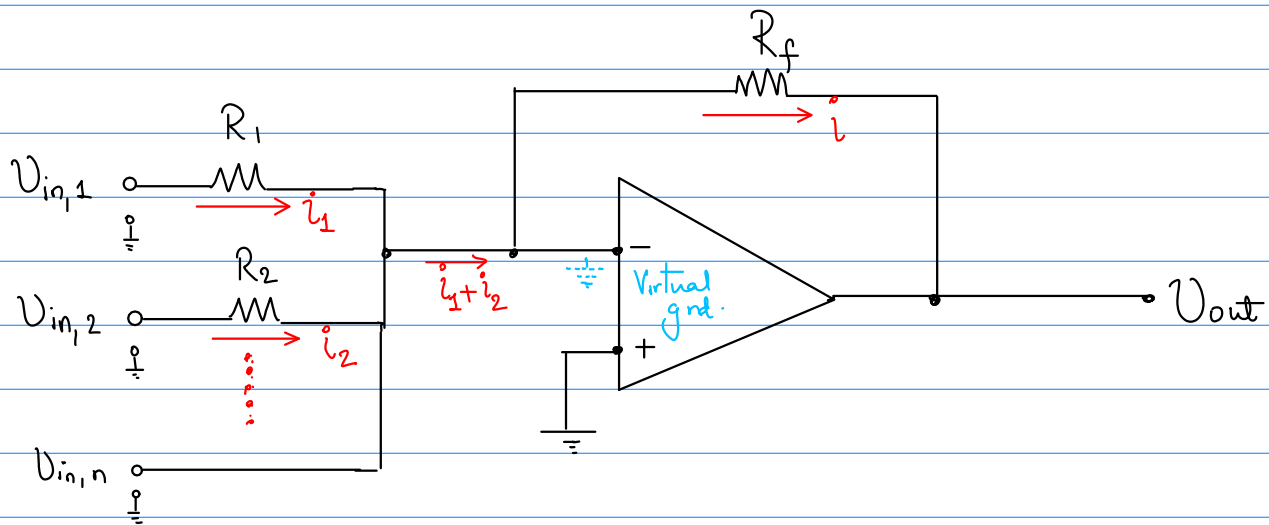
## 1. Summing Amplifiers :

- Make use of inverting op-amp configuration
- It has two or more input <sup>voltages</sup> connected to the inverting input terminal.
- Output voltage is proportional to negative of the algebraic sum of its input voltages



Total current through  $R_f$  is given as

$$i = i_1 + i_2 \quad \text{where, } i_1 = \frac{V_{in,1}}{R_1}$$

$$i_2 = \frac{V_{in,2}}{R_2}$$

here, 
$$V_{out} = -R_f i = -R_f (i_1 + i_2)$$

$$V_{out} = - \left[ \frac{V_{in,1}}{R_1} + \frac{V_{in,2}}{R_2} \right] R_f$$

finally,

$$V_{out} = - \left[ V_{in,1} \left( \frac{R_f}{R_1} \right) + V_{in,2} \left( \frac{R_f}{R_2} \right) \right]$$

Special Case:  $R_1 = R_2 = R_f = R$

$$V_{out} = - (V_{in,1} + V_{in,2})$$

(i) Generalization: Let we have 'n' number of input voltages  
and  $R_1 = R_2 = R_3 = \dots = R_f = R$

$$V_{out} = - (V_{in,1} + V_{in,2} + \dots + V_{in,n})$$

(ii) Summing amplifier with gain greater than unity

$$R_1 = R_2 = R_3 = \dots = R_n = R$$

$$R \neq R_f$$

$$V_{out} = - \underbrace{\frac{R_f}{R}} \left[ V_{in,1} + V_{in,2} + \dots + V_{in,n} \right]$$

factor with which the sum of inputs is multiplied with.

(iii) Lets choose  $\frac{R_f}{R} = \frac{1}{n}$  where 'n' is the number of input voltages.

$$V_{out} = -\frac{1}{n} [V_{in,1} + V_{in,2} + \dots + V_{in,n}]$$

$\uparrow$   
 $V_{out}$  (ave.)  $\rightarrow$  Averaging Operation.

(iv) Scaling Adder :


- Assigning different weights to each of the inputs of the summing amplifier.

$$V_{out} = - \left[ V_{in,1} \underbrace{\left( \frac{R_f}{R_1} \right)}_{\text{Weight to } V_{in,1}} + V_{in,2} \underbrace{\left( \frac{R_f}{R_2} \right)}_{\text{Weight to } V_{in,2}} + \dots + V_{in,n} \underbrace{\left( \frac{R_f}{R_n} \right)}_{\text{Weight to } V_{in,n}} \right]$$

2

Integrator Circuit :
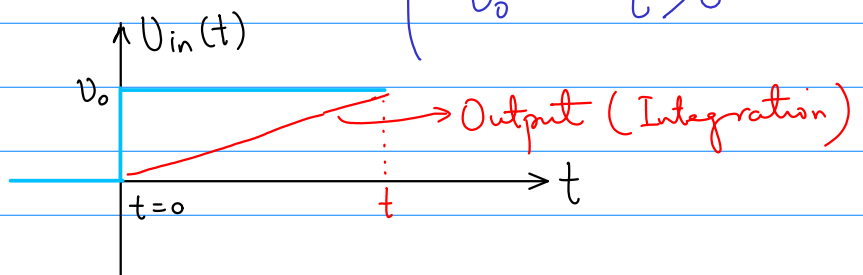
$$V_{in}(t) = \begin{cases} 0 & t < 0 \\ V_0 & t > 0 \end{cases}$$






Integration of input voltage

$$\int_{-\infty}^{\infty} V_{in}(t) dt = \underbrace{\int_{-\infty}^0 V_{in}(t) dt}_0 + \underbrace{\int_0^{\infty} V_{in}(t) dt}_{\int_0^t V_o dt} = V_o t$$

Integration of <sup>constant</sup> input voltage <sup>(w.r.t 't')</sup> is a linear function of 't'.

Ideal Integrator ckt :

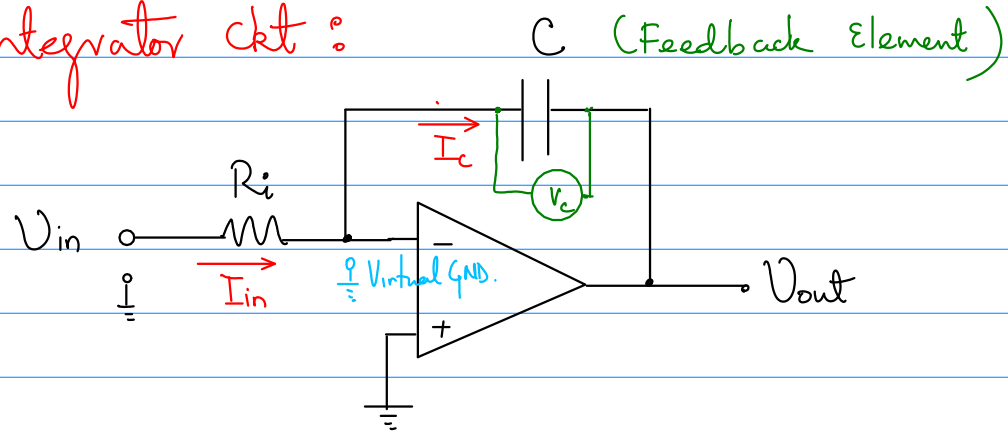

$$I_{in} = \frac{V_{in}}{R_i} = \text{Constant}$$

$$I_c = I_{in} = \text{Constant}$$

We know that the charge on the capacitor at any time 't' is given as

$$Q = I_c t$$

$$V_c = \frac{Q}{C} = \left( \frac{I_c}{C} \right) t$$

$$V_c = \left( \frac{I_c}{C} \right) t$$

$$\left\{ Y = mx + c \right\}$$

Now,  $V_{out} = -V_c = -\left(\frac{I_c}{C}\right) t$

$$V_{out} = -\left(\frac{V_{in}}{R_i C}\right) t$$

$$V_{out} = -\frac{1}{R_i C} V_{in} t$$

$$Y = Mx$$

$$M = -\frac{V_{in}}{R_i C}$$

$$x = t$$

$$Y = V_{out}$$

